
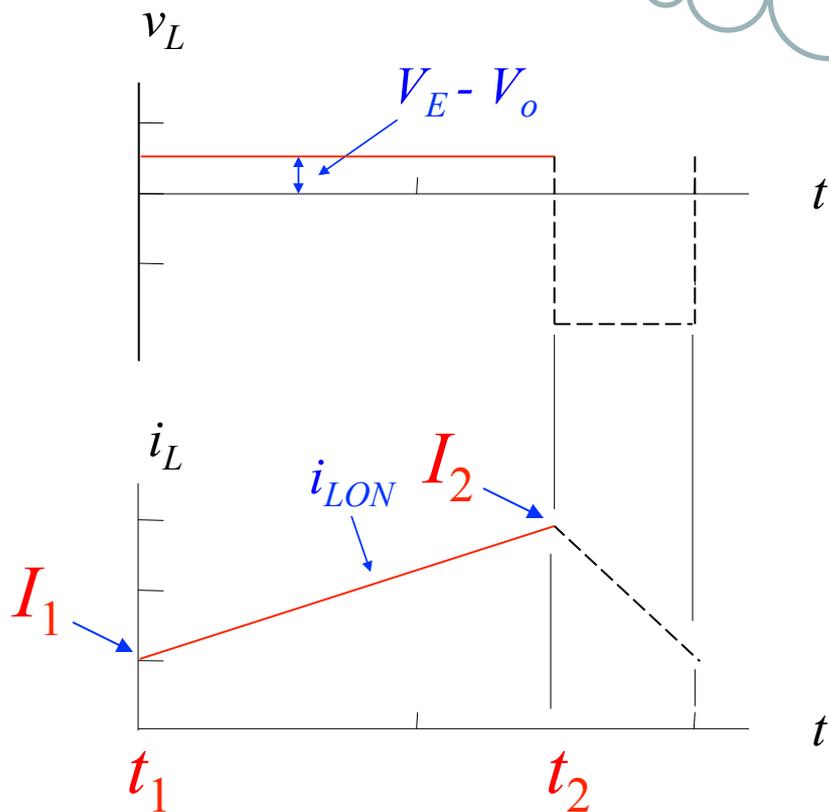
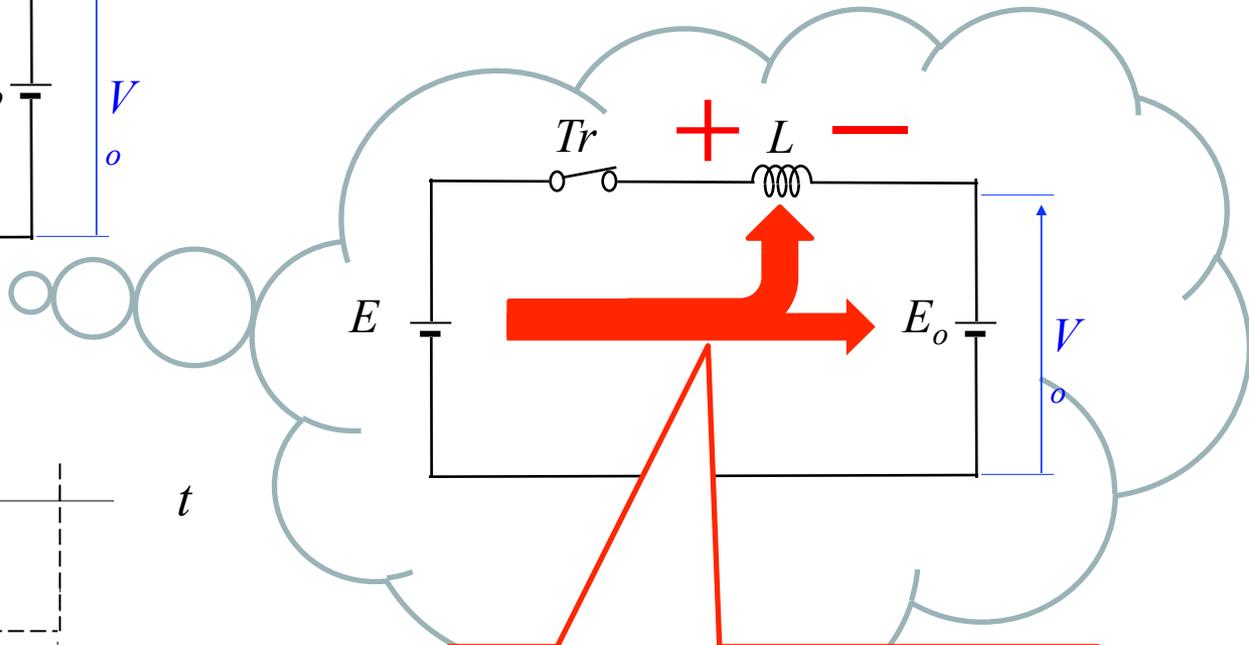


Power Electronics



No. 6: Step-up, Step-up/down choppers

Takeshi Furuhashi


Furuhashi_at_cse.nagoya-u.ac.jp

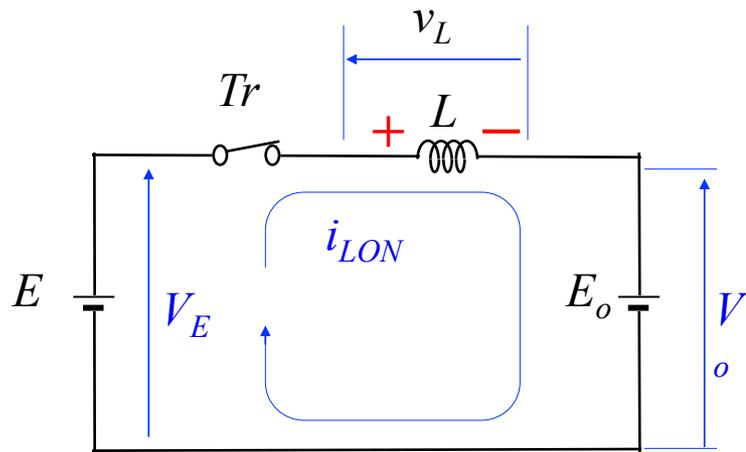


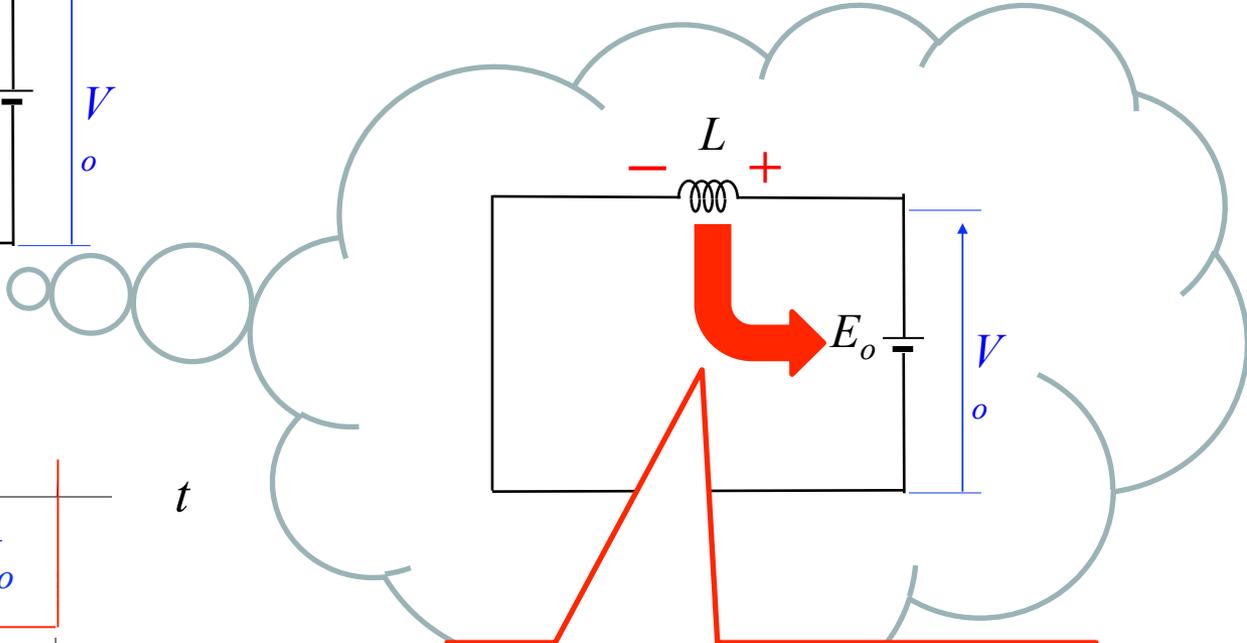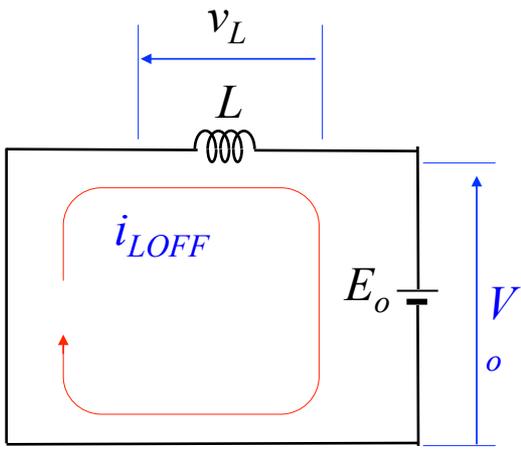Energy is supplied from the power source to reactor L and output voltage source E_o .



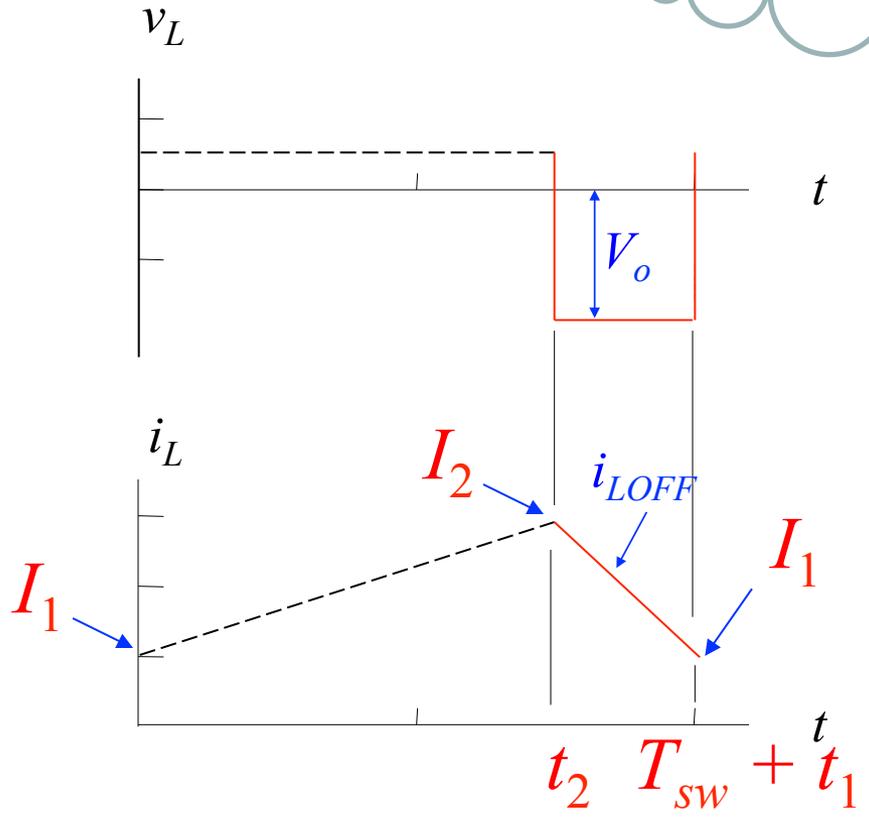Energy is supplied by reactor L to output voltage source E_o .



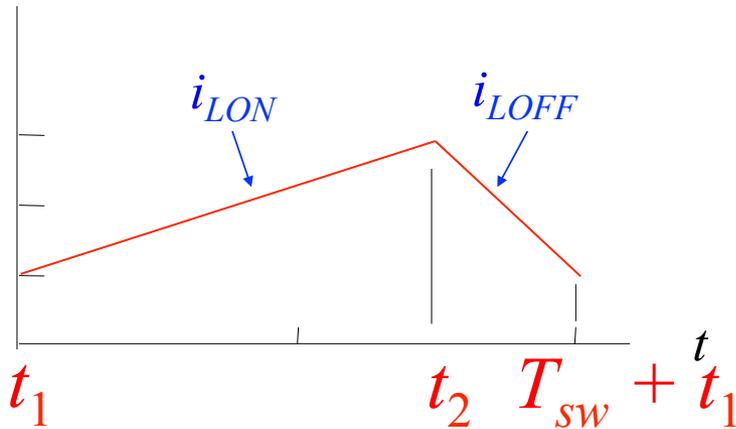




$$\Delta I = I_2 - I_1 = \frac{V_E - V_o}{L} \delta T_{SW}$$

$$\Delta I = I_2 - I_1 = \frac{V_o}{L} T_{SW} (1 - \delta)$$

The right hand side of both equations are equal.

$$\frac{V_E - V_o}{L} \delta T_{SW} = \frac{V_o}{L} T_{SW} (1 - \delta)$$

$$V_o = \delta V_E$$

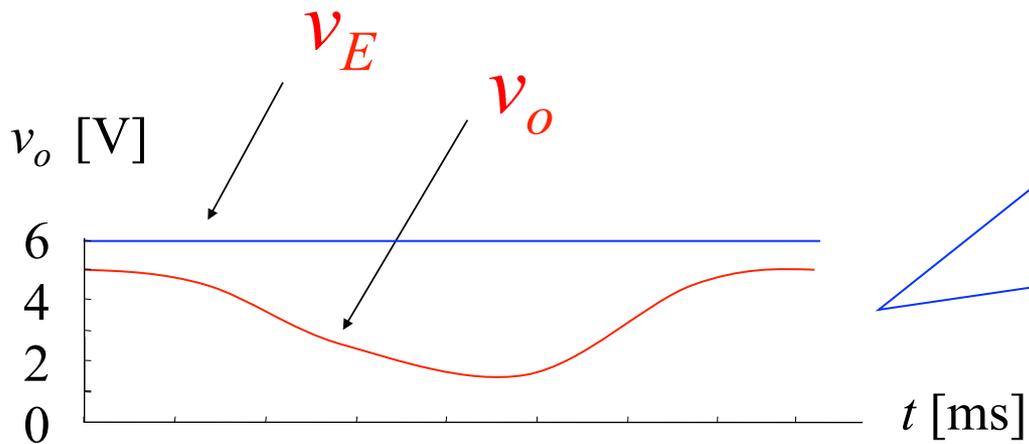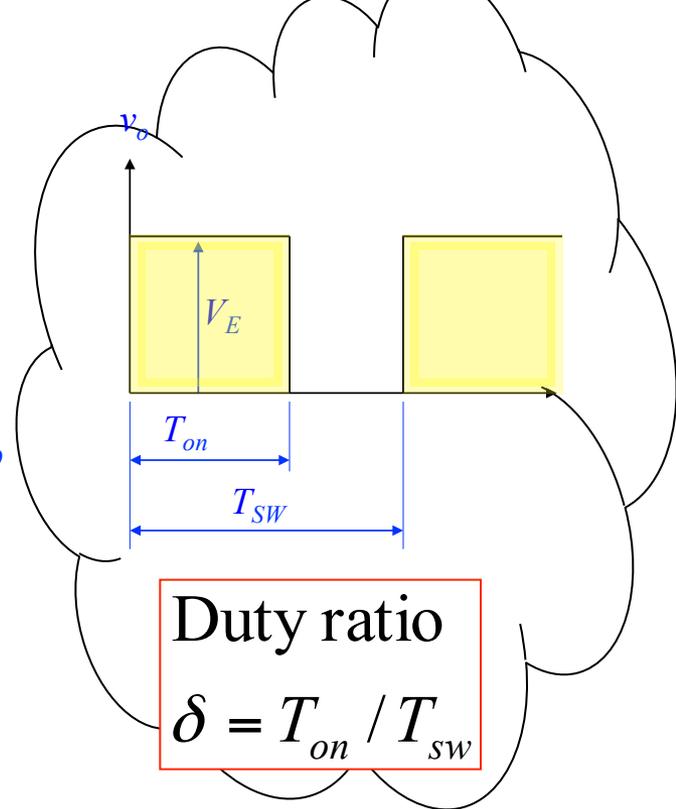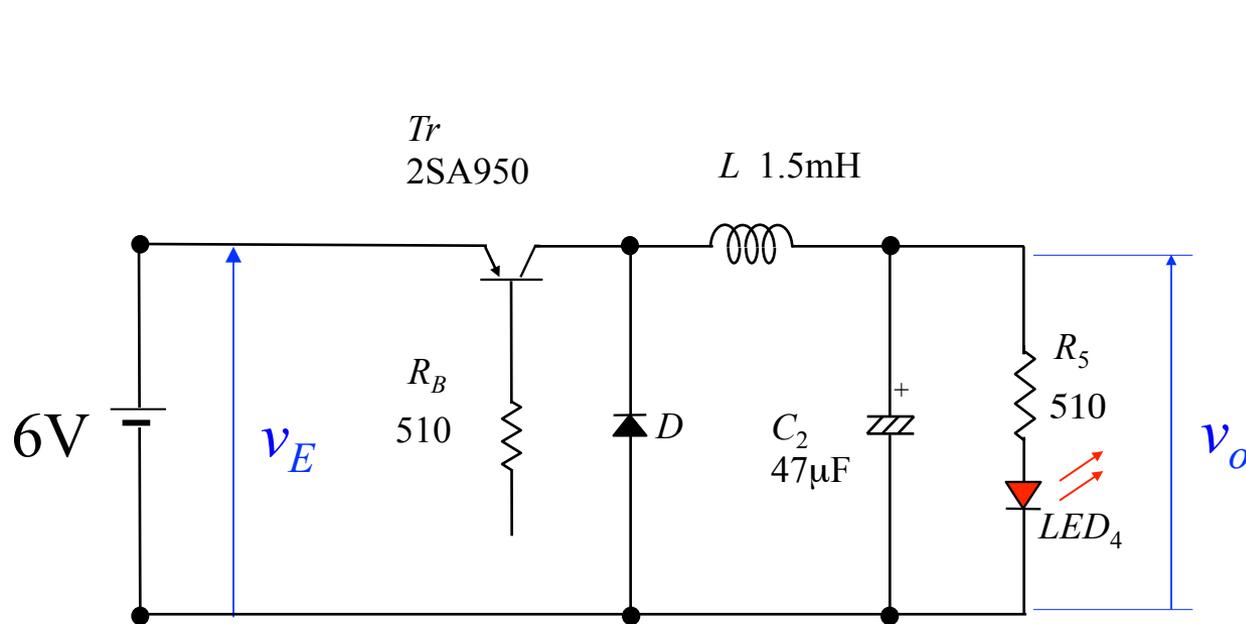


$$V_o = \delta V_E$$



$$0 \leq \delta \leq 1$$

The output voltage is not larger than the source voltage.

Step-up chopper

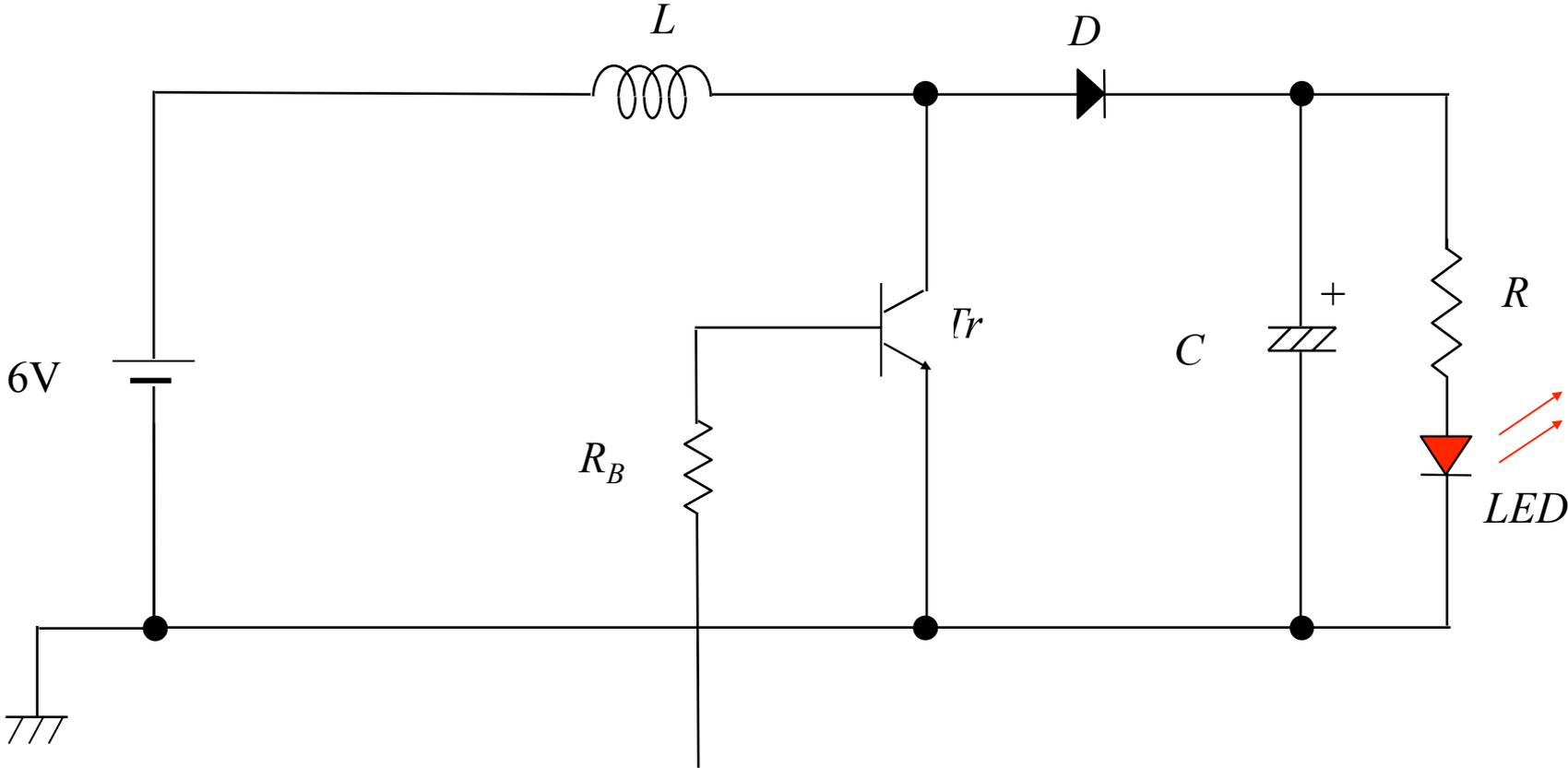


Step-up chopper

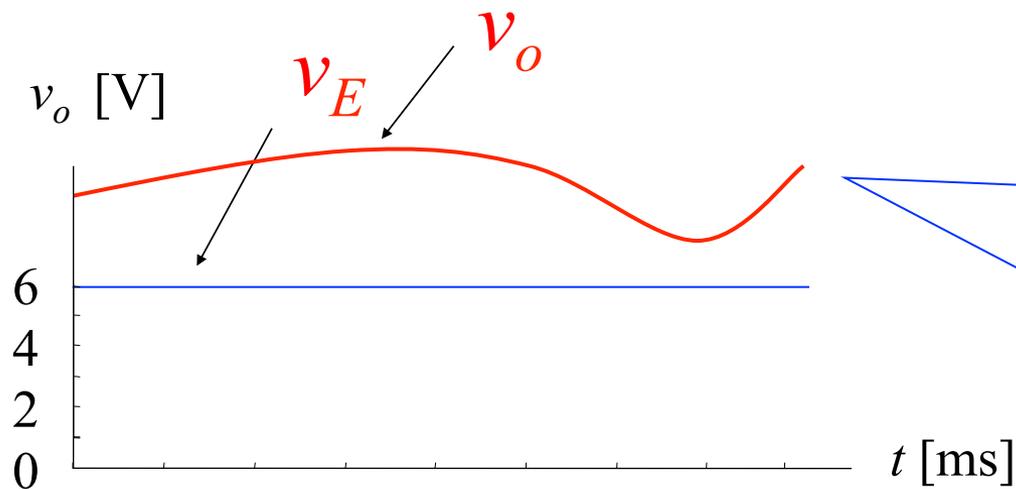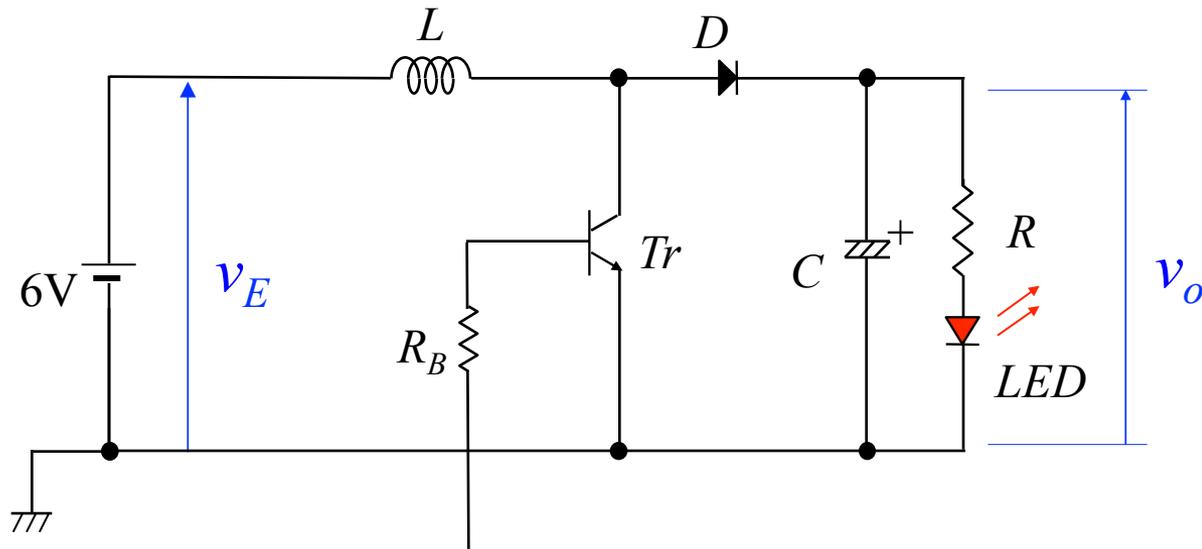


The output voltage is larger than the source voltage.

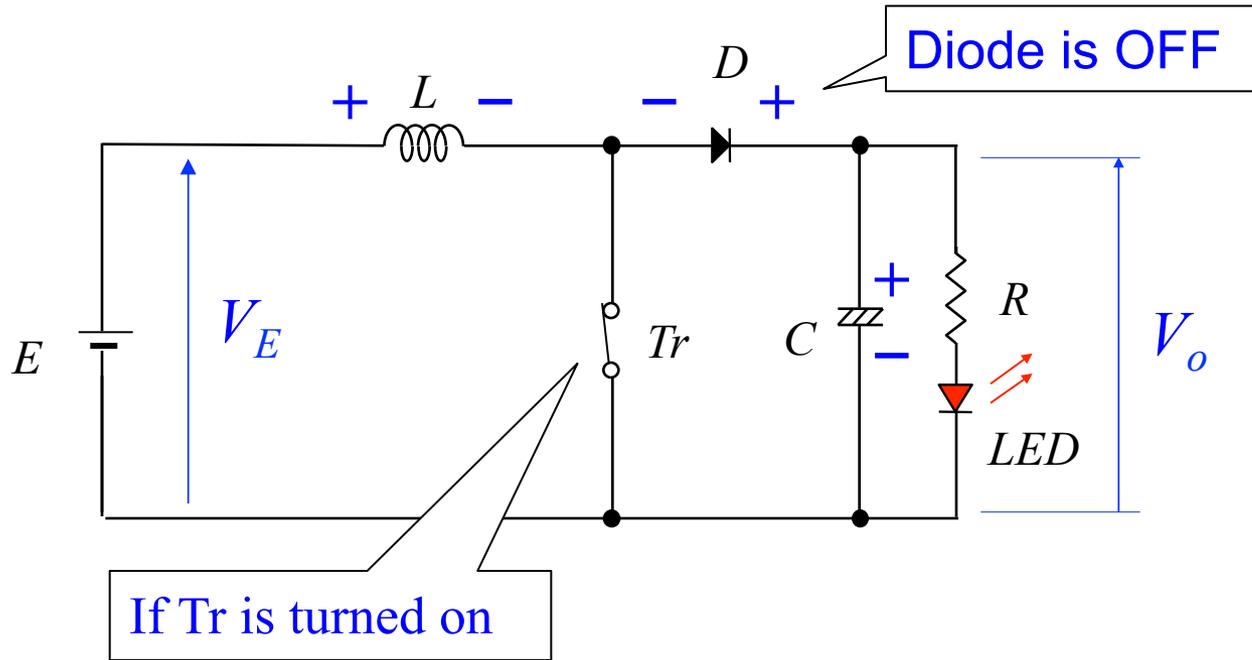
Operating principle of the step-up chopper




Assume that $V_o > V_E > 0$
 While Tr is turned off, current from the voltage source E to the capacitor C does not flow.

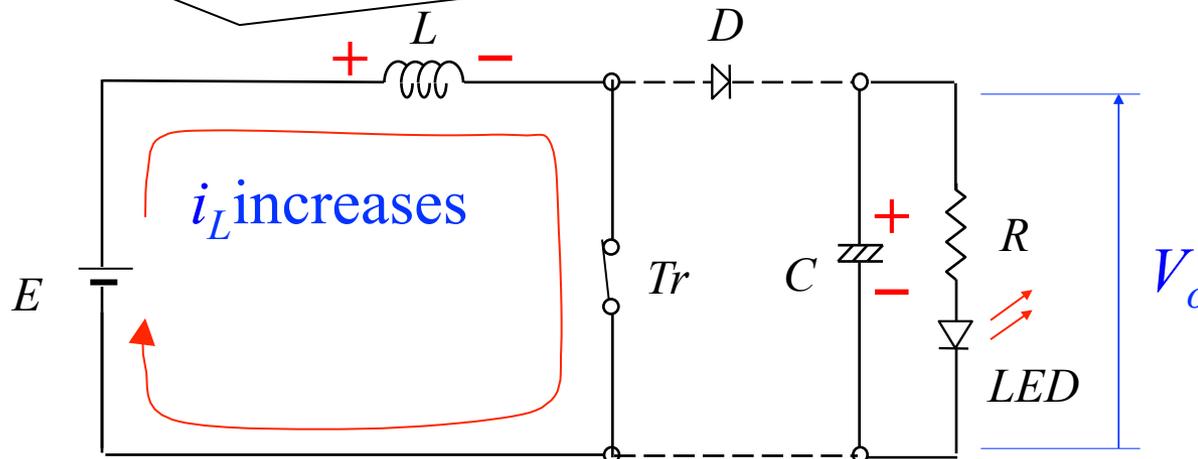Magnetic energy ($Li^2/2$) is accumulated in reactor L .



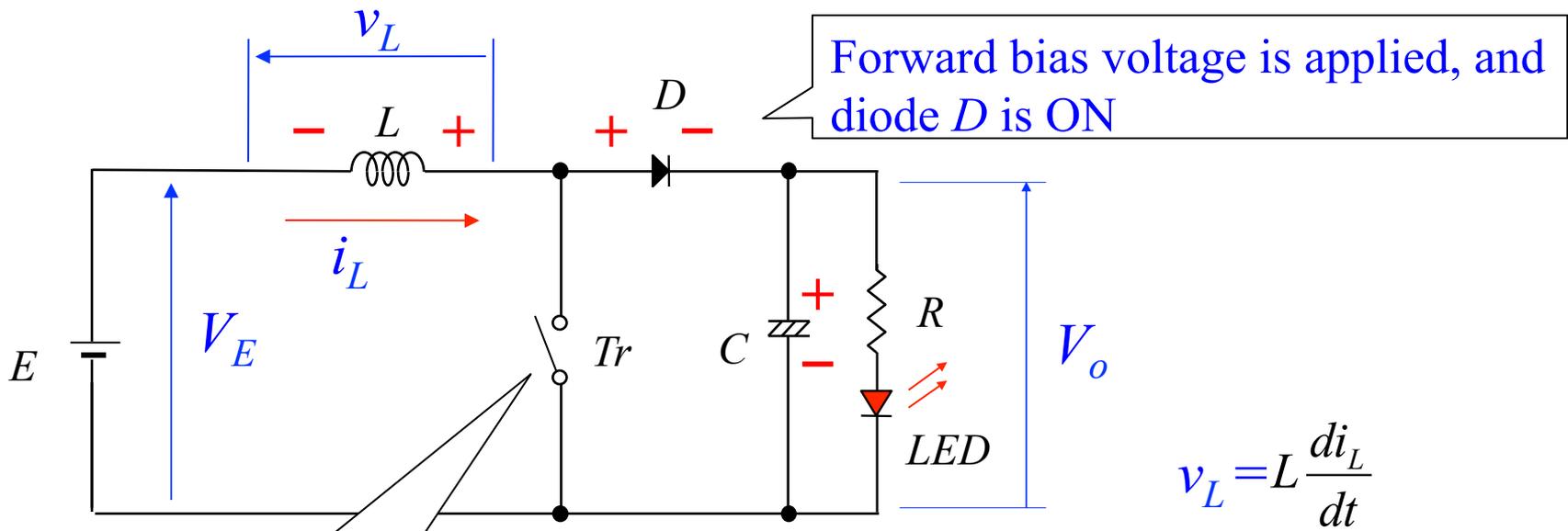

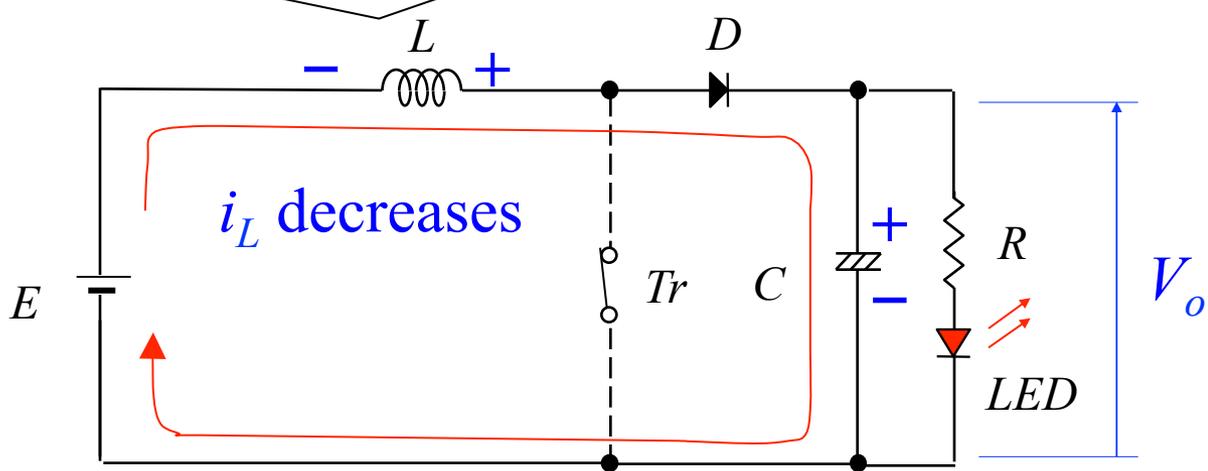Magnetic energy ($Li^2/2$) is discharged from reactor L .






When i_L decreases, $v_L < 0$. In this case, $V_E - v_L > V_o$.

PWM control method


If $v_{com} \geq v_{tri}$, then Tr is turned on.

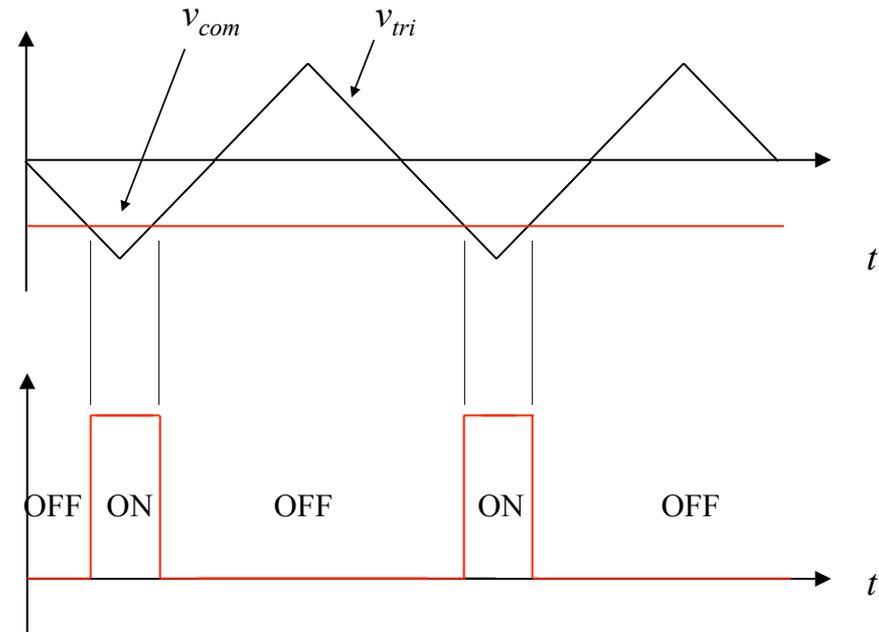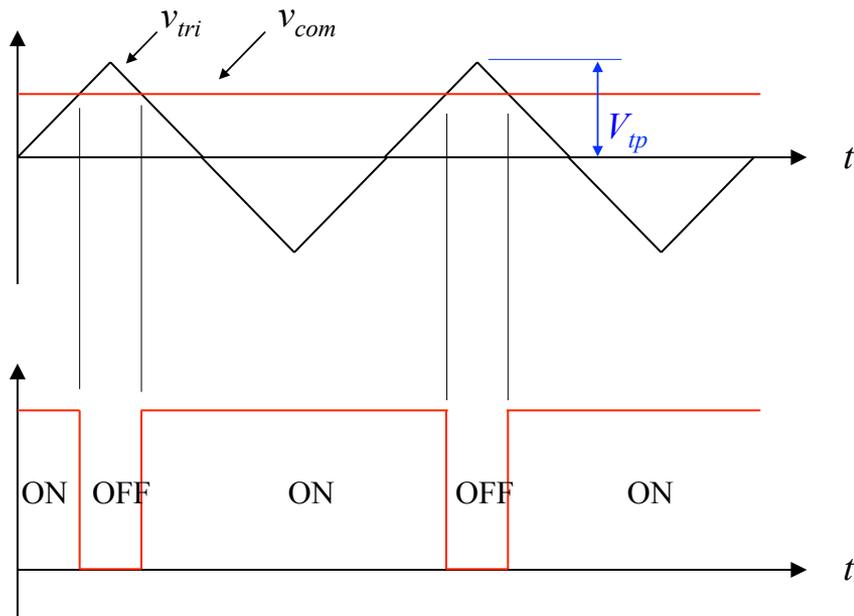If $v_{com} < v_{tri}$, then Tr is turned off.



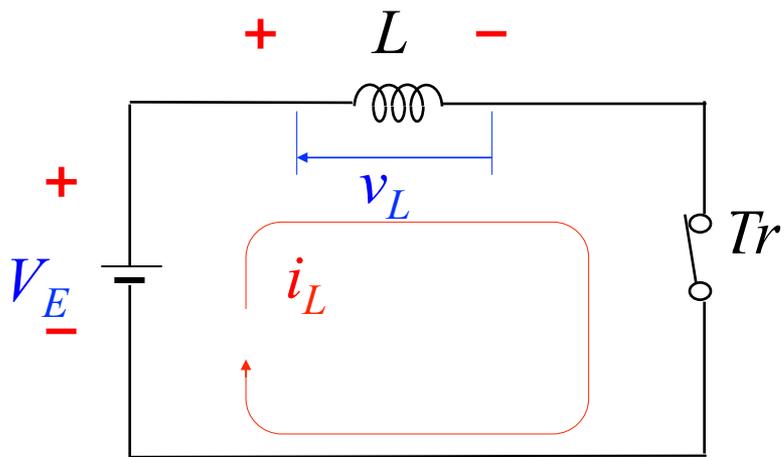


(a) Tr: ON

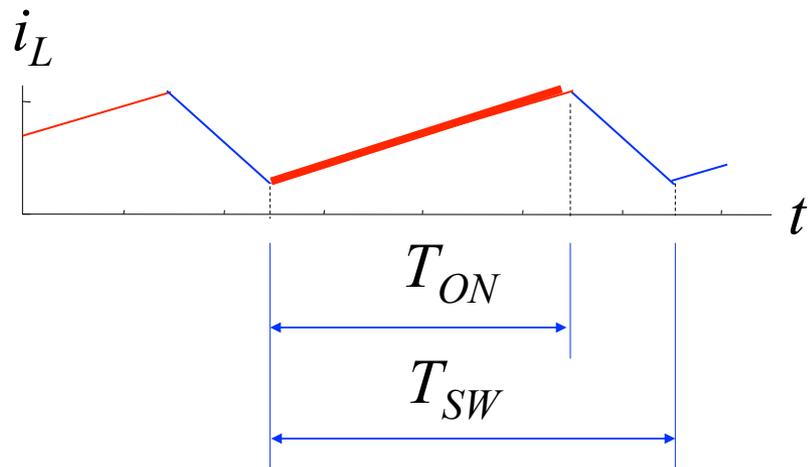

$$v_L = L \frac{di_L}{dt}$$

$$v_L = V_E$$


Current flowing through reactor L

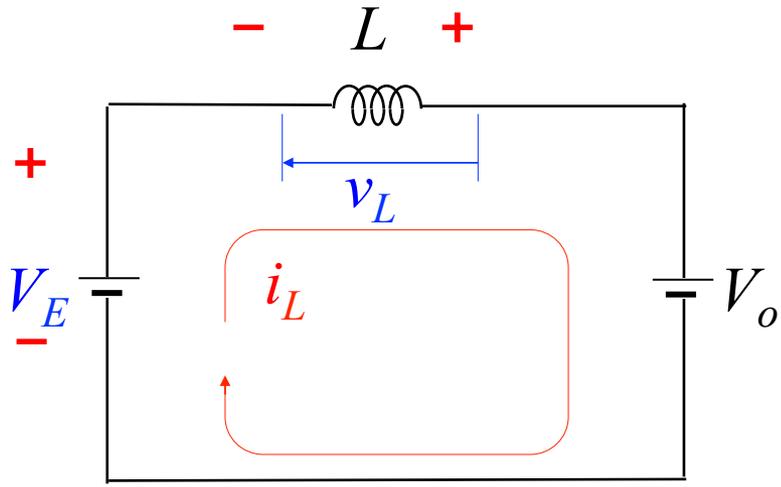


(b) Tr: OFF

$$v_L = L \frac{di_L}{dt}$$

$$v_L = V_E - V_o$$

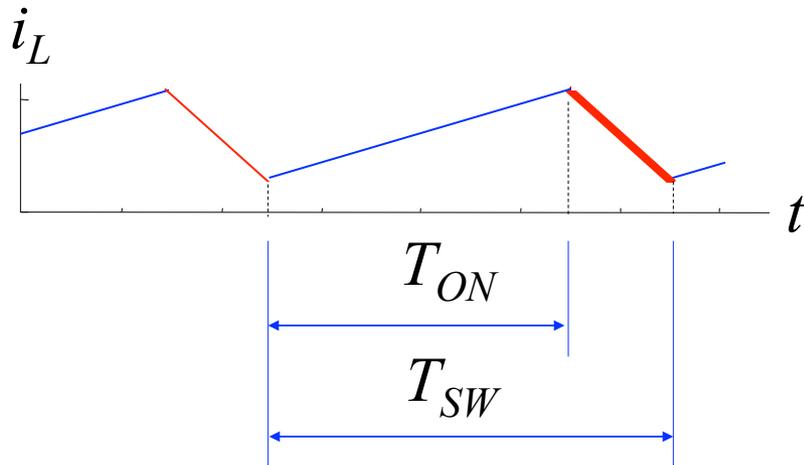


Current flowing through reactor L

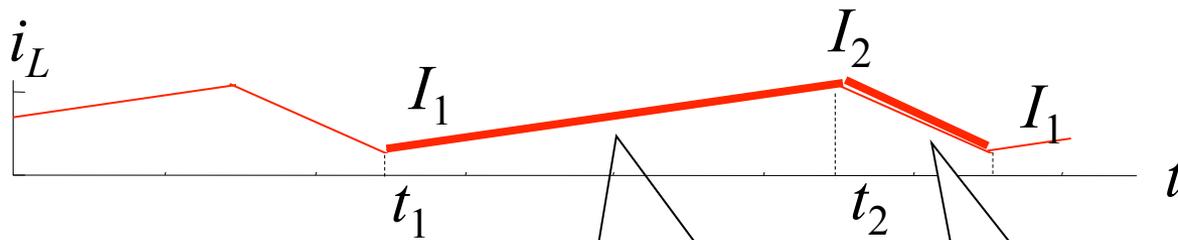

$$\Delta I_L = I_2 - I_1 = \frac{V_E}{L} \delta T_{SW}$$

$$\Delta I_L = I_2 - I_1 = -\frac{V_E - V_o}{L} T_{SW} (1 - \delta)$$

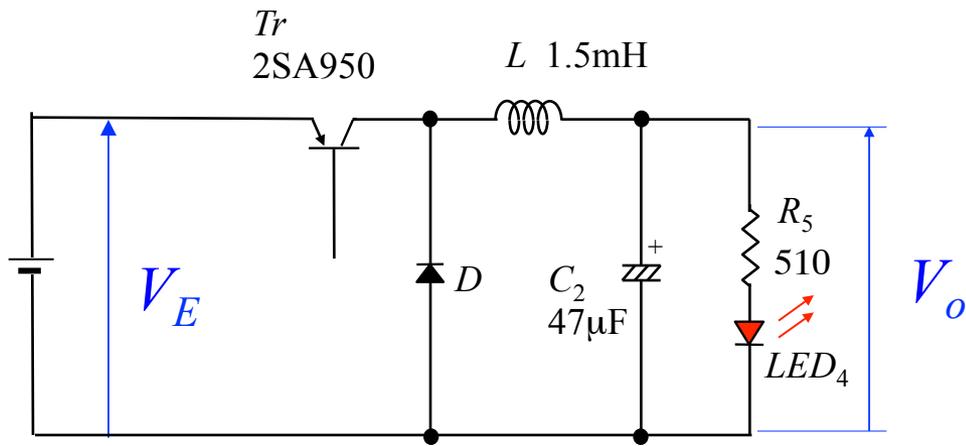
$$V_o = \frac{1}{1 - \delta} V_E \quad 0 \leq \delta < 1$$



$$V_o \leq V_E$$

Step-down chopper


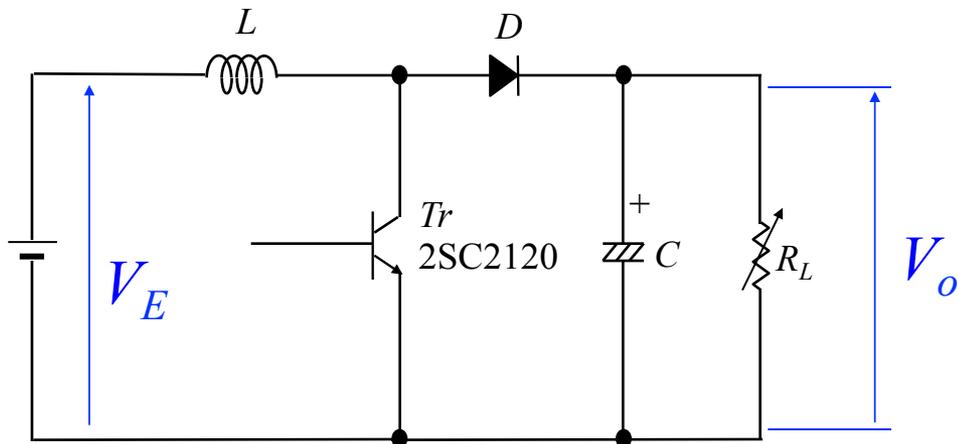
Which configuration's output voltage range covers both regions?






$$V_E \leq V_o$$

Step-up chopper

Step-up/down chopper

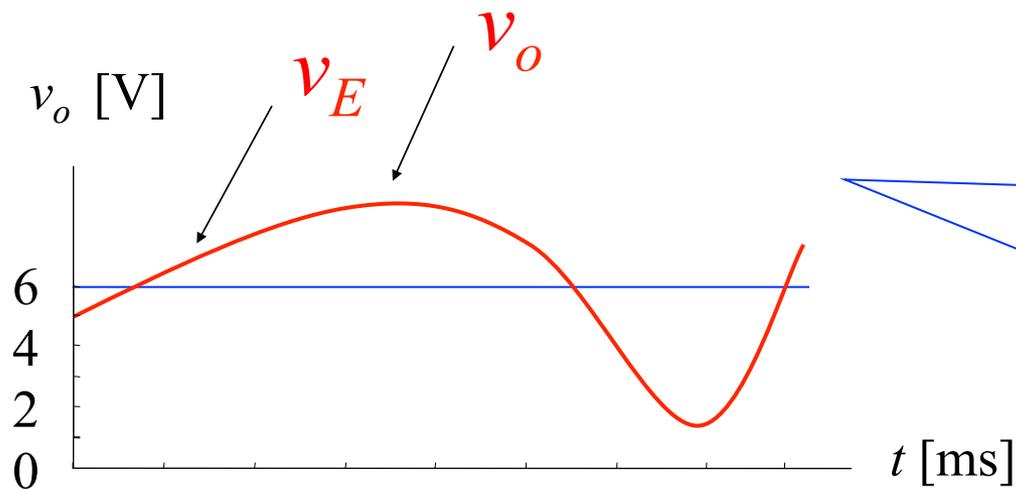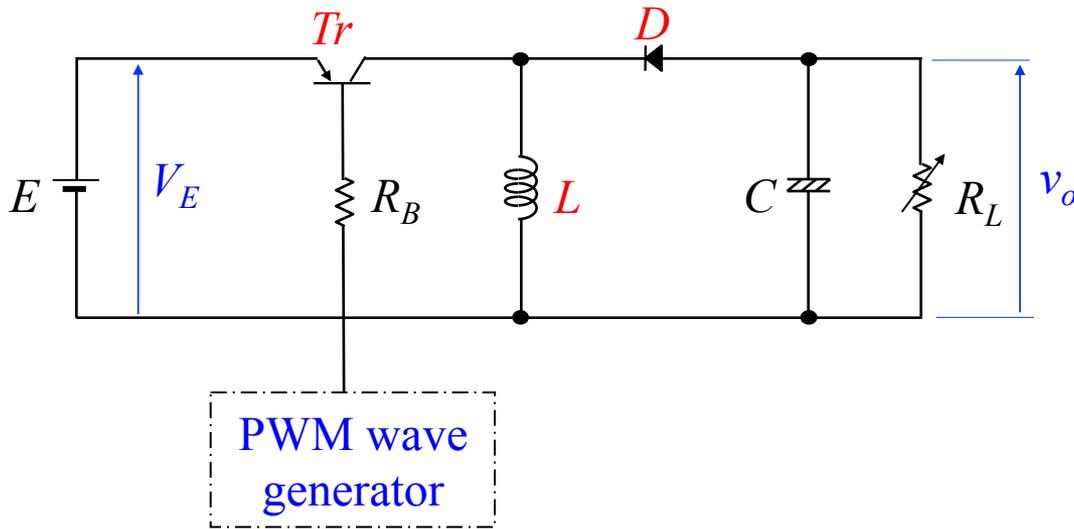

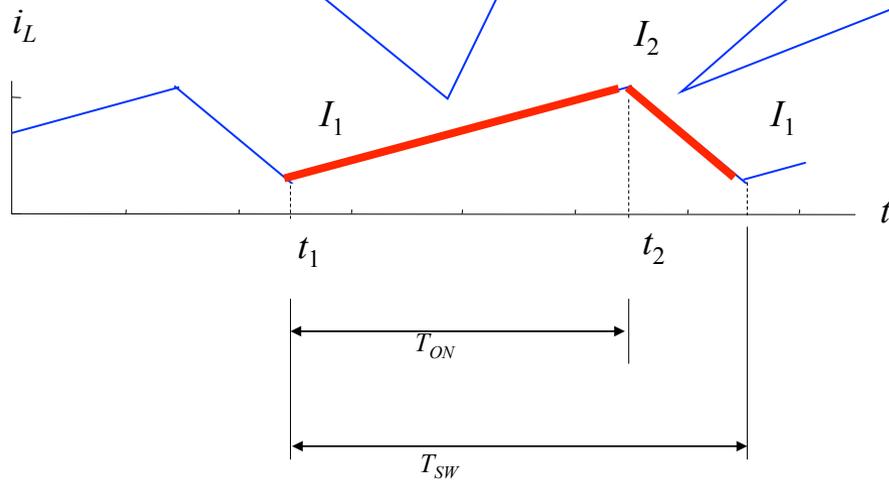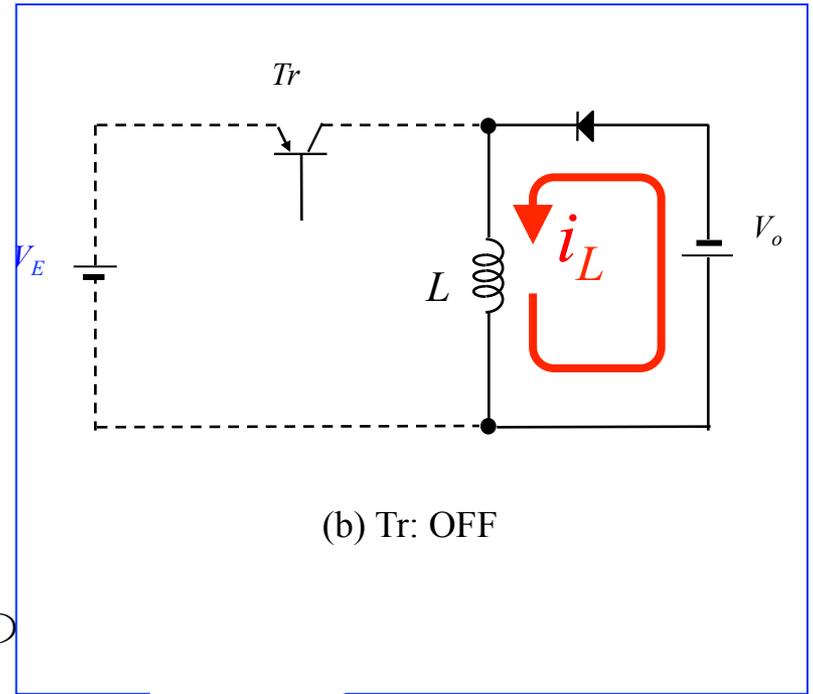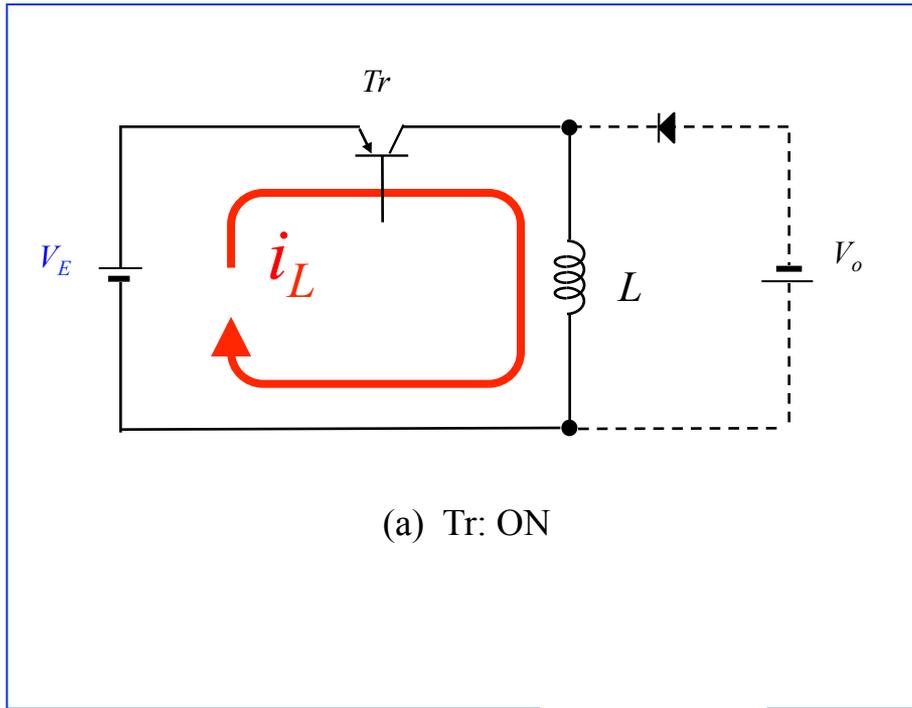The output voltage is smaller/larger than the source voltage.




$$V_o = \frac{\delta}{1 - \delta} V_E$$


$$0 \leq \delta < 1$$

Current flowing through reactor L

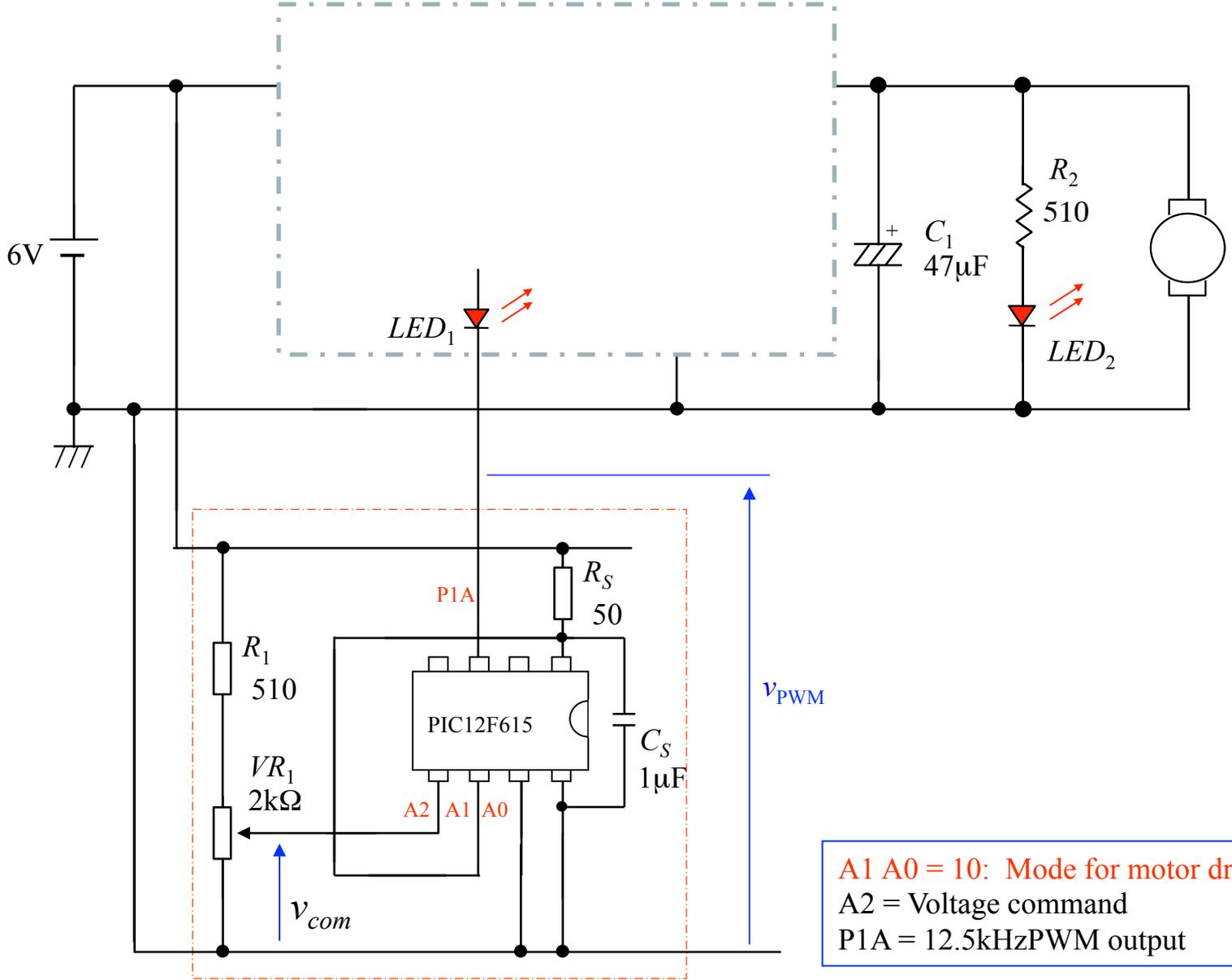STEP 5. Circuit construction practice Construct a step-down chopper with a smoothing circuit that includes a reactor, Schottky barrier diode, and electrolytic capacitor. After rotating the motor at a low speed for a few minutes, check the temperature of the transistor by touching it.



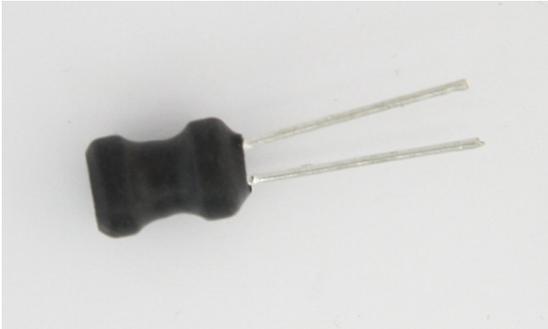A1 A0 = 10: Mode for motor drive
A2 = Voltage command
P1A = 12.5kHz PWM output




Reactor (1.5 mH)




Reactor symbol


The stripe indicates cathode.

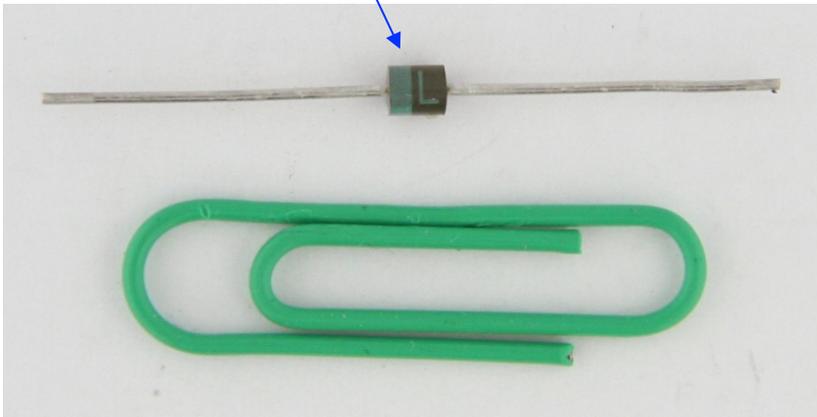


Schottky barrier diode (30V, 1A)

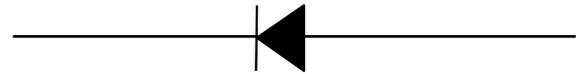

Diode symbol


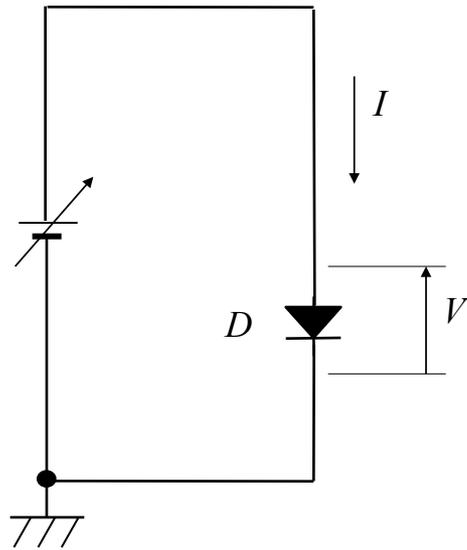


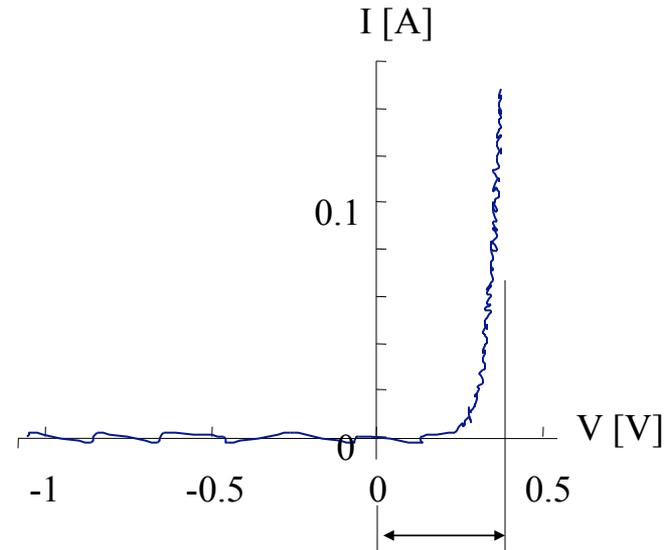(a) Definitions of voltage direction across diode V and current direction into diode I



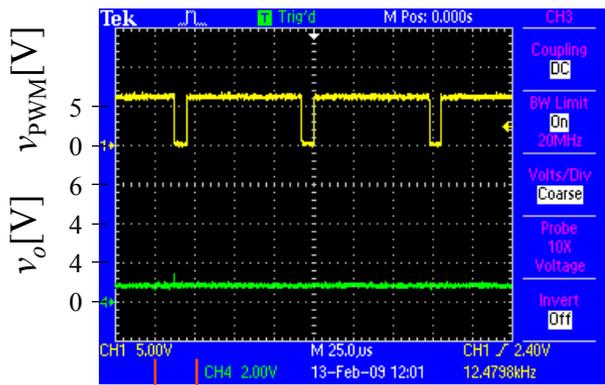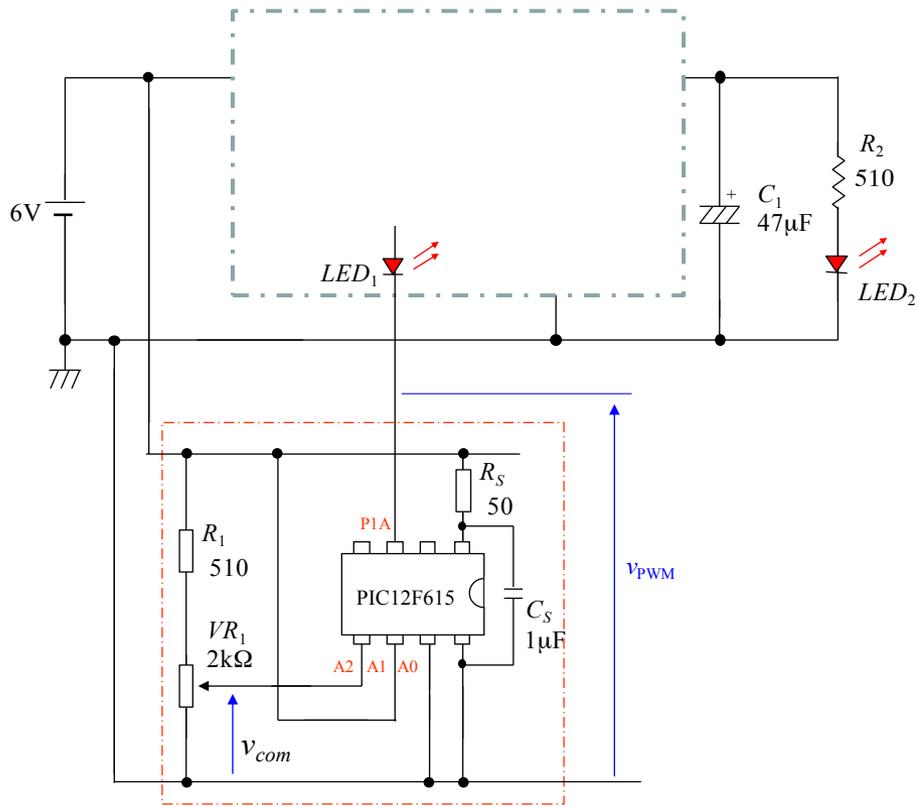
(b) Characteristic of the Schottky barrier diode

Characteristic of the Schottky barrier diode




25μsec

(a) $v_{ref} = 0.5$ [V]

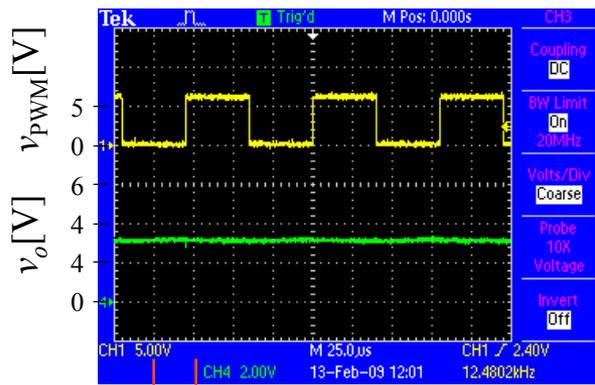

25μsec

(b) $v_{ref} = 3$ [V]

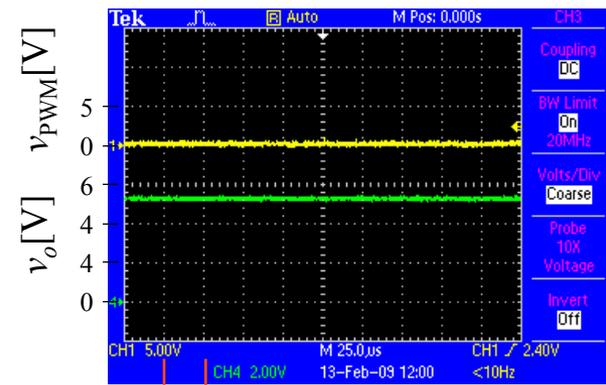

25μsec

(c) $v_{ref} = 6$ [V]


Step 5. problem 1

(a) Draw the energy flow in the case where Tr is ON in a step-up chopper.

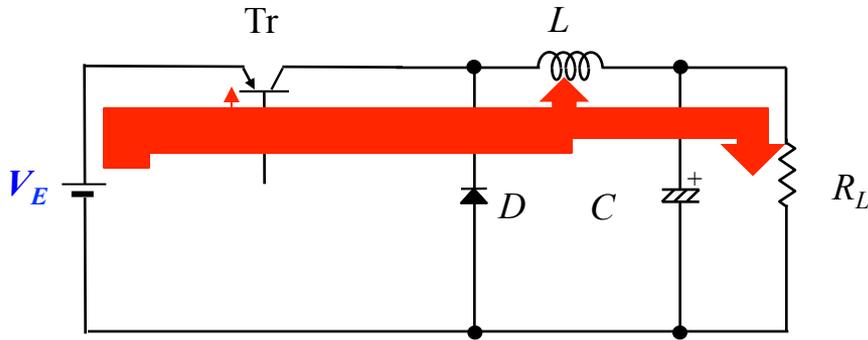
(b) Draw the energy flow in the case where Tr is OFF in a step-up chopper.

(hint) Energy flow in a step-down chopper.

Small amounts of energy are consumed in transistor Tr and diode D .



Tr: ON

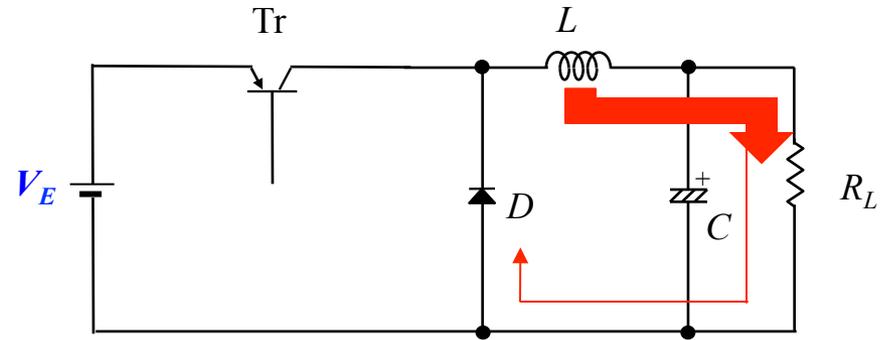

Tr: OFF