

Power Electronics

No. 14: Three-phase Inverter

Takeshi Furuhashi

Furuhashi_at_cse.nagoya-u.ac.jp

Three-phase AC

Three-phase AC is the most common method used for the generation, transmission, and distribution of electric power.

Heavy users of electric power, such as factories, use three-phase AC. Light users, such as individual houses, use single-phase AC.



Most industry equipment uses three-phase AC.


- Motor: Three-phase induction motor
 - Shinkansen, subway trains
 - Three-phase synchronous motor
 - Brushless motor
 - Hybrid vehicles, Electric cars

The small motors used in home appliances (such as refrigerators, washing machines, and electric fans) are single phase induction type motors.


Eco-generation systems (such as wind power generation, solar power generation, and fuel cell generation) also use three-phase AC to connect to the power grid.

Three-phase inverter

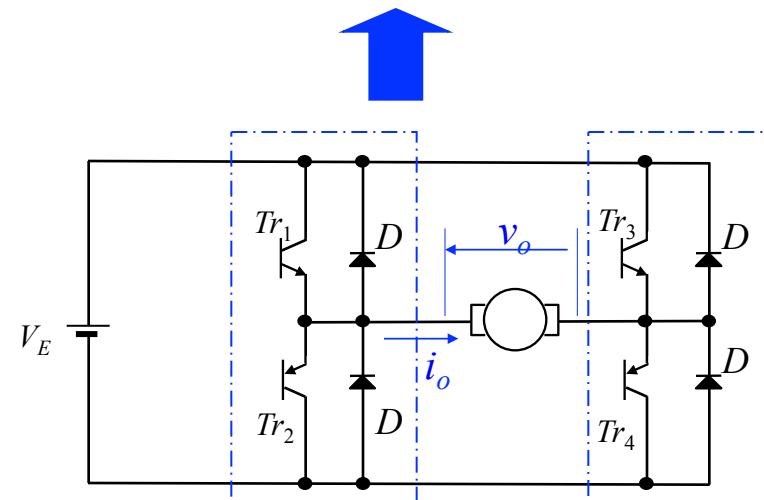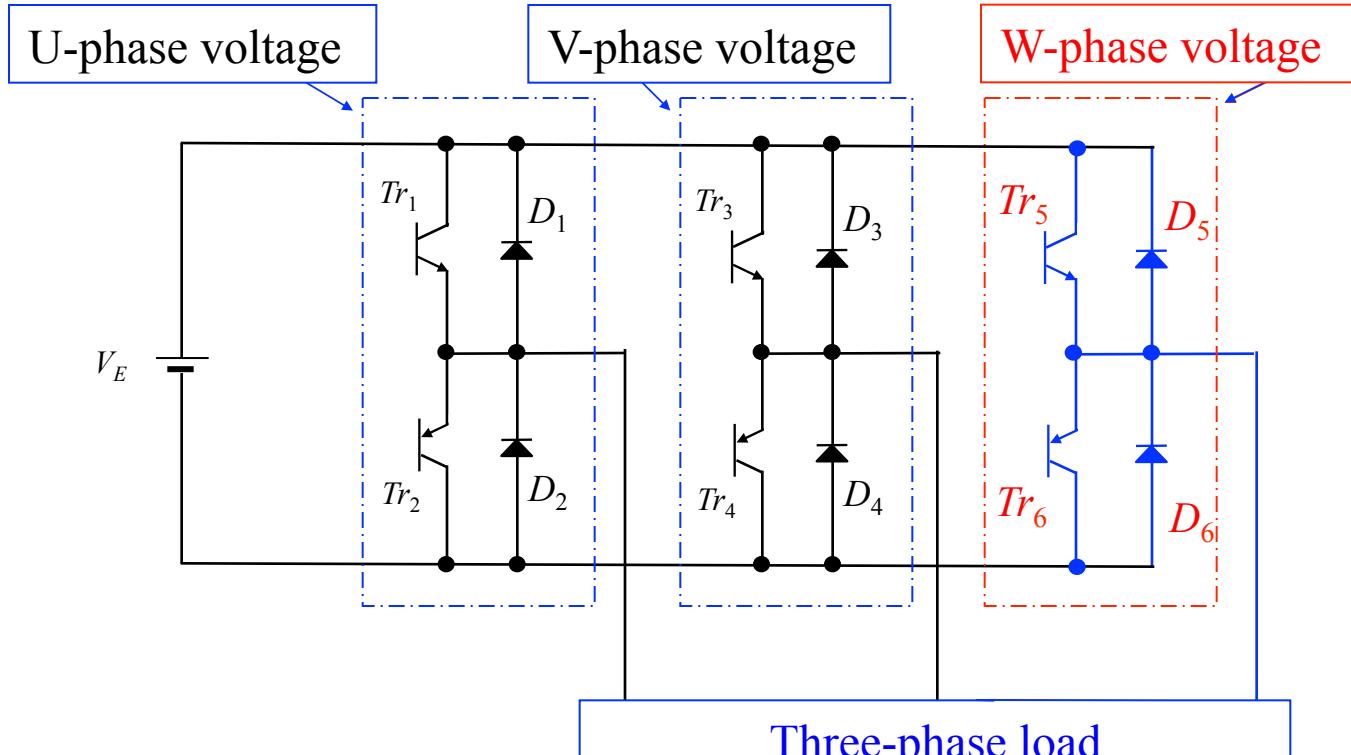

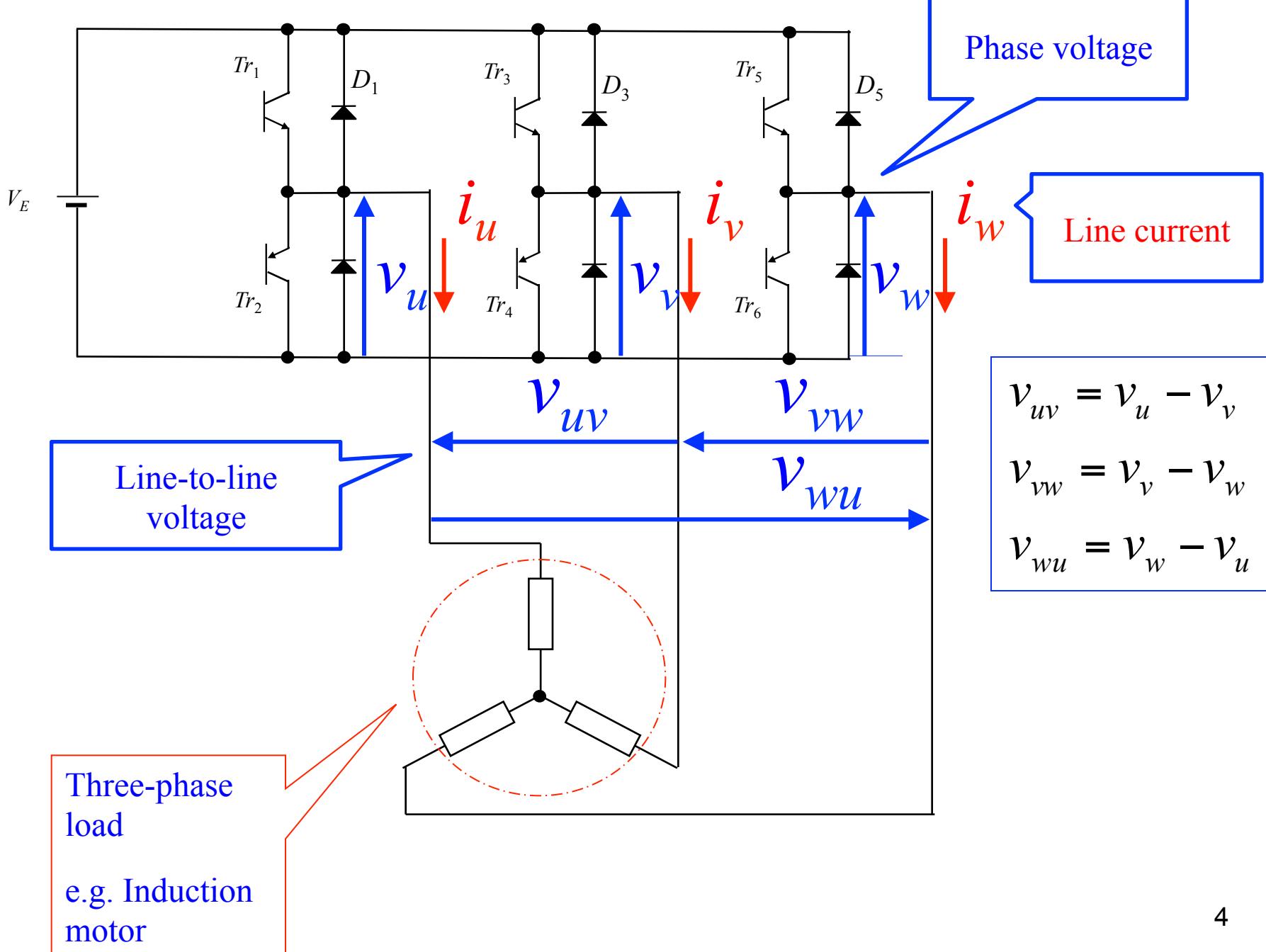

120 degree conduction mode inverter

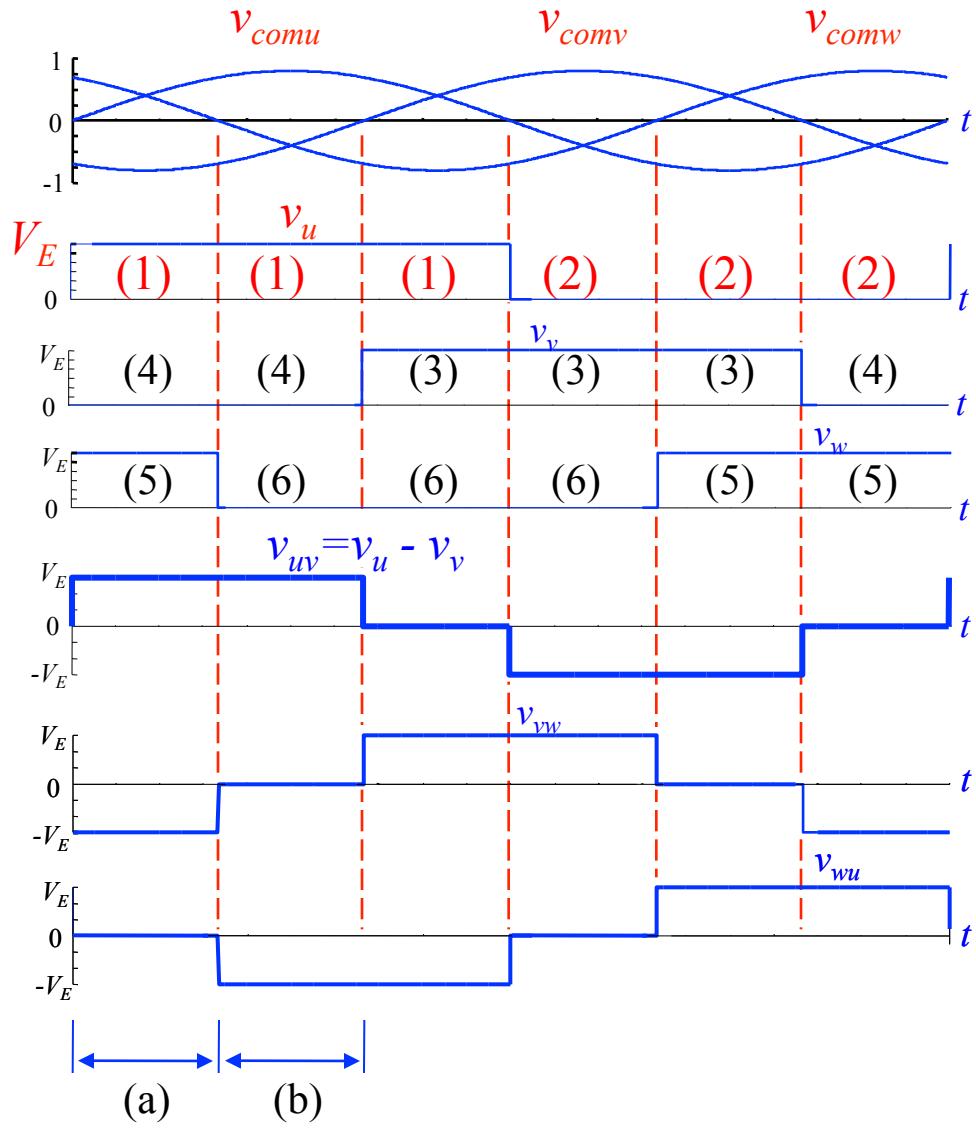

If $v_{comu} > 0$
Tr1 ON, Tr2 OFF

If $v_{comu} < 0$
Tr1 OFF, Tr2 ON


If $v_{comv} > 0$
Tr3 ON, Tr4 OFF

If $v_{comv} < 0$
Tr3 OFF, Tr4 ON

If $v_{comw} > 0$
Tr5 ON, Tr6 OFF

If $v_{comw} < 0$
Tr5 OFF, Tr6 ON

Fourier transform of phase voltage

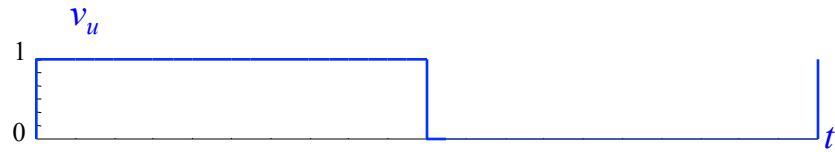

$$v_u = a_0 + \sum_{n=1} a_n \cos n\theta + \sum_{n=1} b_n \sin n\theta$$

$$a_1 = \frac{1}{\pi} \int_0^{2\pi} v_u \cos \theta d\theta$$

$$b_1 = \frac{1}{\pi} \int_0^{2\pi} v_u \sin \theta d\theta$$

$$= \frac{1}{\pi} \int_0^{\pi} V_E \cos \theta d\theta$$

$$= \frac{1}{\pi} \int_0^{\pi} V_E \sin \theta d\theta$$

$$= \frac{V_E}{\pi} [\sin \theta]_0^\pi$$

$$= 0$$


$$= \frac{V_E}{\pi} [-\cos \theta]_0^\pi$$

$$= \frac{2V_E}{\pi}$$

Fundamental component
of phase voltage

$$v_{u1} = \frac{2V_E}{\pi} \sin \omega t$$

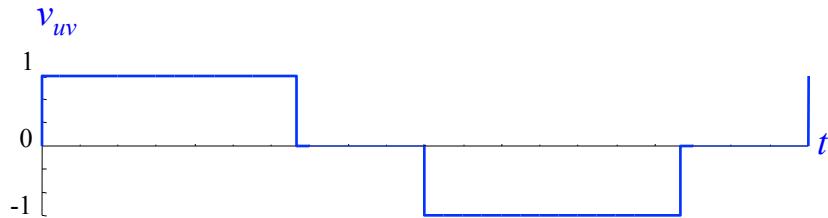Fourier transform of line-to-line voltage



$$v_{uv} = a_0 + \sum_{n=1} a_n \cos n\theta + \sum_{n=1} b_n \sin n\theta$$

$$a_1 = \frac{1}{\pi} \int_0^{2\pi} v_{uv} \cos \theta d\theta$$

$$b_1 = \frac{1}{\pi} \int_0^{2\pi} v_{uv} \sin \theta d\theta$$

$$= \frac{1}{\pi} \left\{ \int_0^{\frac{2\pi}{3}} V_E \cos \theta d\theta + \int_{\pi}^{\frac{5\pi}{3}} (-V_E) \cos \theta d\theta \right\}$$

$$= \frac{V_E}{\pi} \left\{ [\sin \theta]_0^{\frac{2\pi}{3}} + [-\sin \theta]_{\pi}^{\frac{5\pi}{3}} \right\}$$

$$= \frac{\sqrt{3}V_E}{\pi}$$

$$= \frac{1}{\pi} \left\{ \int_0^{\frac{2\pi}{3}} V_E \sin \theta d\theta + \int_{\pi}^{\frac{5\pi}{3}} (-V_E) \sin \theta d\theta \right\}$$

$$= \frac{V_E}{\pi} \left\{ [-\cos \theta]_0^{\frac{2\pi}{3}} + [\cos \theta]_{\pi}^{\frac{5\pi}{3}} \right\}$$

$$= \frac{3V_E}{\pi}$$

Fundamental component
of line - to - line voltage

$$\begin{aligned} v_{uv1} &= \frac{V_E}{\pi} (3 \sin \omega t + \sqrt{3} \cos \omega t) \\ &= \frac{2\sqrt{3}V_E}{\pi} \left(\frac{\sqrt{3}}{2} \sin \omega t + \frac{1}{2} \cos \omega t \right) \\ &= \frac{2\sqrt{3}V_E}{\pi} \left(\cos \frac{\pi}{6} \sin \omega t + \sin \frac{\pi}{6} \cos \omega t \right) \\ &= \frac{2\sqrt{3}V_E}{\pi} \sin \left(\omega t + \frac{\pi}{6} \right) \end{aligned}$$

The amplitude and phase of line-to-line voltage is $\sqrt{3}$ times larger than and $\pi/6$ leading to those of the phase voltage.

STEP 10. Circuit construction practice

Design and construct a D-class amplifier using a full-bridge inverter.

