


# Power Electronics

## No. 10: PI-controller for DC motor speed control


Takeshi Furuhashi

Furuhashi\_at\_cse.nagoya-u.ac.jp

# P-controller

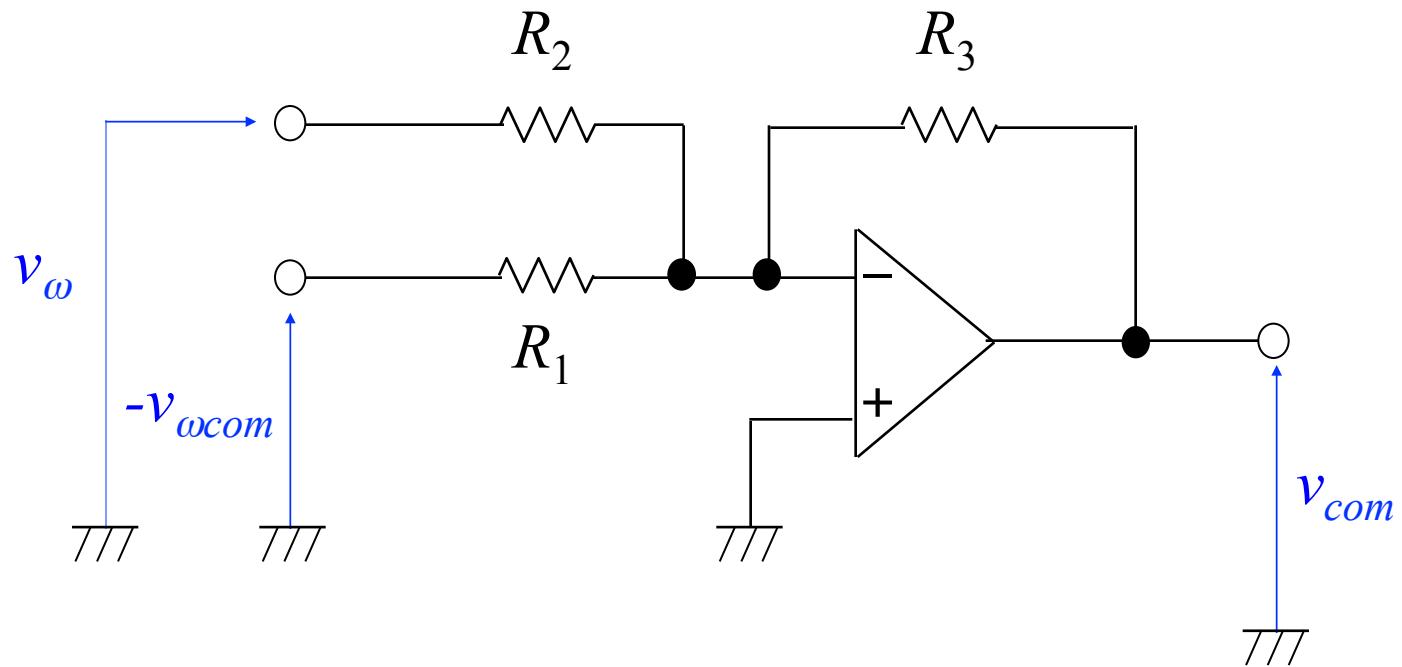

P-controller using op-amp

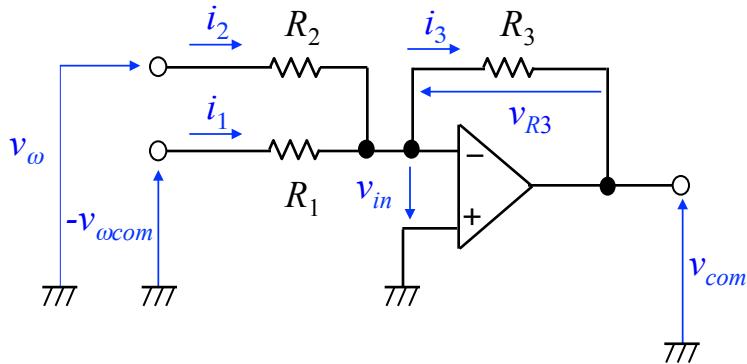

P-controller using op-amp

$$v_{in} = 0, \text{ then } i_1 = \frac{-v_{\omega com}}{R_1}, \quad i_2 = \frac{v_\omega}{R_2}$$

$$R_{in} = \infty, \text{ then } i_3 = i_1 + i_2$$

$$v_{R3} = R_3 i_3 \quad \text{and} \quad v_{com} = -v_{in} - v_{R3}$$

$$v_{com} = \frac{R_3}{R_1} v_{\omega com} - \frac{R_3}{R_2} v_\omega$$


Let,  $R_1 = R_2$ , then

$$v_{com} = \frac{R_3}{R_1} (v_{\omega com} - v_\omega) = \underline{K_P} (v_{\omega com} - v_\omega)$$


Proportional gain

# PI-controller

Capacitor  $C_1$   
is inserted.

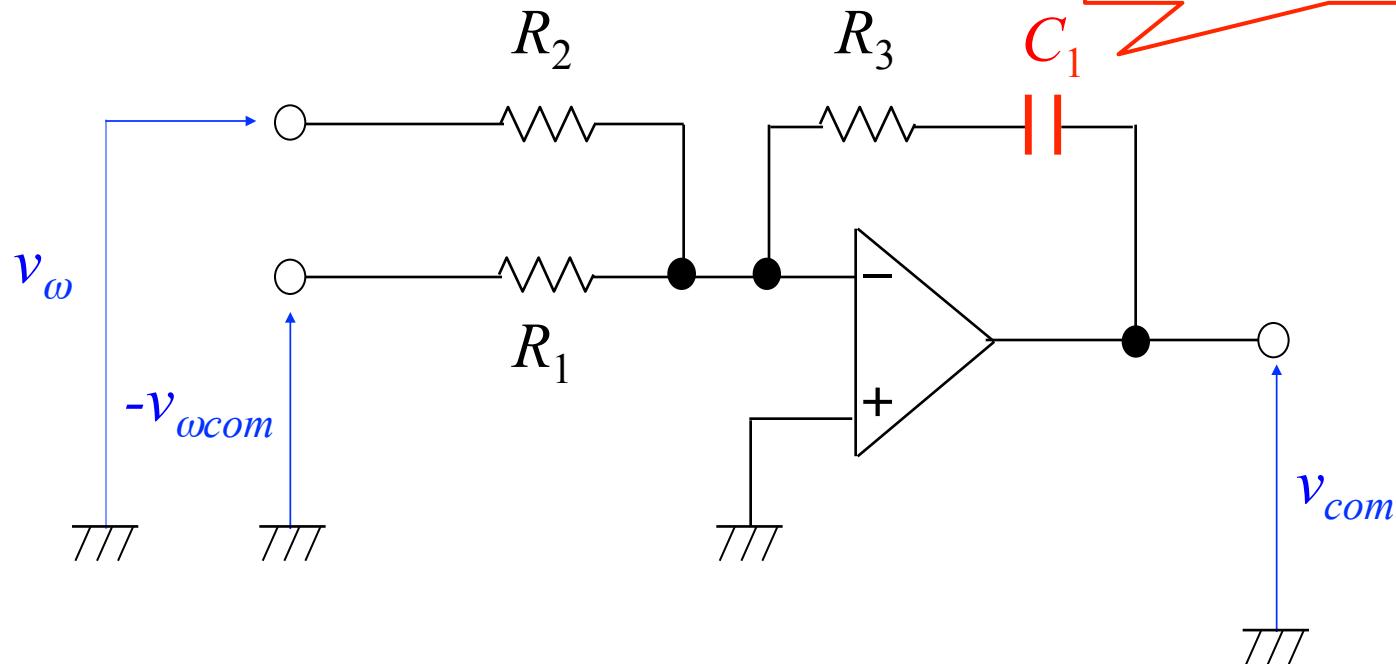

PI-controller using op-amp

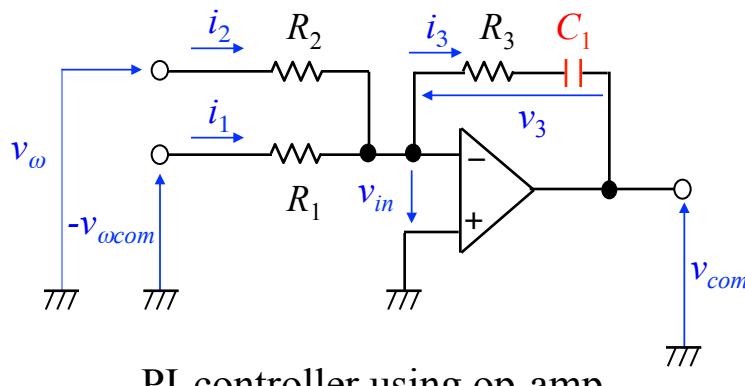

PI-controller using op-amp

$$v_{in} = 0, \text{ then } i_1 = \frac{-v_{\omega com}}{R_1}, \quad i_2 = \frac{v_\omega}{R_2}$$

$$R_{in} = \infty, \text{ then } i_3 = i_1 + i_2$$



$$v_3 = R_3 i_3 + \frac{1}{C_1} \int i_3 dt$$

$$v_{com} = -v_{in} - v_3$$



Assuming that  $R_1 = R_2$ ,

$$\begin{aligned} v_{com} &= \frac{R_3}{R_1} (v_{\omega com} - v_\omega) + \frac{1}{R_1 C_1} \int (v_{\omega com} - v_\omega) dt \\ &= \underline{K_P} (v_{\omega com} - v_\omega) + \underline{K_I} \int (v_{\omega com} - v_\omega) dt \end{aligned}$$

Proportional gain    Integral gain

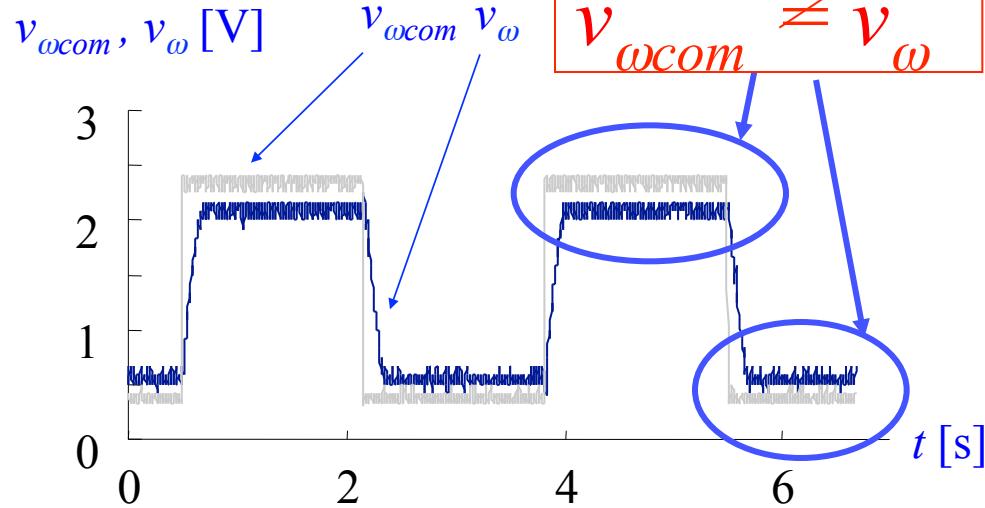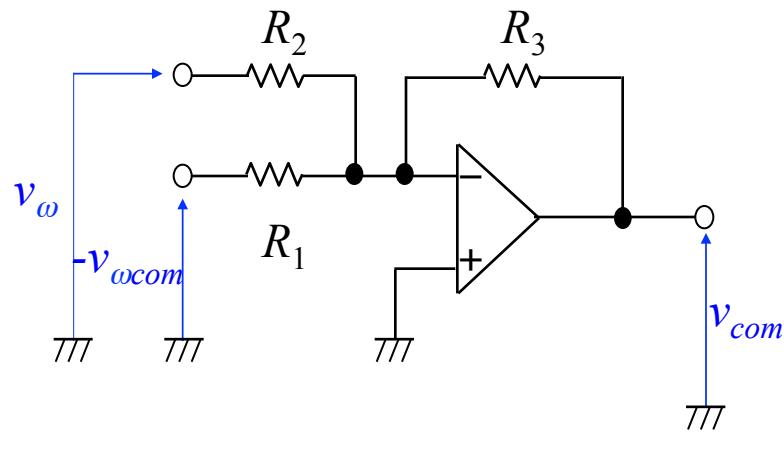

P-controller

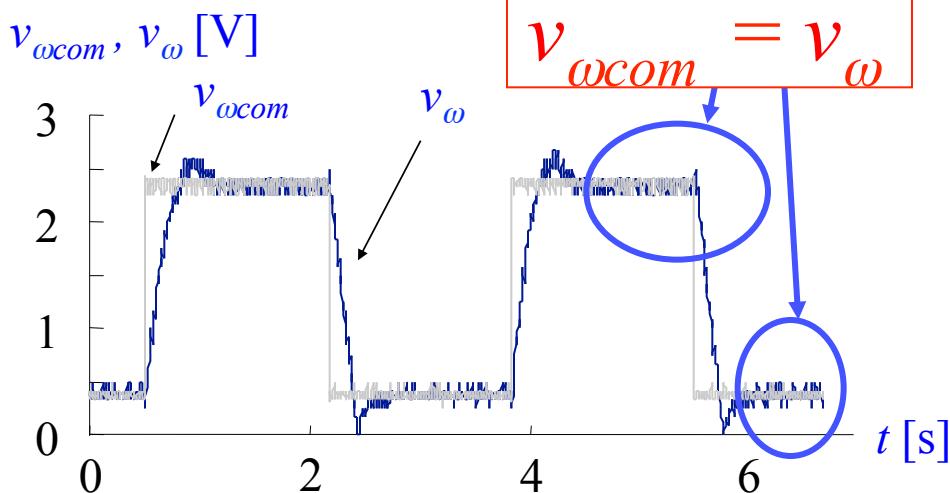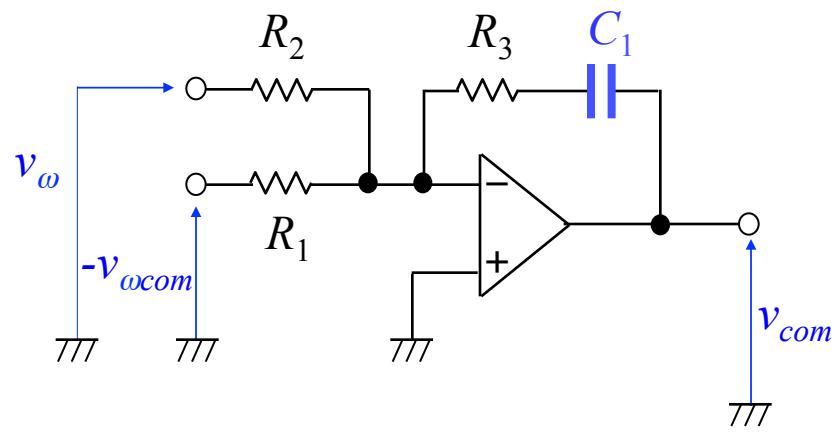

PI-controller

## Step 8. Problem

P-controller cannot make  $v_{\omega com}$  and  $v_\omega$  coincide with each other.  
Conversely, PI-controller can make them coincide.

Explain the reason.