


Power Electronics

No.3 Smoothing Circuit

Takeshi Furuhashi


Furuhashi_at_cse.nagoya-u.ac.jp

Smoothing circuit

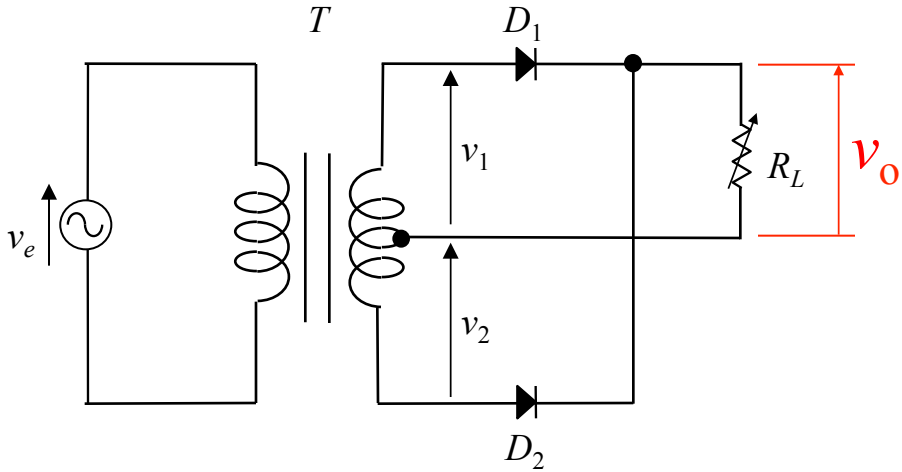


Full-wave rectifier

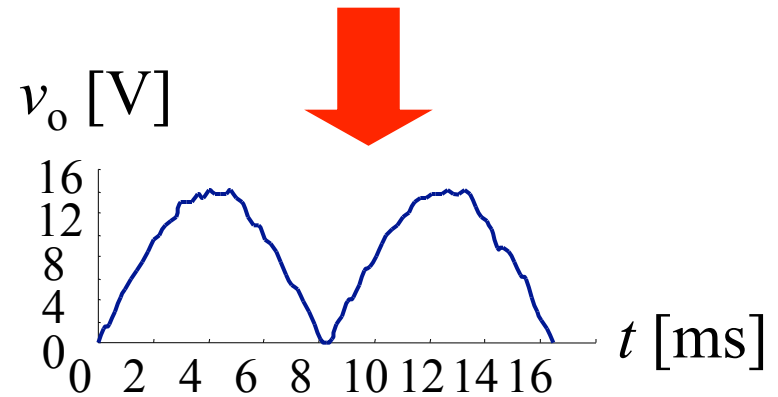This voltage cannot be applied to electronic circuits



Wave form of output voltage v_o

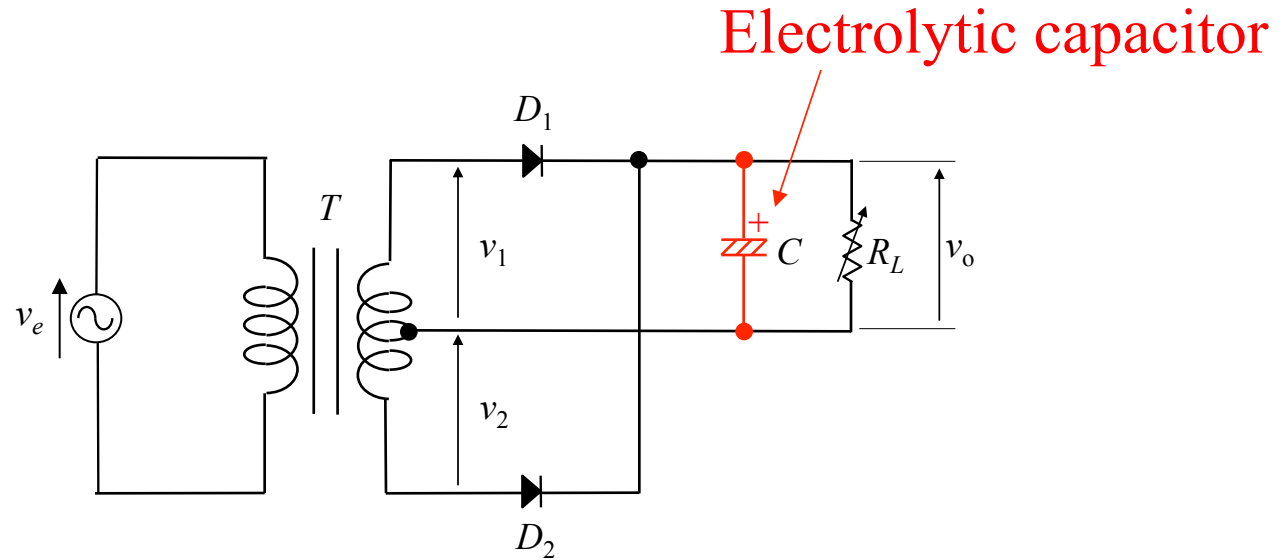


Full-wave rectifier with smoothing circuit using a capacitor

Transformer T

Diode D_1

Electrolytic capacitor C

Variable resistor R_L

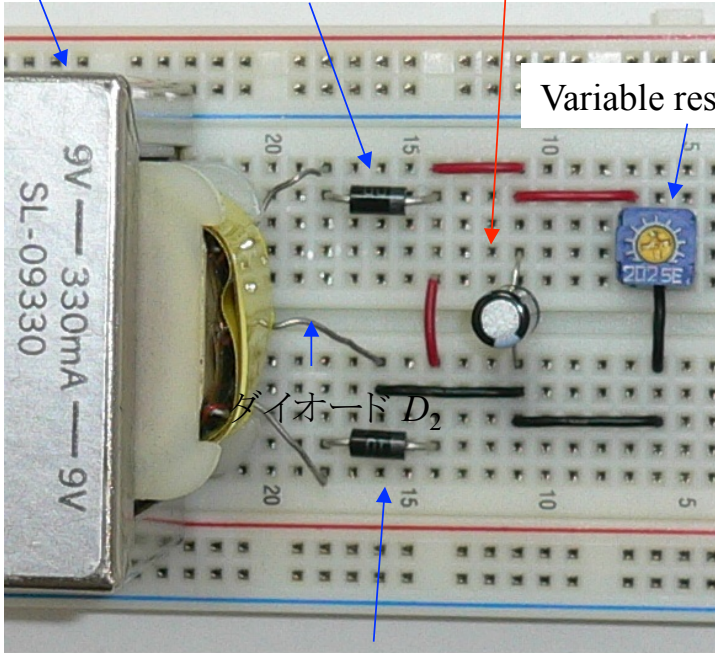

ダイオード D_2

Diode D_2


Example of a smoothing circuit

Electrolytic capacitor C

Transformer T


Diode D_1

Variable resistor R_L



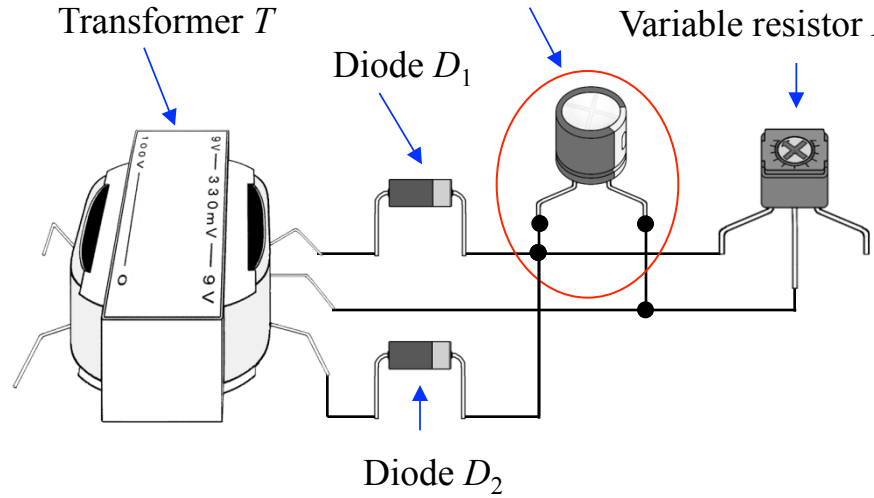


Diode D_2


Wiring diagram of a smoothing circuit

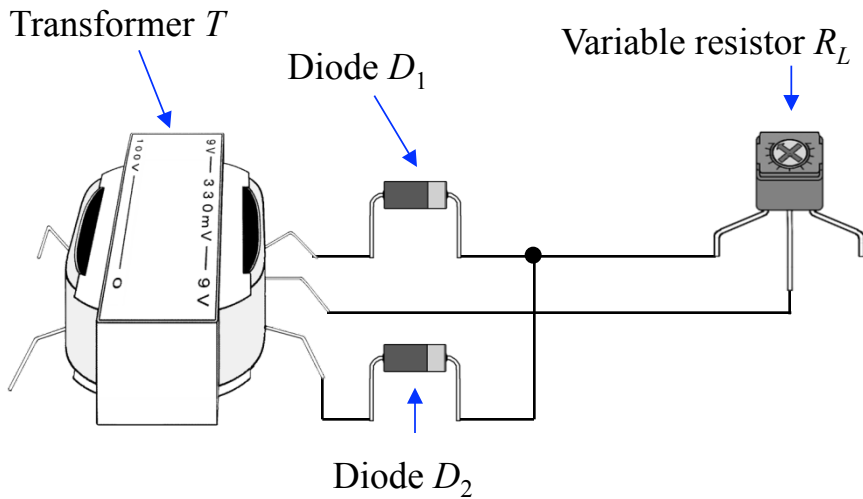


Electrolytic capacitor C

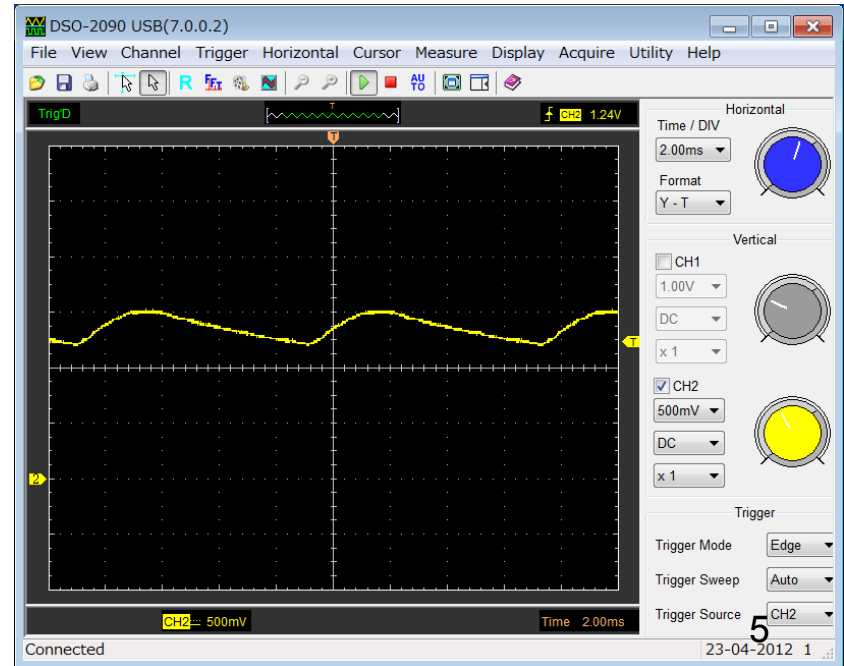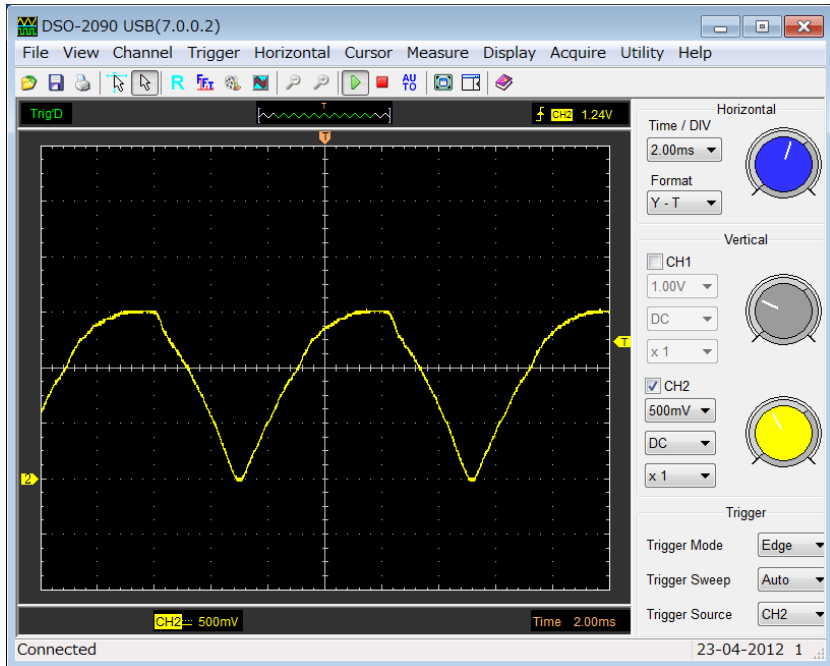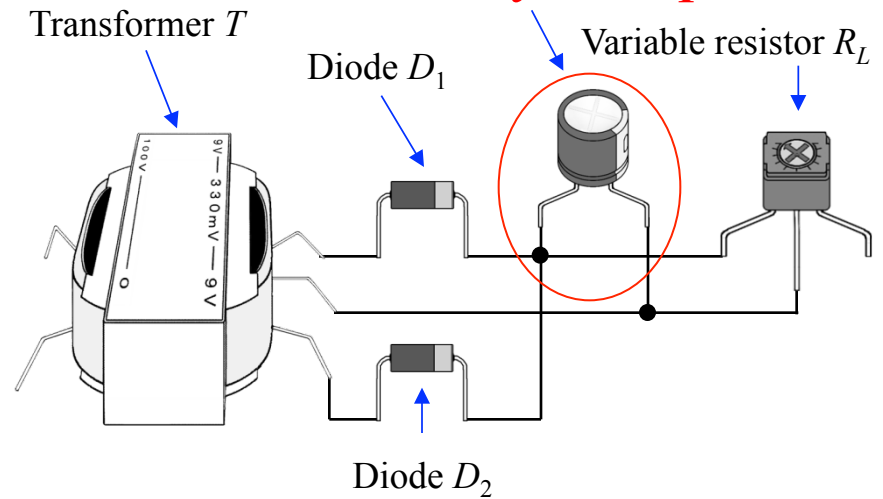

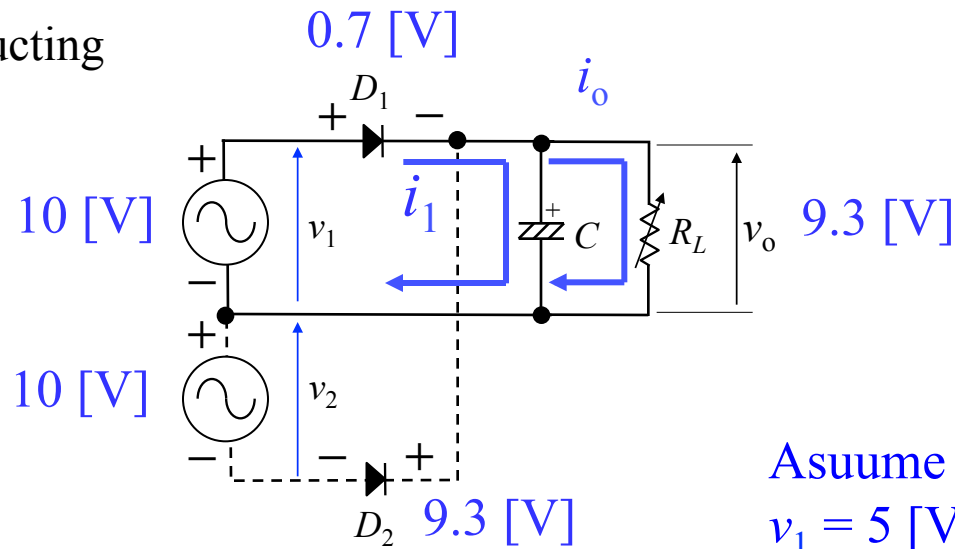
(a) Diode D_1 is conducting
 $(v_1 > v_o, v_1 > -v_2)$



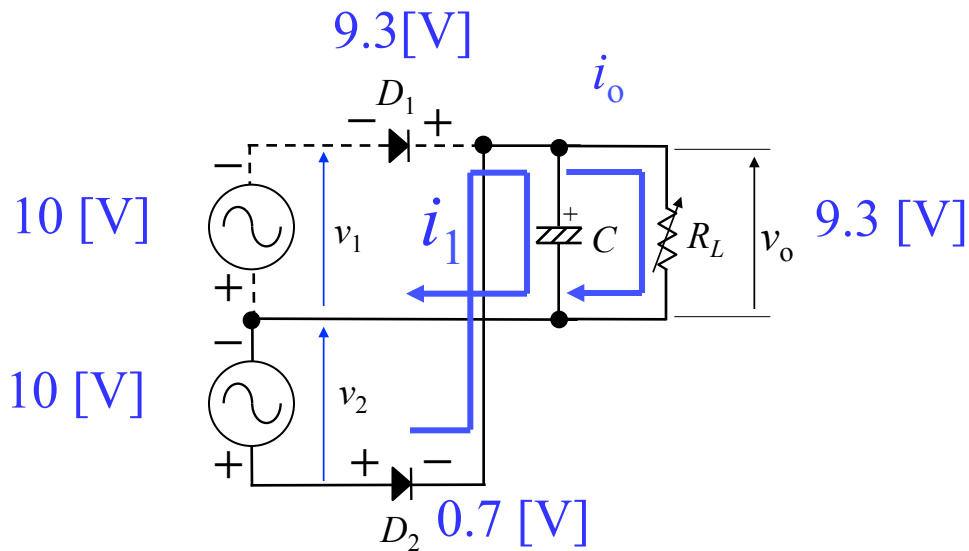
Assume that
 $v_1 = 5$ [V], $v_2 = 5$ [V]
 $v_o = 9$ [V]



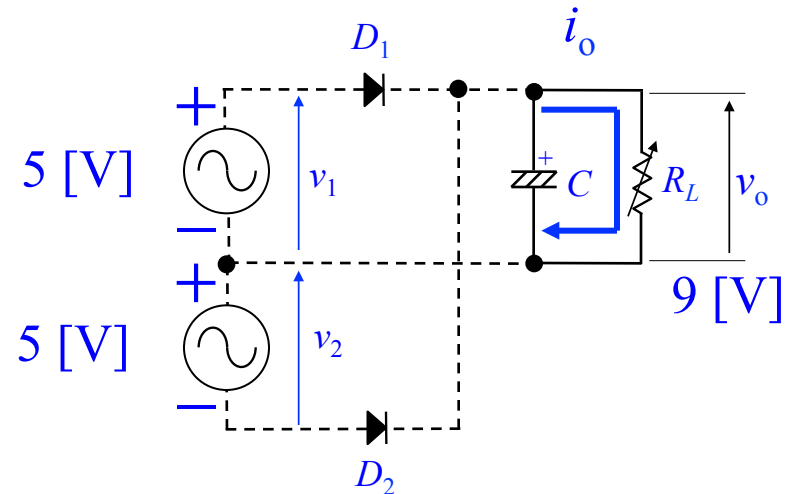(b) Diode D_2 is conducting
 $(-v_2 > v_o, -v_2 > v_1)$



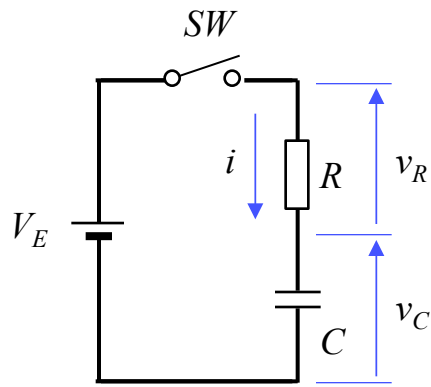(c) Diodes are not conducting
 $(v_1 < v_o, -v_2 < v_o)$



At $t = 0$, SW is turned on and the initial voltage of C : $v_C = V_{C0}$

$$V_E = Ri + \frac{1}{C} \int_0^t i dt + V_{C0}$$

$$i = \frac{dq}{dt}, \quad q = \int_0^t i dt + CV_{C0}$$

Then

$$V_E = R \frac{dq}{dt} + \frac{q}{C} \quad (1)$$

Assuming that the charge q is in the form given by

$$q = Ae^{-\frac{t}{RC}} + B \quad (2)$$

where A and B are constants. By substituting (2) into (1),

$$V_E = -\frac{A}{C} e^{-\frac{t}{RC}} + \frac{1}{C} (Ae^{-\frac{t}{RC}} + B) \quad (3)$$

The initial condition is that at $t = 0$, $q = CV_{C0}$. Then, from (2)

$$CV_{C0} = A + B, \quad (4)$$

and from (3),

$$B = CV_E. \quad (5)$$


By substituting (5) into (4),


$$A = C(V_{C0} - V_E).$$

Thus,

$$q = CV_E(1 - e^{-\frac{t}{RC}}) + CV_{C0}e^{-\frac{t}{RC}}$$
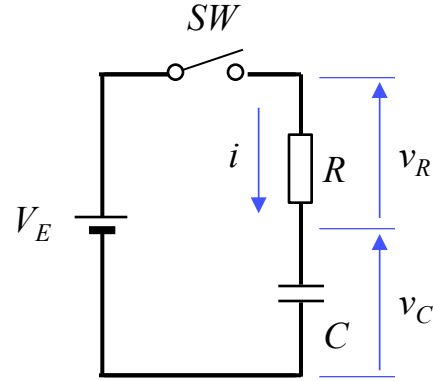
$$i = \frac{dq}{dt} = \frac{V_E - V_{C0}}{R} e^{-\frac{t}{RC}}$$



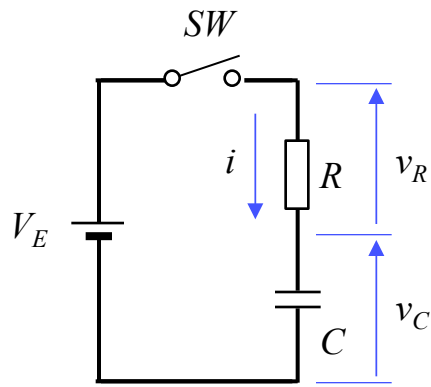

At $t = 0$, SW is turned on and the initial voltage of C : $v_C = V_{C0}$

$$V_E = Ri + \frac{1}{C} \int_0^t i dt + V_{C0}$$

By applying the Laplace transform to this eq.,


$$\frac{V_E}{s} = RI(s) + \frac{I(s)}{sC} + \frac{V_{C0}}{s}$$

$$\left(R + \frac{1}{sC} \right) I(s) = \frac{V_E - V_{C0}}{s}$$

$$I(s) = \frac{V_E - V_{C0}}{R} \frac{1}{s + \frac{1}{RC}}$$

By applying the Inverse Laplace transform to the above eq.,
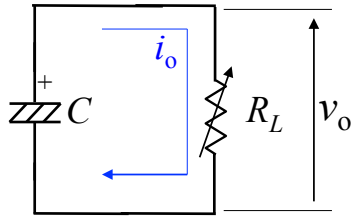
$$i(t) = \frac{V_E - V_{C0}}{R} e^{-\frac{1}{RC}t}$$



(b) Diode is not conducting

Equivalent circuit of the rectifier


$$V_E = Ri + \frac{1}{C} \int_0^t i dt + V_{C0}$$

At $t = 0$,

$$i = i_o$$

$$V_E = 0, V_{C0} = -v_o(0)$$
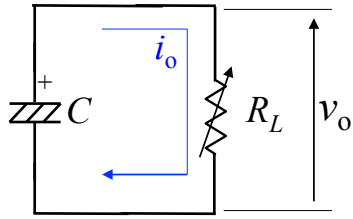
$$R_L i_o + \frac{1}{C} \int_0^t i_o dt = v_o(0)$$



$$R_L i_o + \frac{1}{C} \int_0^t i_o dt = v_o(0)$$


(b) Diode is not conducting

$$R_L I_o + \frac{1}{sC} I_o = \frac{V_p}{s}$$


Equivalent circuit of the rectifier

$$I_o = \frac{1}{s + \frac{1}{R_L C}} \frac{V_p}{s}$$
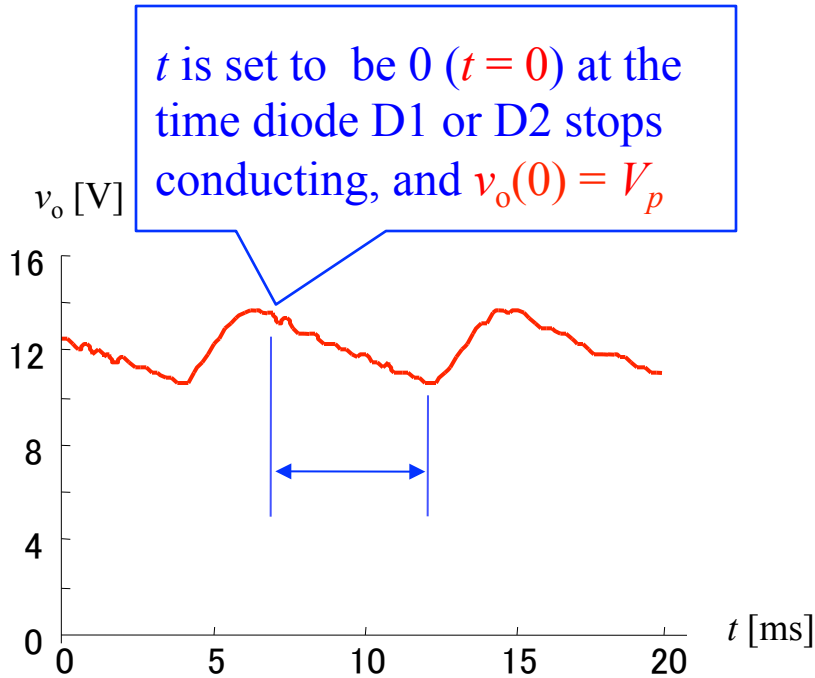
$$i_o = \frac{V_p}{R_L} e^{-\frac{t}{R_L C}}$$



Voltage waveform of v_o

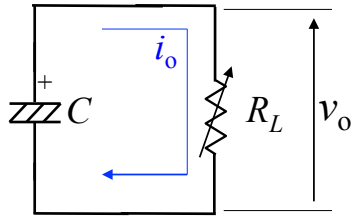


(b) Diode is not conducting

Equivalent circuit of the rectifier


$$v_o = R_L i_o = V_p e^{-\frac{t}{R_L C}}$$

t is set to be 0 ($t = 0$) at the time diode D1 or D2 stops conducting, and $v_o(0) = V_p$

$R_L C$: time constant [sec]

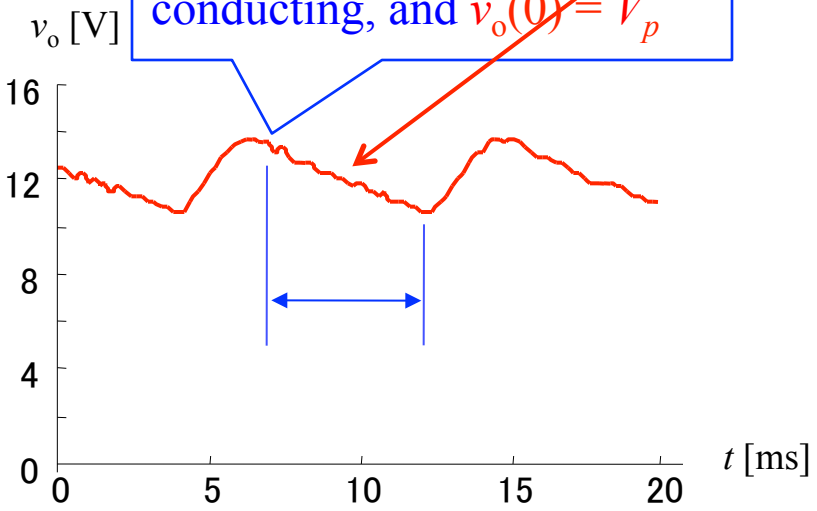

Voltage waveform of v_o

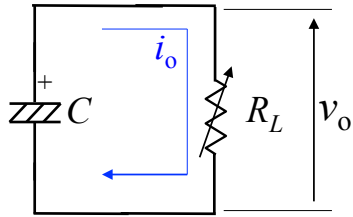


$$v_o = V_p e^{-\frac{t}{R_L C}}$$

(b) Diode is not conducting

$R_L = 100[\Omega], C = 1 [\mu\text{F}]$ のとき


Equivalent circuit of the rectifier

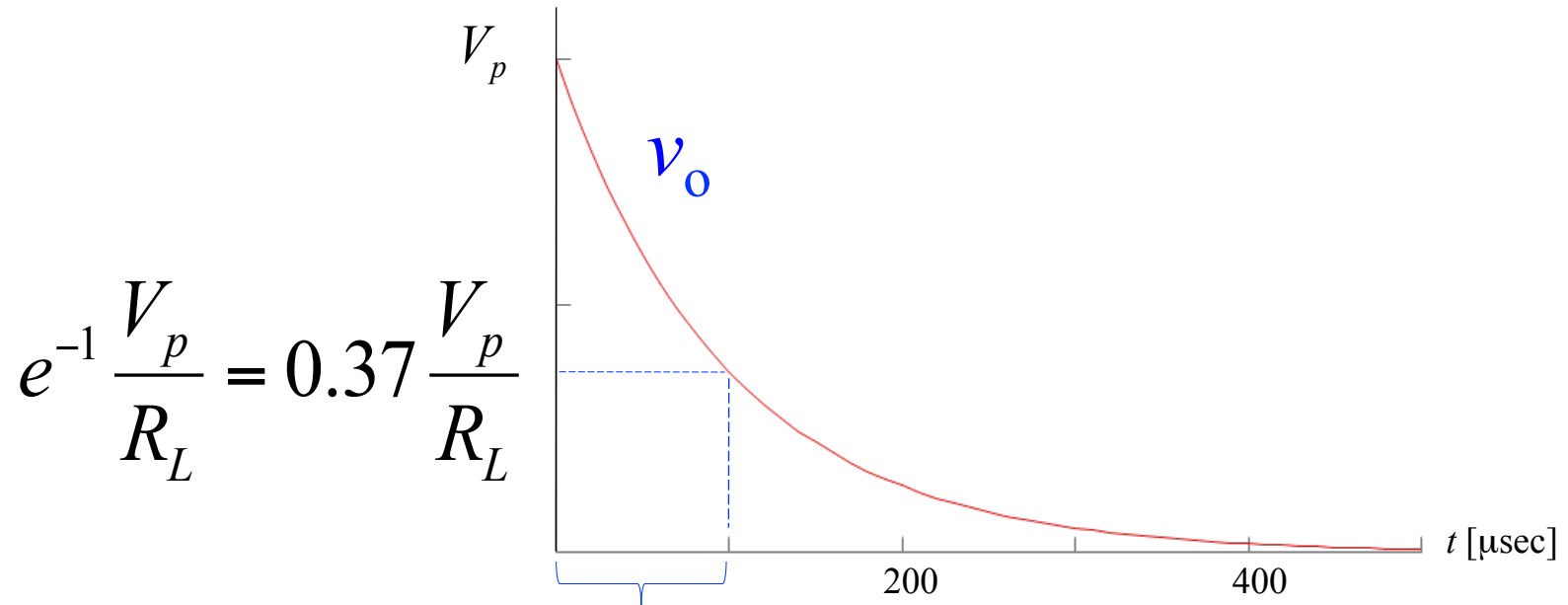


$$e^{-1} \frac{V_p}{R_L} = 0.37 \frac{V_p}{R_L}$$

$$\tau = R_L C = 100 \times 10^{-6} = 100 [\mu\text{sec}]$$

Time constant

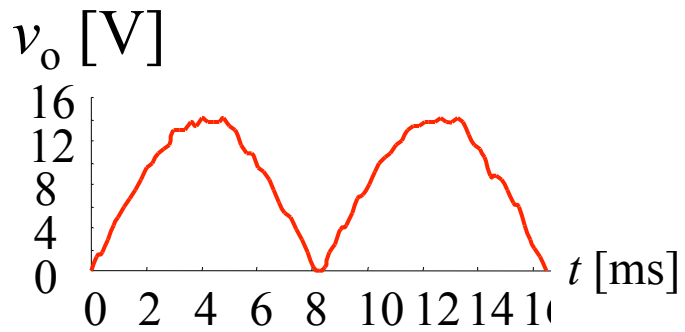

Not smoothed

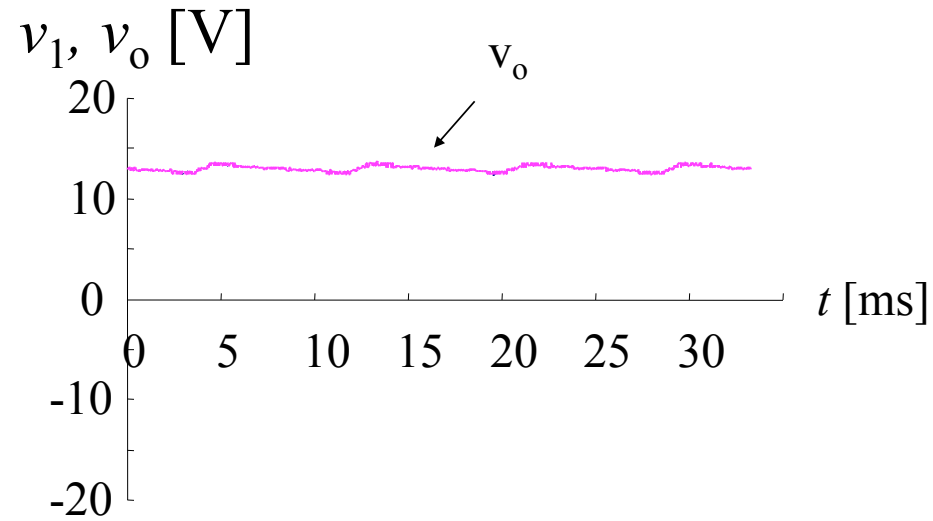


Smoothed

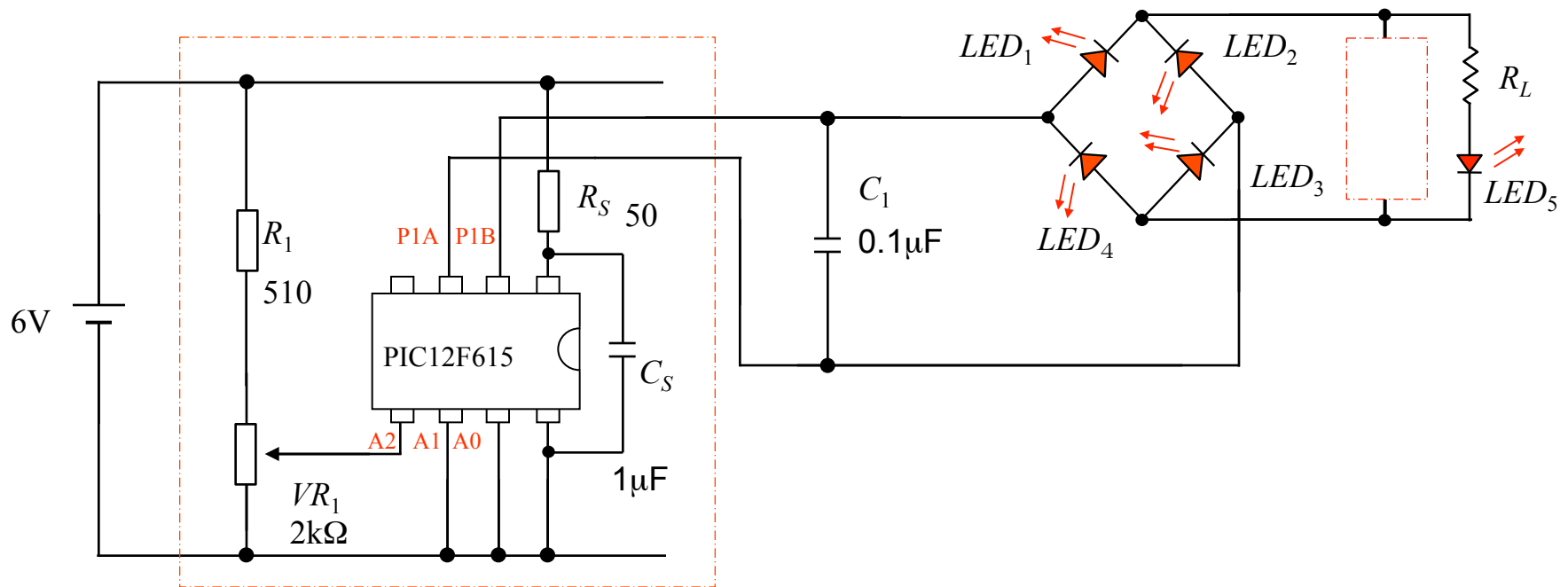Example of the measured output voltage waveform v_o



STEP 2. Circuit construction practice (smoothing circuit)

Design a smoothing circuit. Capacitor C should be designed so that the capacitor can be connected and disconnected to the rectifier by a push switch. Determine the capacitance of capacitor C and the resistance of resistor R_L so that the time constant of the smoothing circuit is approximately 0.24[sec].



STEP 2. Problem 1

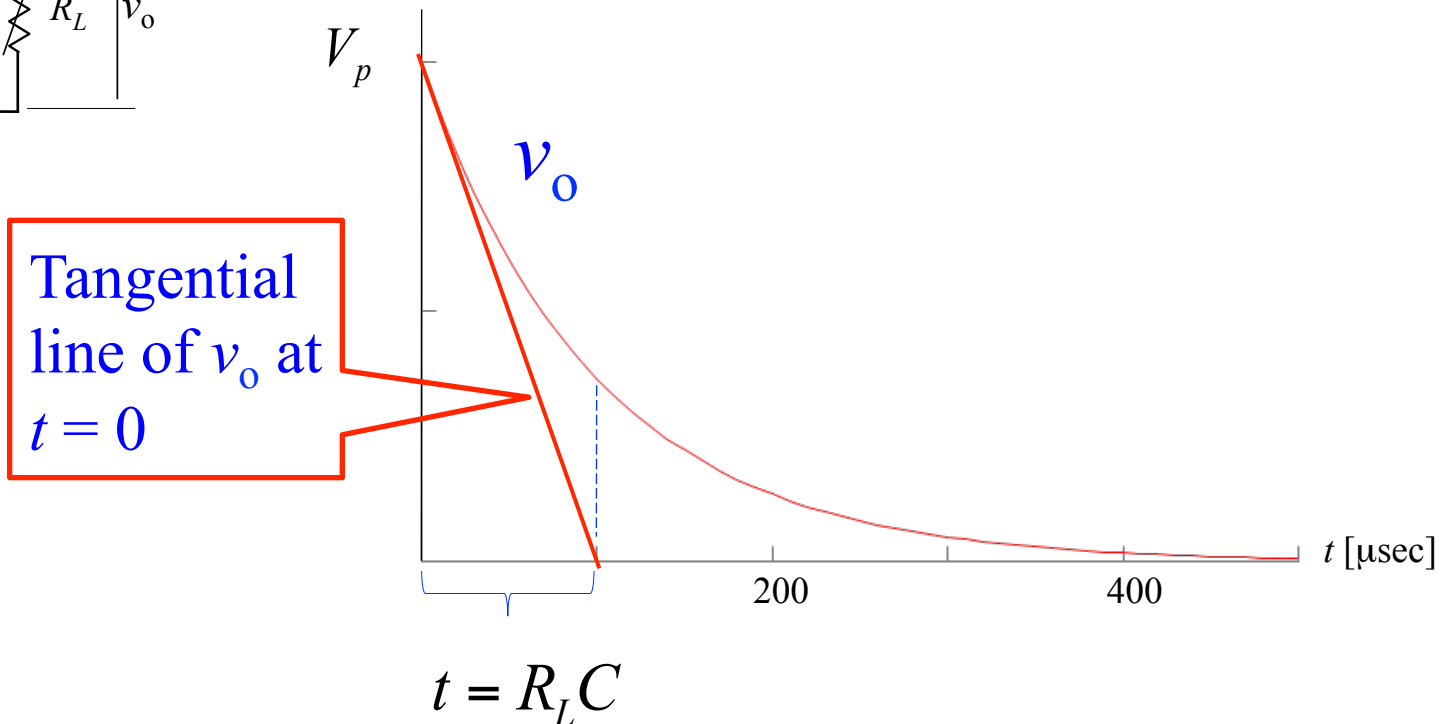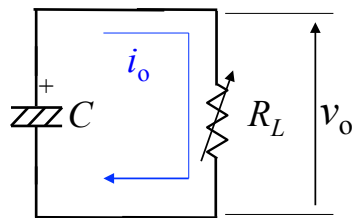The figure below shows a waveform of output voltage v_o in the non-conducting mode of diodes. At $t = 0$, the diode is assumed to stop conducting. Show that the tangential line of v_o at $t = 0$ crosses the horizontal axis at $t = R_L C$.



STEP 2. Problem 2

The figure below shows a series circuit of resistor R and reactor L . Answer the following questions:

- Assume that switches SW_1 and SW_2 are OFF. At $t = 0$, switch SW_1 is turned on. Write the differential equation of this circuit at $t \geq 0$.
- At $t = 0$, current $i = 0$. Solve the differential equation at $t \geq 0$, and obtain the equation of current i .
- At $t = 10 L/R$, switch SW_1 is turned off, and switch SW_2 is turned on. Write the differential equation of this circuit at $t \geq 10 L/R$.
- At $t = 10 L/R$, current $i = I_0$. Solve the differential equation at $t \geq 10 L/R$, and obtain the equation of current i .
- Draw the waveform of current i .

