


Power Electronics

No. 15: Three-phase Inverter II

Takeshi Furuhashi

Furuhashi_at_cse.nagoya-u.ac.jp

Three Pulse PWM

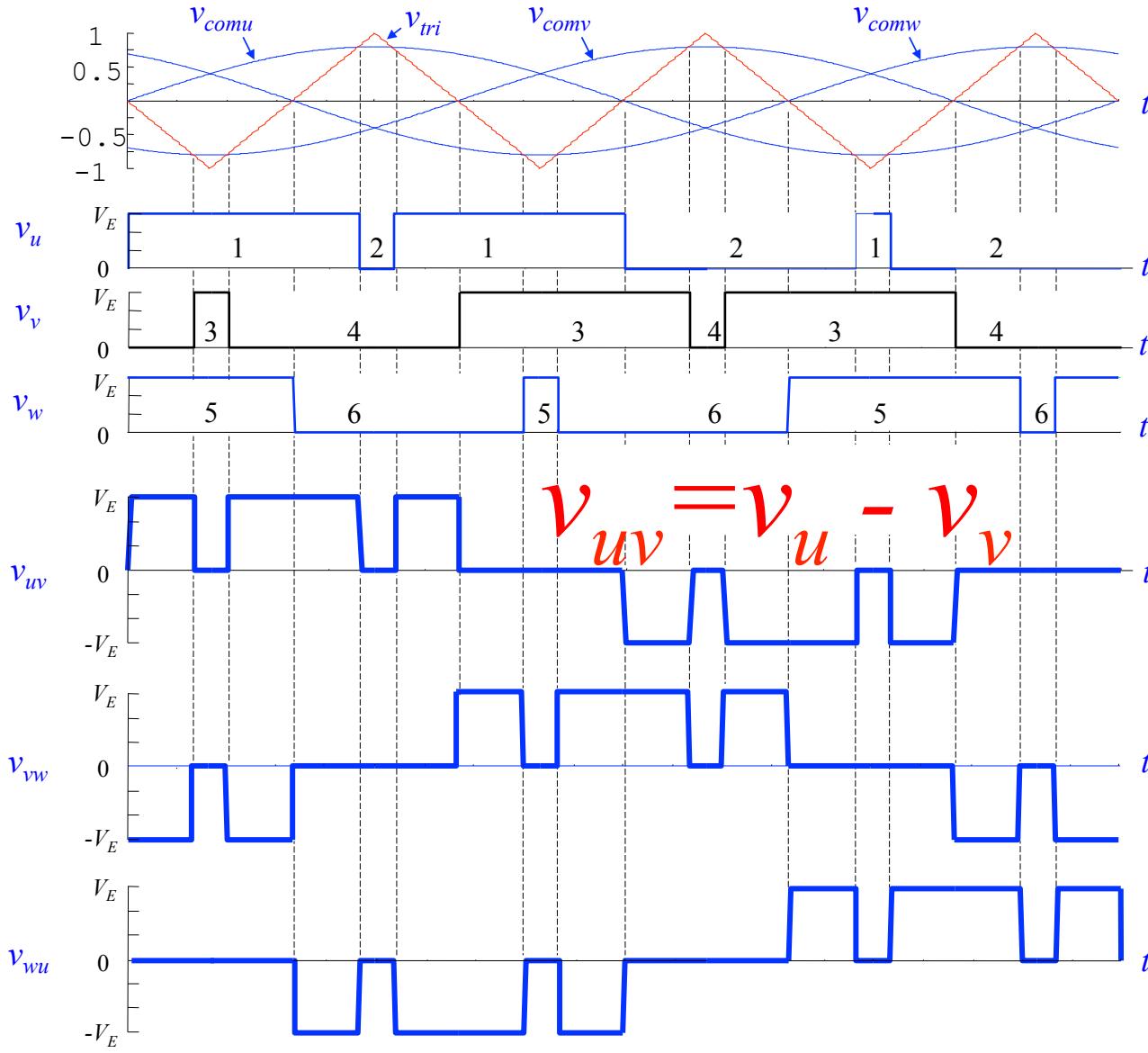

If $v_{comu} > v_{tri}$
Tr1 ON, Tr2 OFF

If $v_{comu} < v_{tri}$
Tr1 OFF, Tr2 ON


If $v_{comv} > v_{tri}$
Tr3 ON, Tr4 OFF


If $v_{comv} < v_{tri}$
Tr3 OFF, Tr4 ON

If $v_{comw} > v_{tri}$
Tr5 ON, Tr6 OFF


If $v_{comw} < v_{tri}$
Tr5 OFF, Tr6 ON

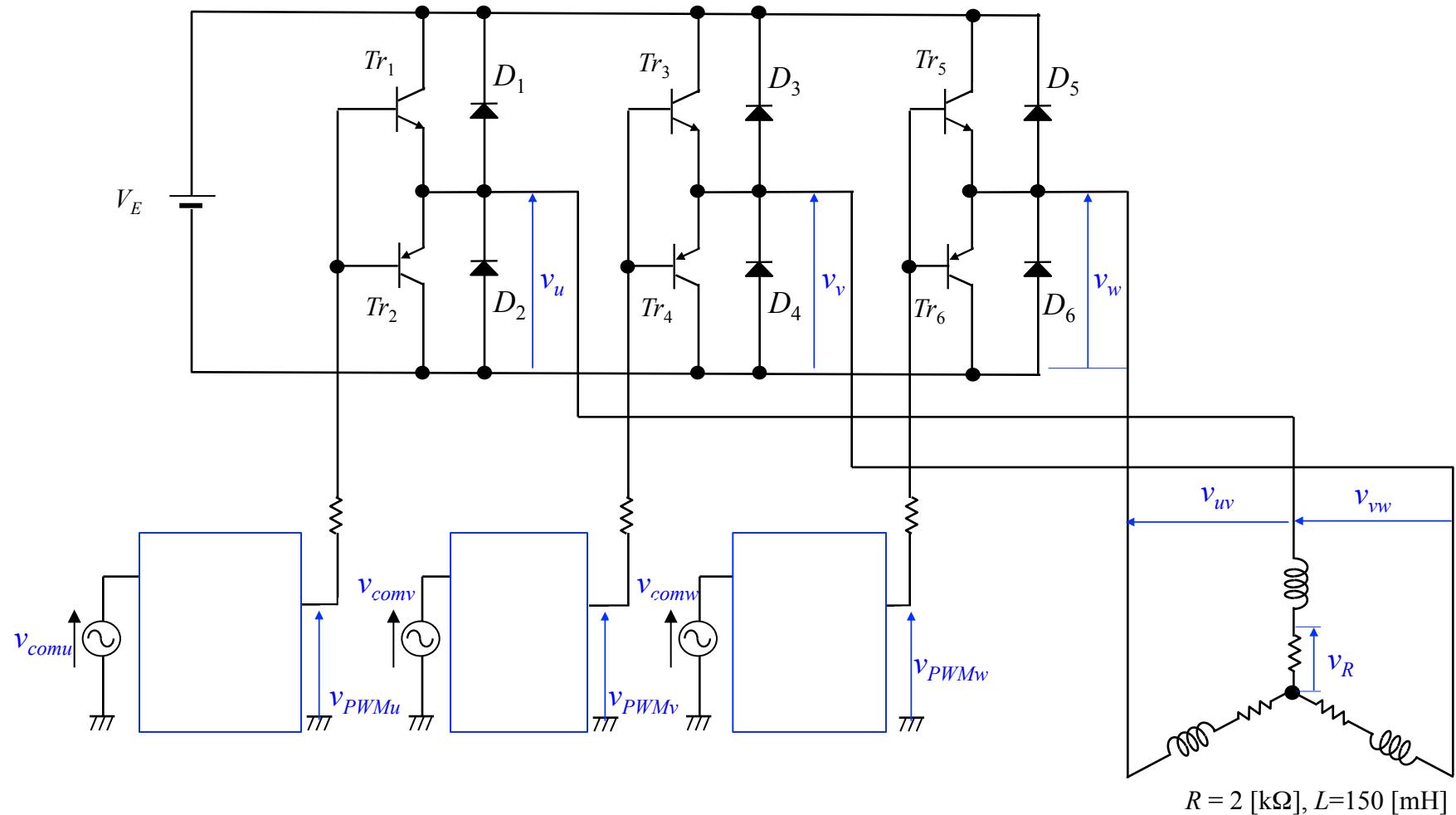Experimental circuit of the three-phase inverter




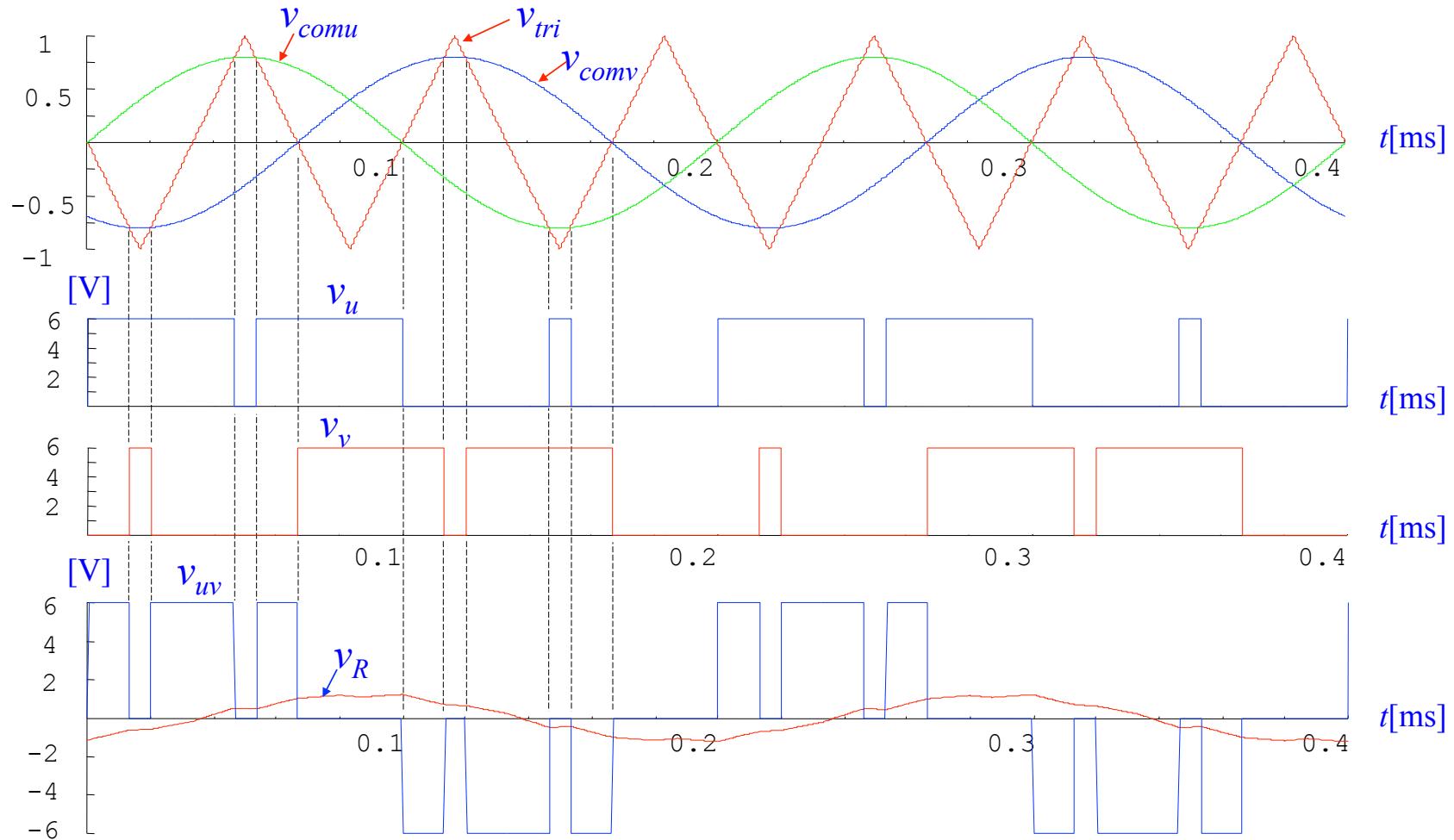



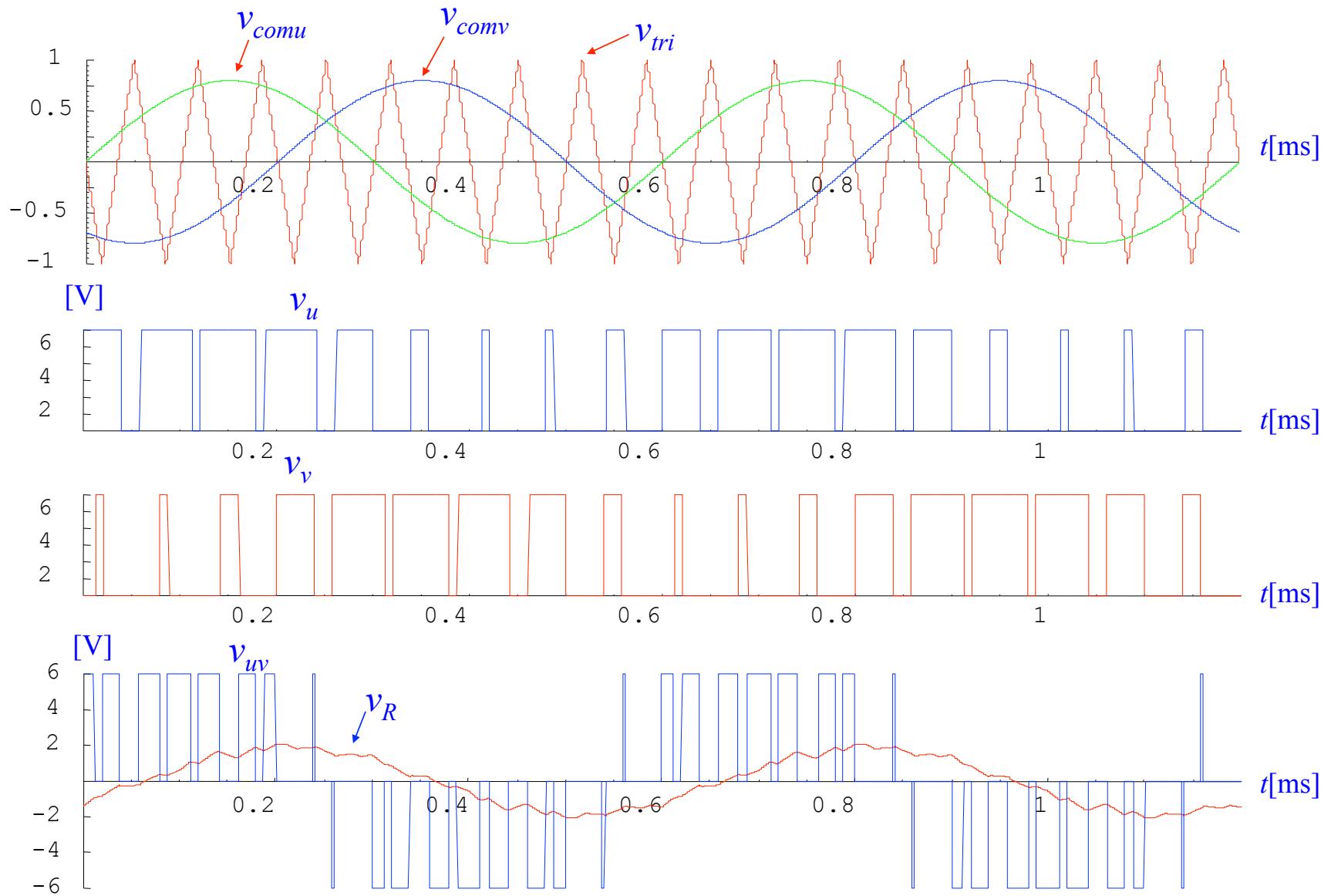
Waveforms of the output voltage and current in the case of a **three-pulse PWM**
 $f_{sw} = 15[\text{kHz}]$, $R=2[\text{k}\Omega]$, $L150[\text{mH}]$, $V_E = 6[\text{V}]$



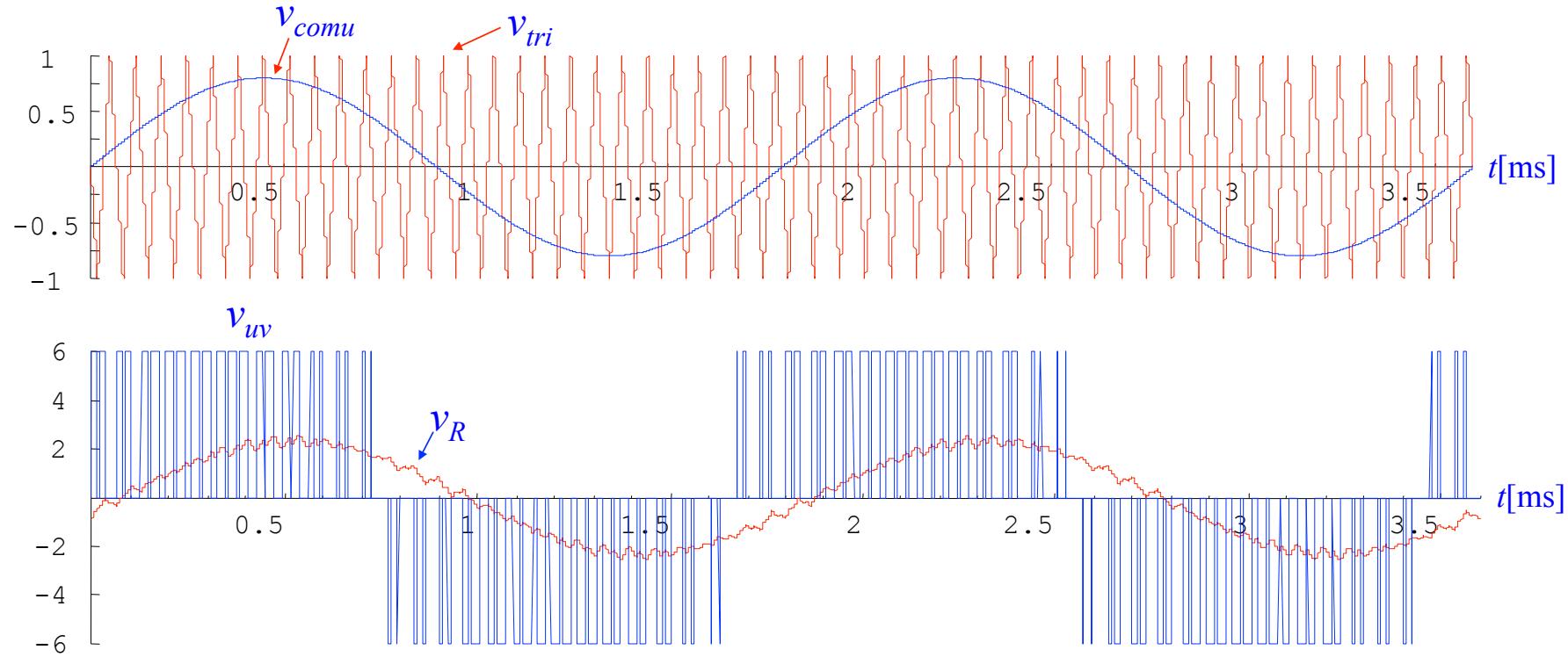
Waveforms of the output voltage and current in the case of a **nine-pulse PWM**
 $f_{sw} = 15[\text{kHz}]$, $R=2[\text{k}\Omega]$, $L150[\text{mH}]$, $V_E = 6[\text{V}]$



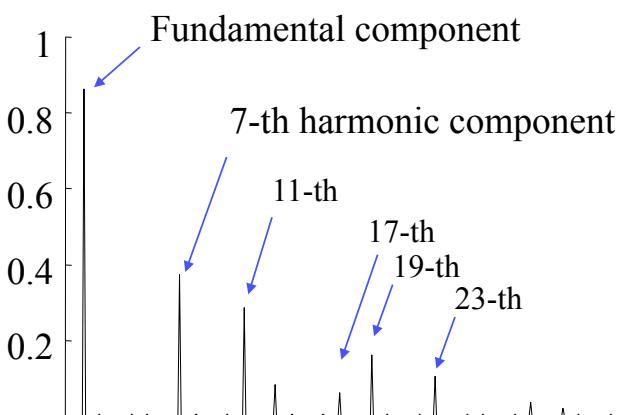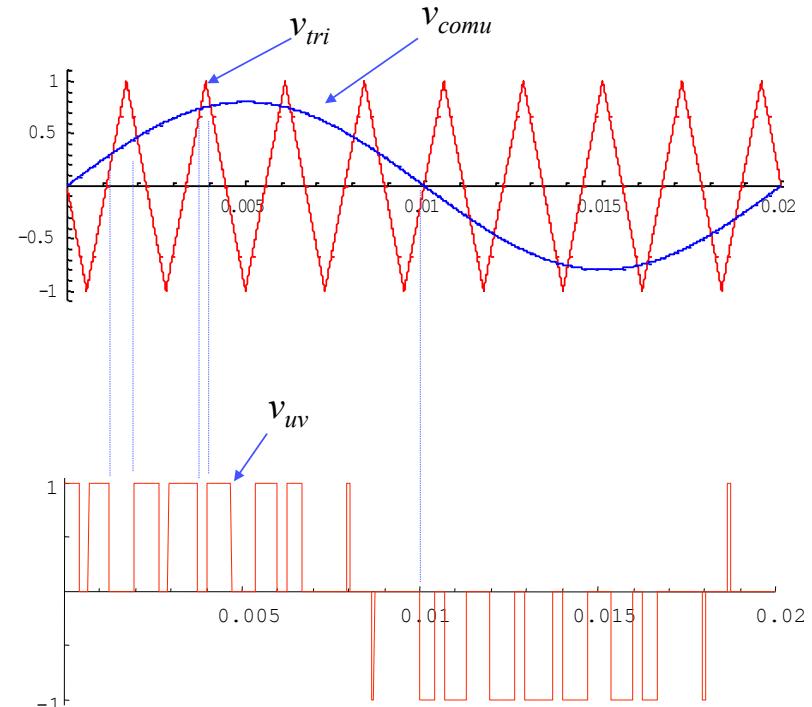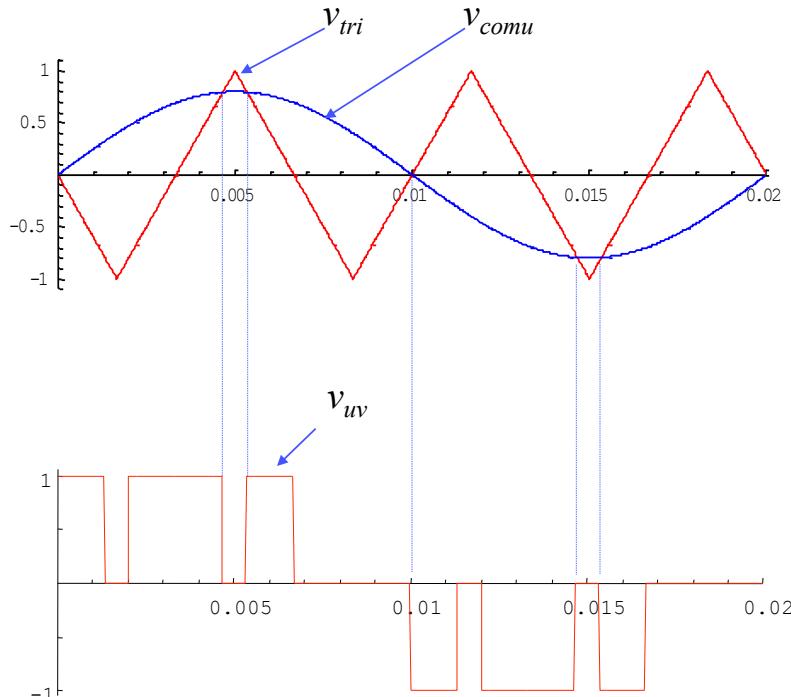Waveforms of the output voltage and current in the case of a **27-pulse PWM**
 $f_{sw} = 15[\text{kHz}]$, $R=2[\text{k}\Omega]$, $L150[\text{mH}]$, $V_E = 6[\text{V}]$




(a) 3-pulse

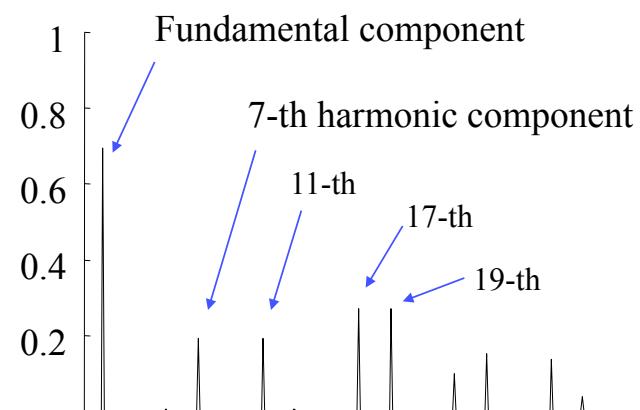


(b) 9-pulse


Asynchronous mode

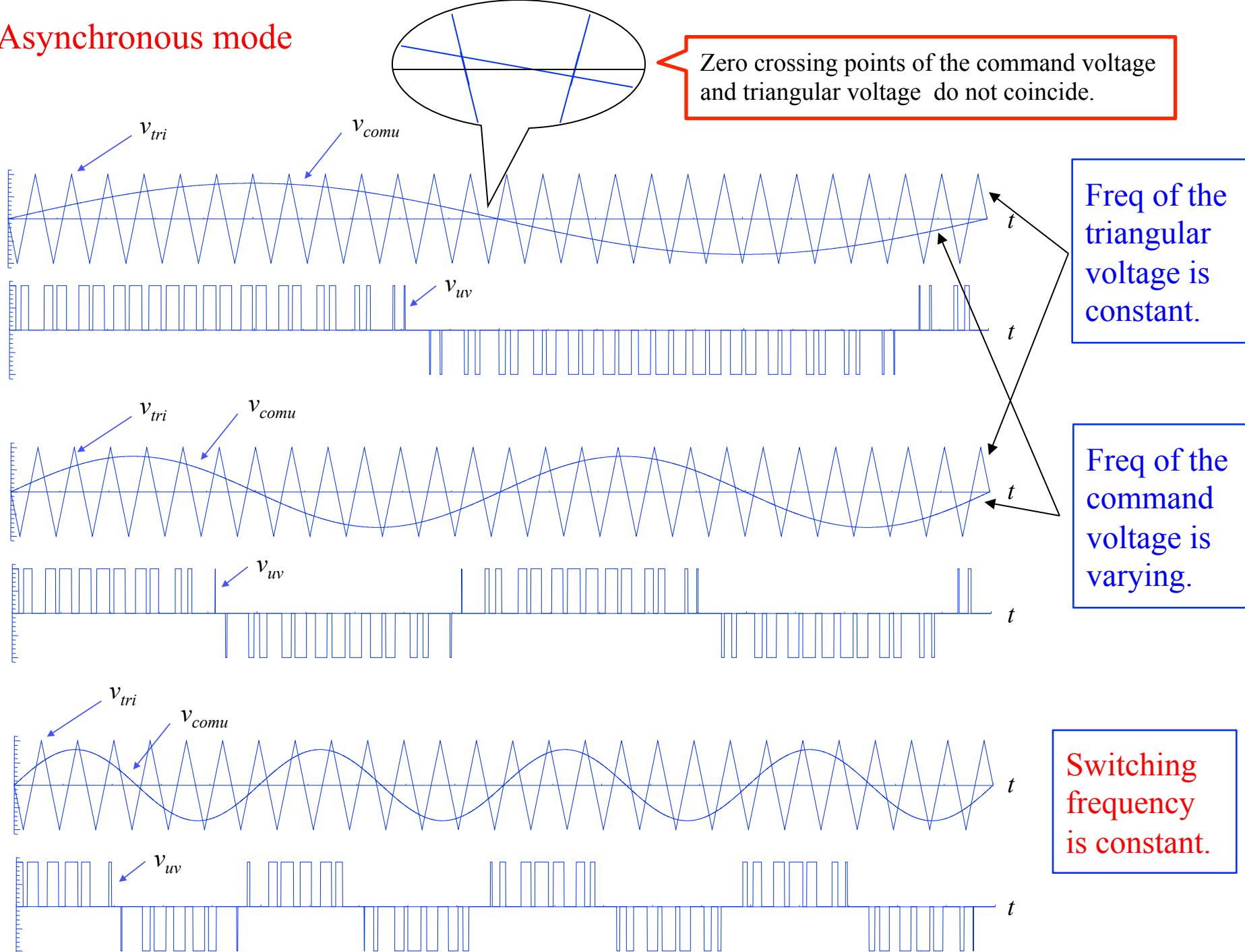


Synchronous mode

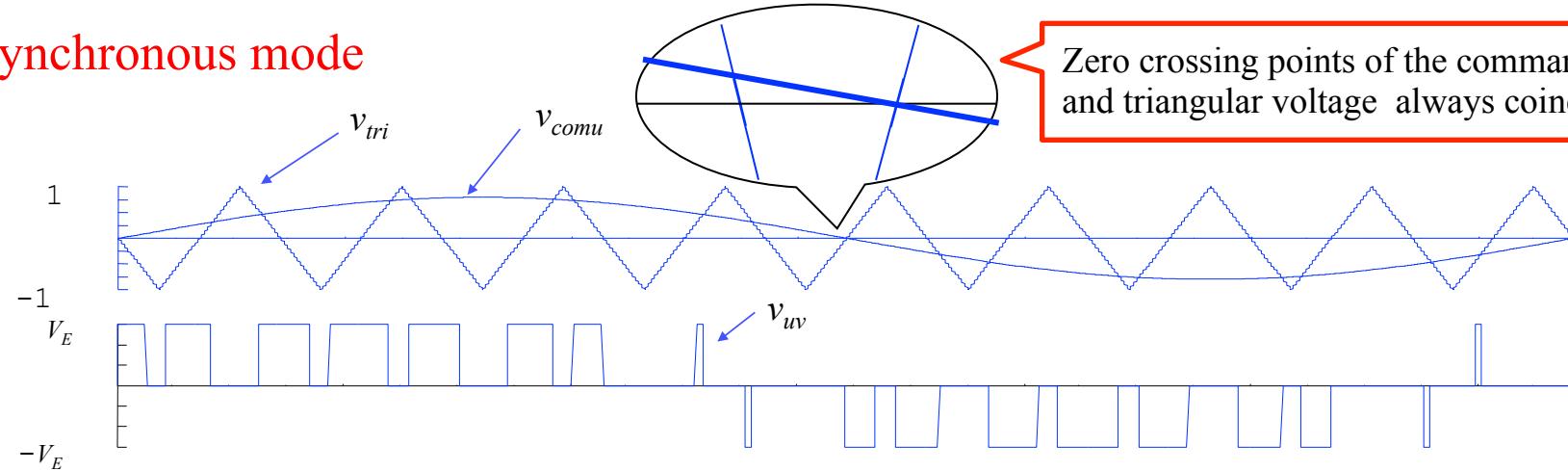

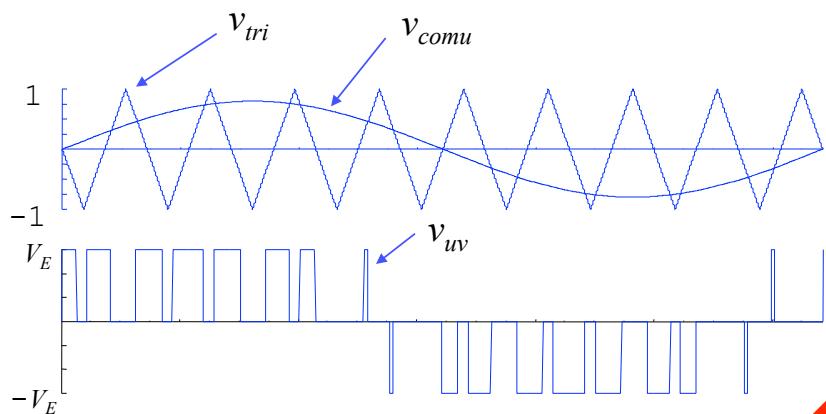Zero crossing points of the command voltage and triangular voltage always coincide.



$$f_{com}/f_{tri} = 1/9$$


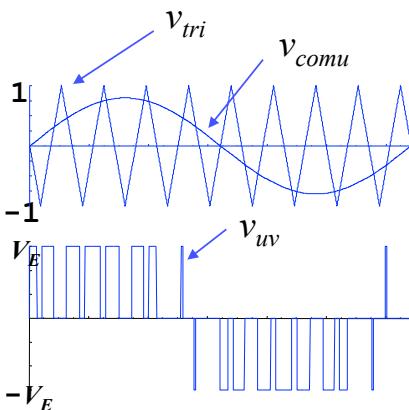


Increased frequency of voltage command
 ↓
 Increased switching frequency

Switching loss by transistor

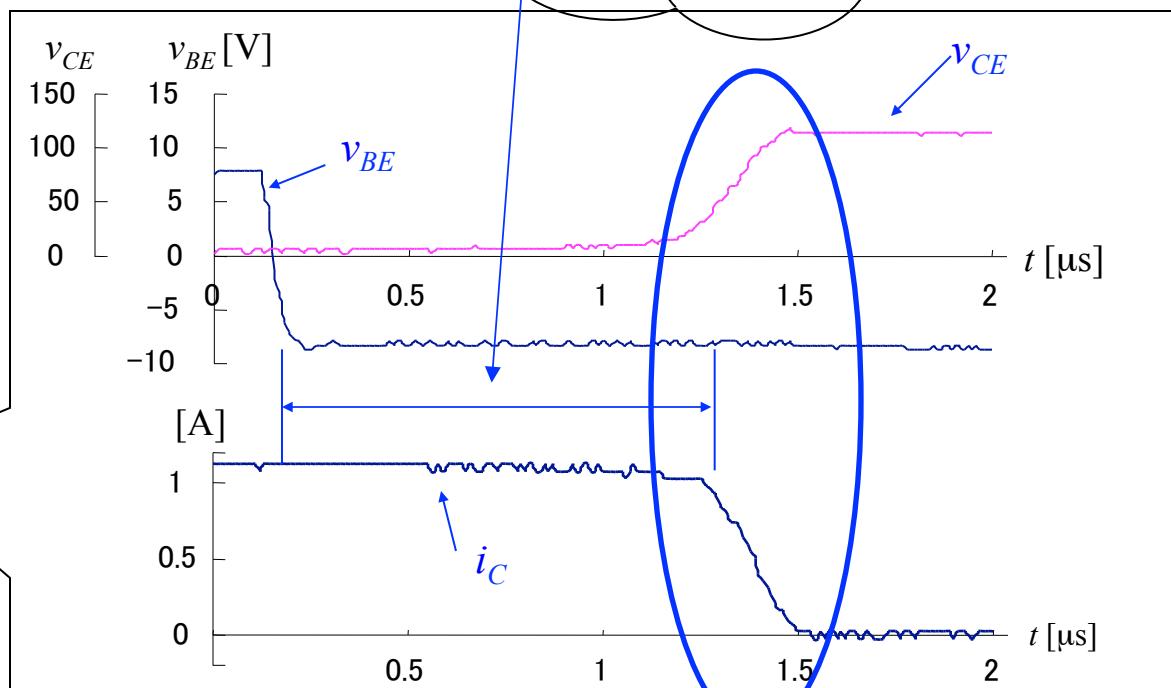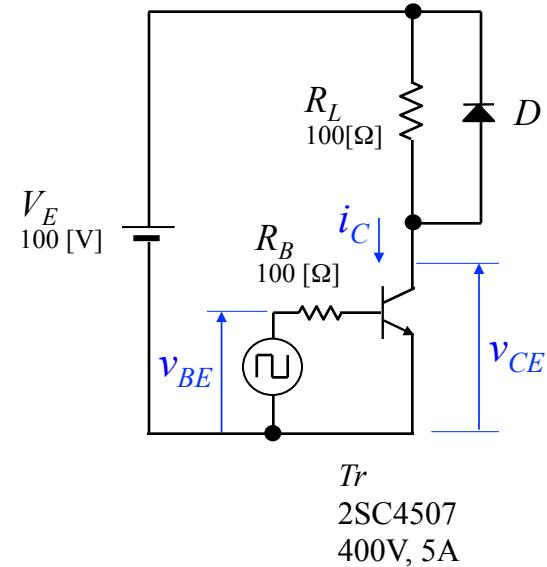(example of an experimental waveform)

Collector current i_C keeps flowing even though the voltage between the base and emitter v_{BE} is made negative.



Energy loss E_{loss} occurs while $v_{CE} > 0$ and $i_C > 0$.

$$E_{loss} = \int v_{CE} i_C dt \text{ [J]}$$

Synchronous mode

Increase of f_{sw}




→ Increase of power loss

$$P_{loss} = E_{loss} \times f_{sw} \text{ [W]}$$


→ Upper limit of f_{sw}

Ex. Shinkansen train

700-Series (1.5kHz)


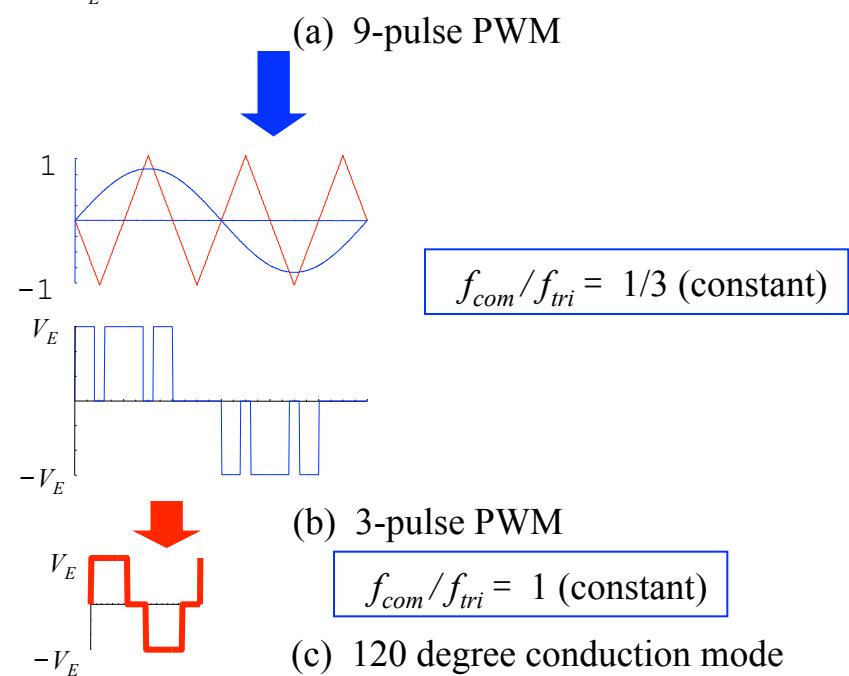
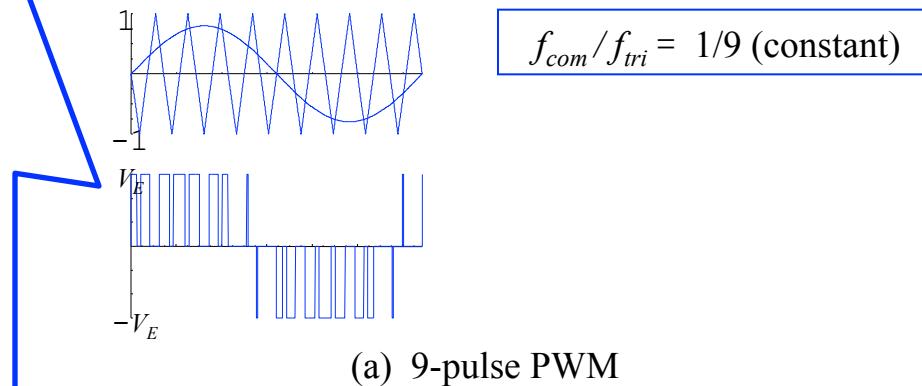
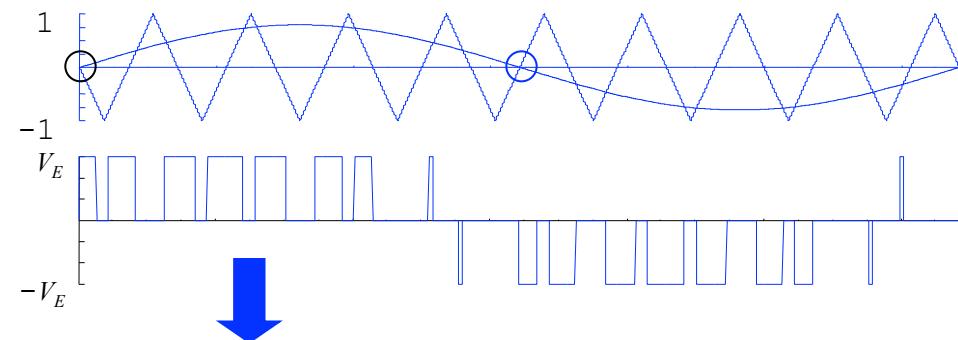


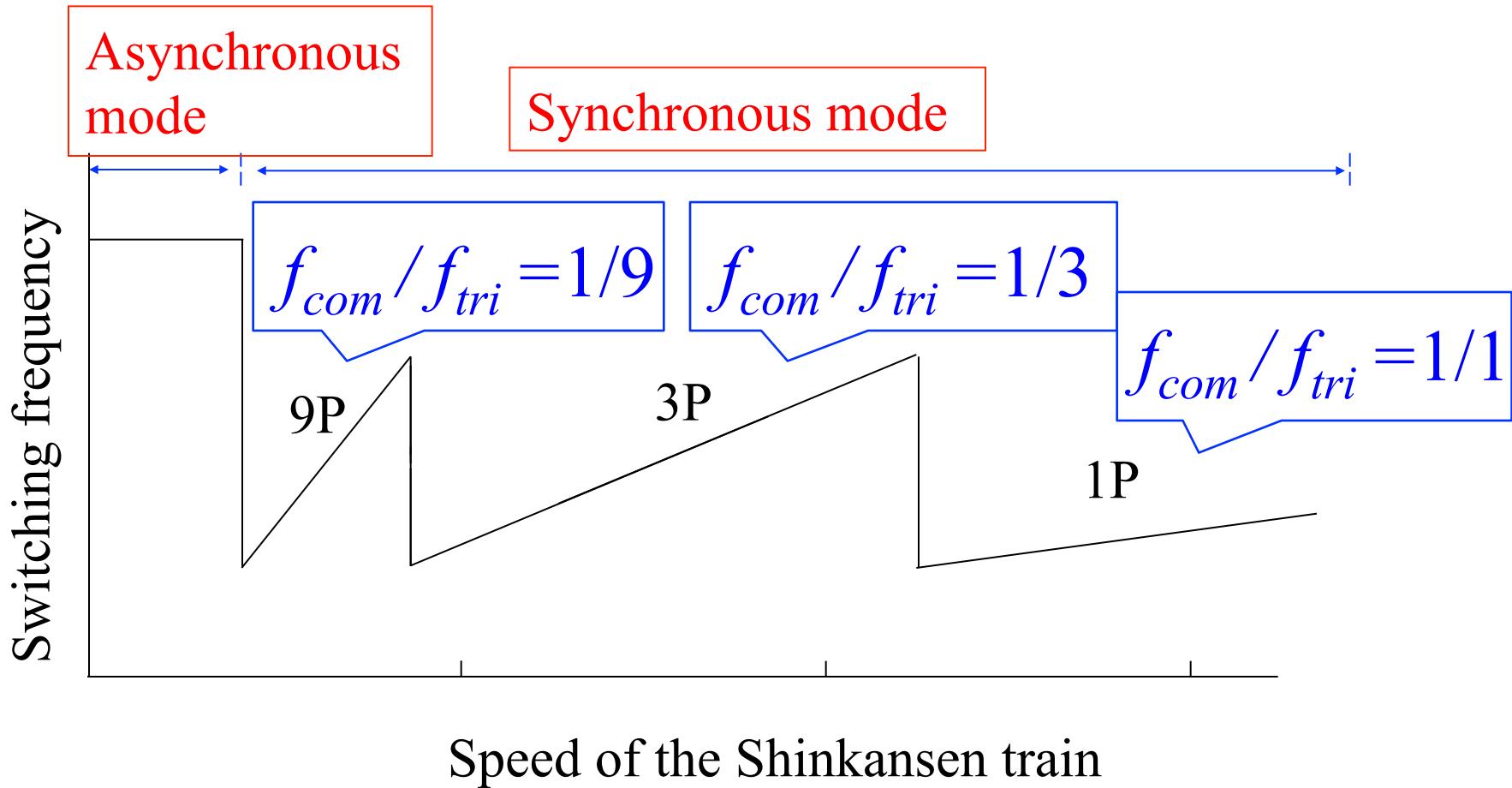Example of switching between asynchronous mode and synchronous mode




Synchronous mode at high speed

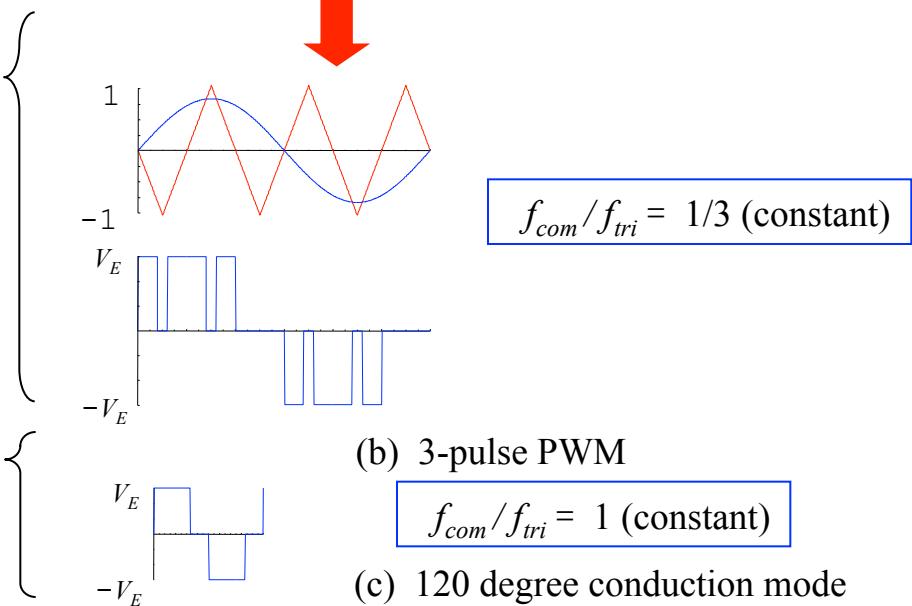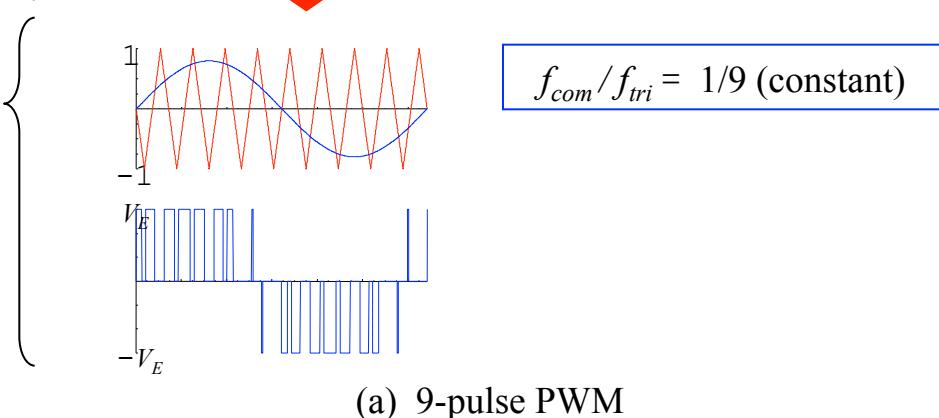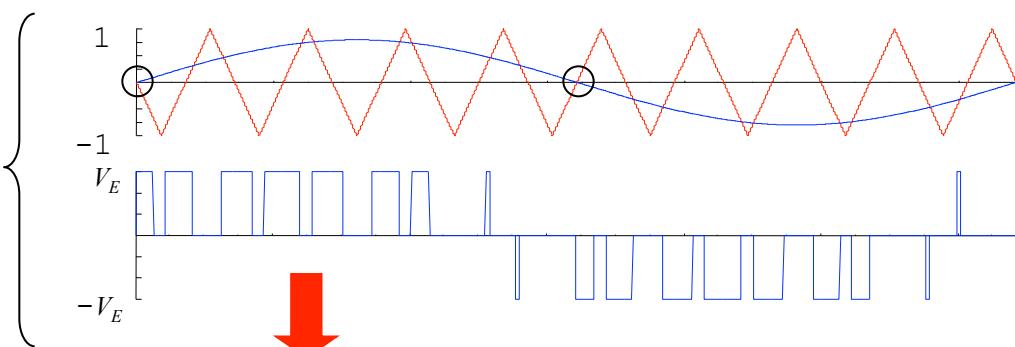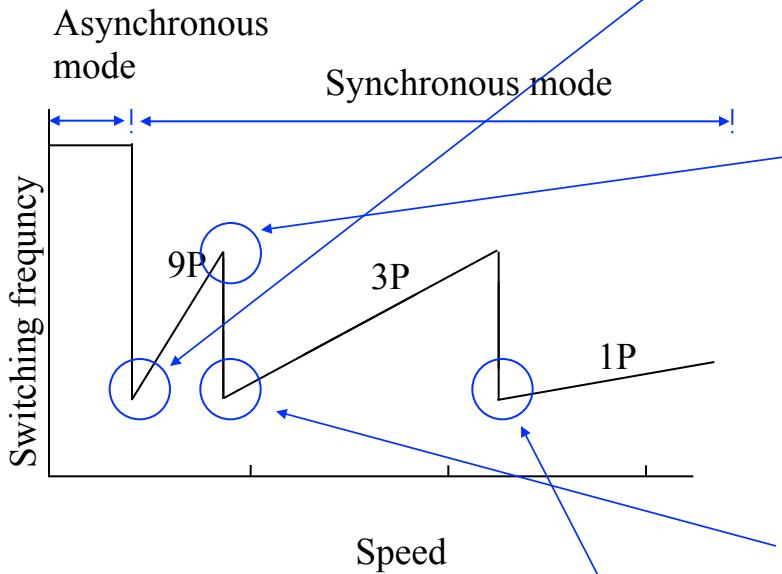Zero crossing points of the voltage command and triangular waveform always coincide.




If not synchronized!

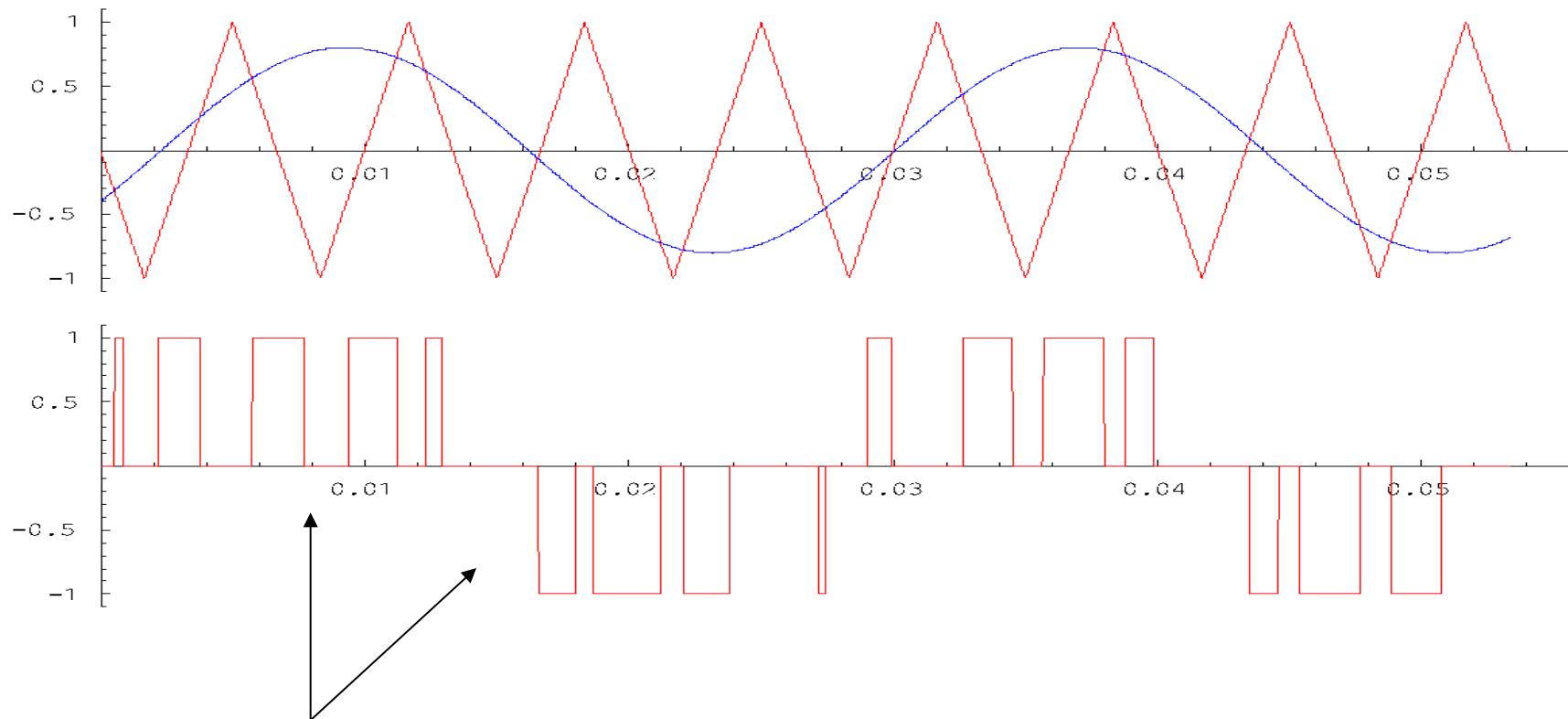

Asymmetry between positive side and negative side.

Waveform varies at every cycle.

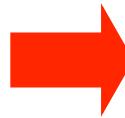

Over heating, vibration of motor
noisy motor sound

Shinkansen



<http://ja.wikipedia.org/wiki/新幹線100系電車>

100-series (1985~)

Max speed: 275 km/h

Main motor: DC series wound
motor

Power converter: Thyristor type

Braking method: Resistance braking



<http://ja.wikipedia.org/wiki/新幹線300系電車>

300-series ((1990~))

Max speed: 285 km/h

Main motor: Three phase induction motor

Power converter: **VVVF Inverter (GTO Thyristor)**

Switching frequency **420 [Hz]**

Braking method: Regenerative braking

The induction motor's output power is 130% and its weight is half of that of the DC motor. Regenerative braking was first introduced to Shinkansen trains.



<http://ja.wikipedia.org/wiki/新幹線500系電車>

500-series(1992～)

Max speed: 365km/h

Main motor: Three phase induction motor

Power converter: **VVVF Inverter (GTO Thyristor)**

Braking method: Regenerative braking



<http://ja.wikipedia.org/wiki/新幹線N700系電車>

N700-series(2005～)

Main motor: Three phase induction motor

Power converter: **VVVF Inverter (IGBT)**

Switching frequency: **1.5 [kHz]**

Braking method: Regenerative braking

- Asynchronous mode
 - From the time train leaves a station
 - 300-series approx. 5 sec
 - 500-series approx. 22 sec
 - N700-series approx. 25 sec
- Sound noise level
 - Sound noise from the motors of N700-series is less than from previous types of Shinkansen trains.