


# Answers to Homework

# Exercise 1.4.2 (Homework)

## Exercise 1.4.2 (Homework)

Exercise 1.4.2. This is your homework.


# Exercise 1.4.2 (Homework)

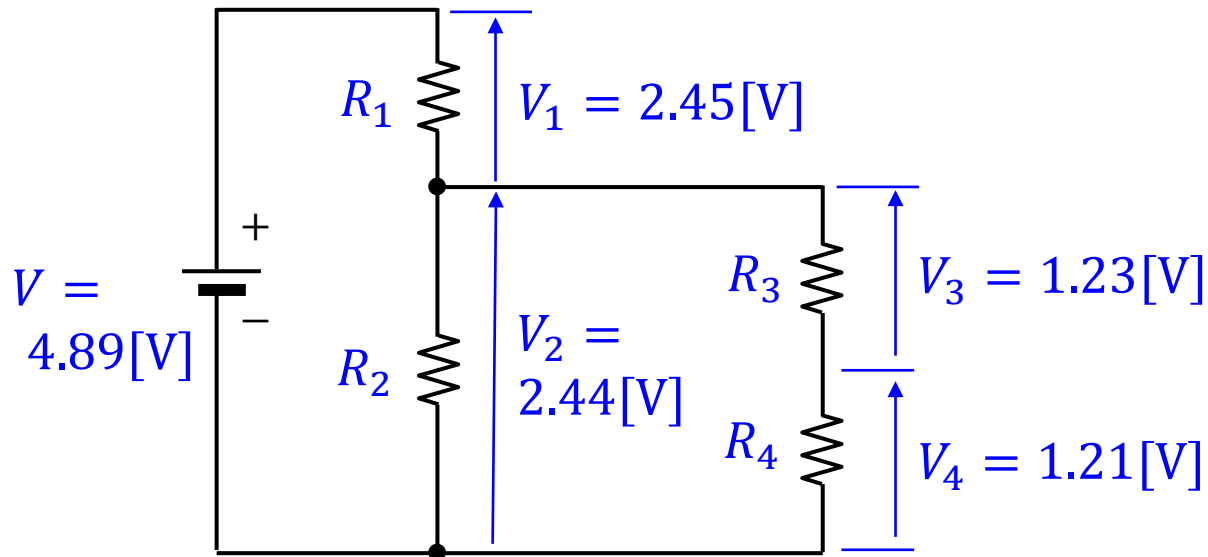

Find the ratios

$$\frac{R_1}{R_{234}}, \quad \frac{R_3}{R_4}$$

$R_{234}$ : combined  
resistance

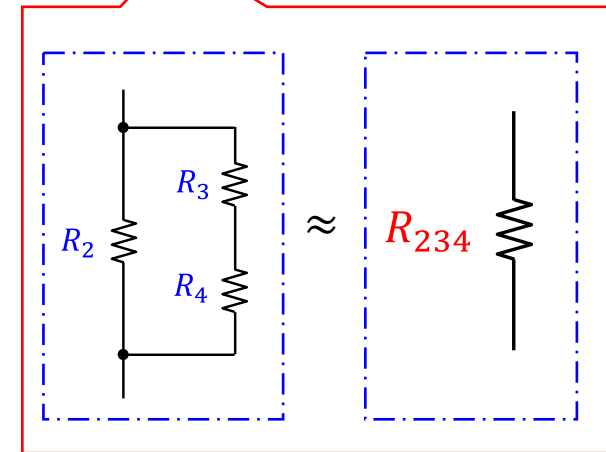


Find the ratios of  $R_1/R_{234}$ , and  $R_3/R_4$ , where  $R_{234}$  is the combined resistance of  $R_2$ ,  $R_3$ , and  $R_4$ . The right bottom figure shows an image of the combined resistance.

# Exercise 1.4.2 (Answers)

## Exercise 1.4.2 (Answers)

# Exercise 1.4.2 (Answers)

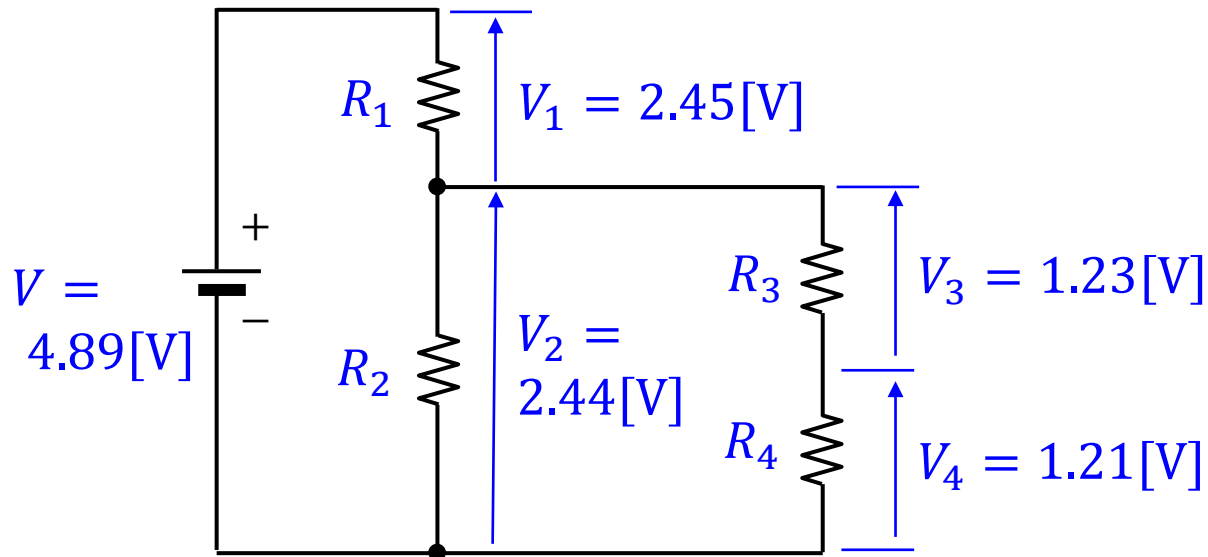

$$\begin{aligned}\frac{R_1}{R_{234}} &= \frac{V_1}{V_2} \\ &= \frac{V_1}{V_3 + V_4} \\ &= \frac{2.45}{2.44} \\ &= 1.00\end{aligned}$$



$$\begin{aligned}\frac{R_3}{R_4} &= \frac{V_3}{V_4} \\ &= \frac{1.23}{1.21} \\ &= 1.02\end{aligned}$$

$R_1/R_{234} = 1.00$ , and  $R_3/R_4 = 1.02$ . The numbers are rounded at the third decimal places.

# Exercise 2.2.1 (Homework)

Exercise 2.2.1 (Homework)

# Exercise 2.2.1 (Homework)

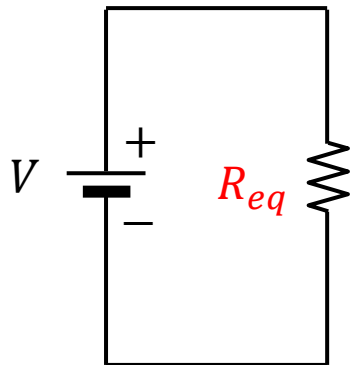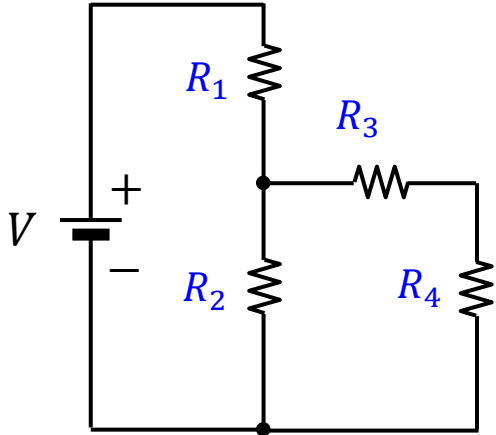

Write  $R_{eq}$ .


Write the resistance  $R_{eq}$  which is equivalent to the combined resistance of  $R_1, \dots, R_4$  in the top circuit.

# Exercise 2.2.1 (Answer)

Exercise 2.2.1 (Answer)



# Exercise 2.2.1


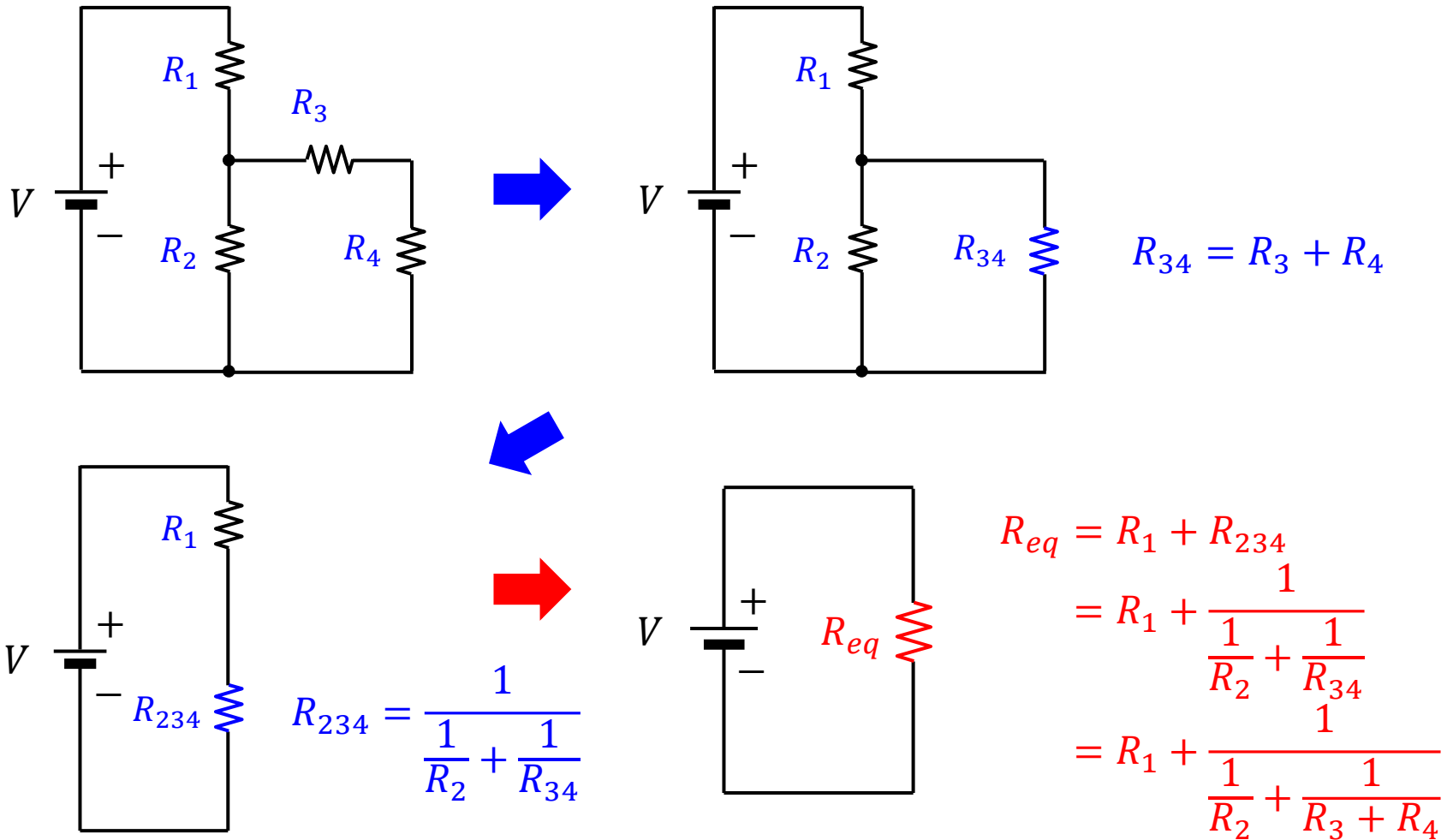


The equivalent resistance  $R_{eq}$  of  $R_1, \dots, R_4$  is that  $R_{eq} = R_1 + 1/(1/R_2 + 1/(R_3 + R_4))$ .

# Exercise 2.2.2 (Homework)

Exercise 2.2.2 (Homework)

# Exercise 2.2.2 (Homework)

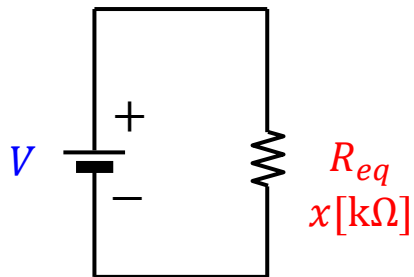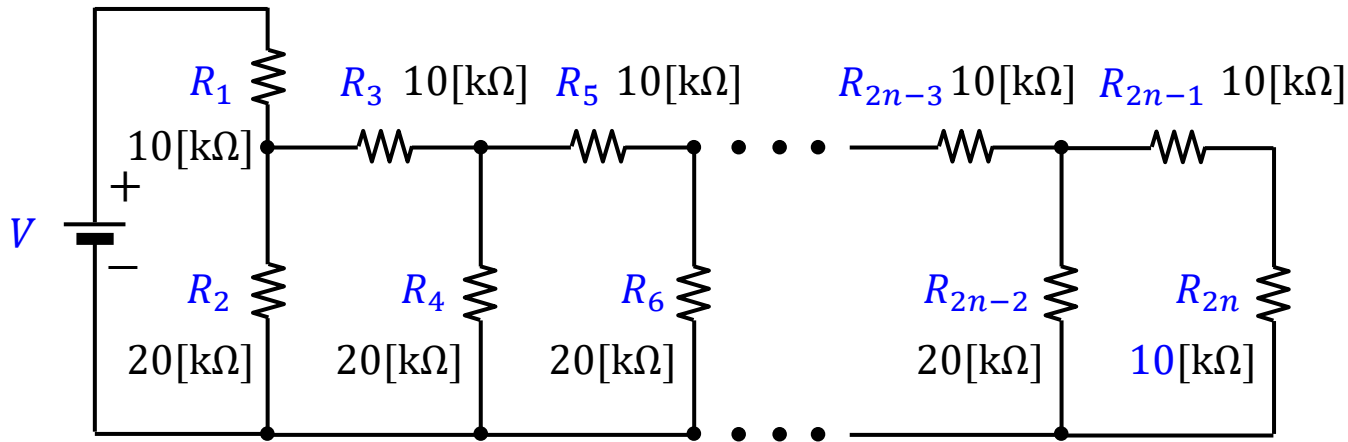

Find  $R_{eq}$ .



Find the equivalent resistance  $R_{eq}$ .

# Exercise 2.2.2 (Answer)

Exercise 2.2.2 (Answer)

---

# Exercise 2.2.2 (Answer)

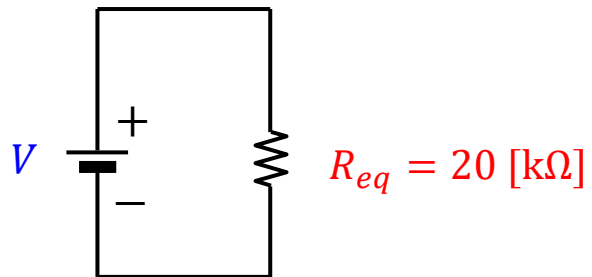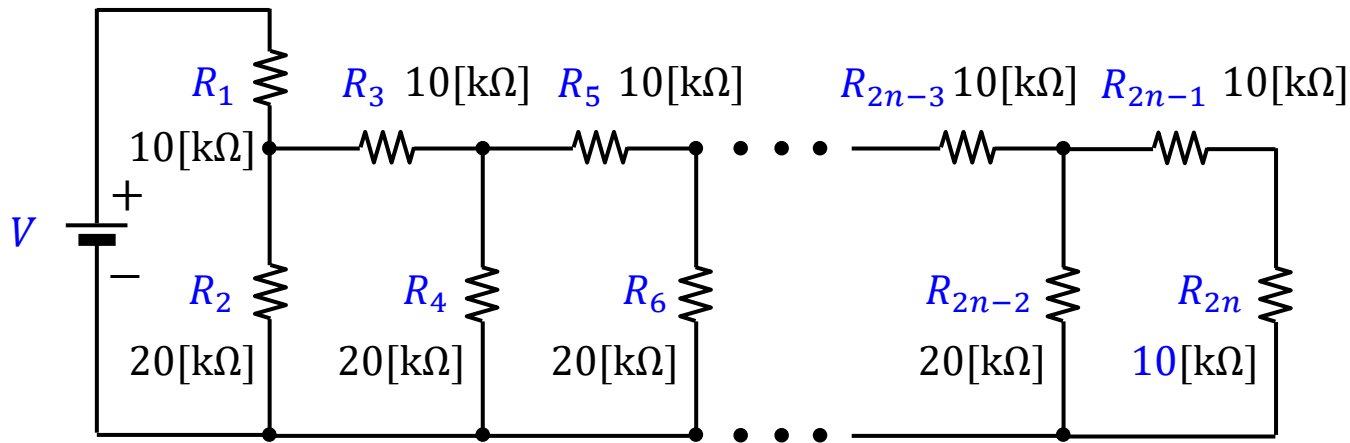


The result of Exercise 2.2.1 can be applied to this circuit.

# Exercise 3.2 (Homework)

Exercise 3.2 (Homework)

# Exercise 3.2 (Homework)

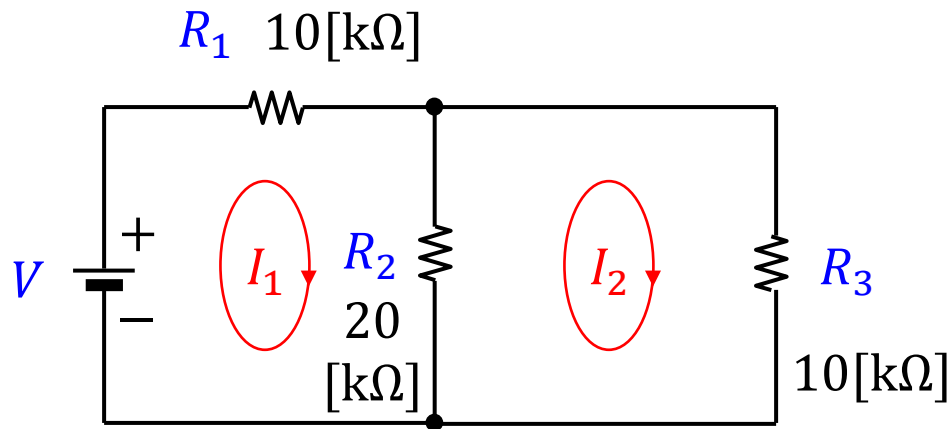

1. Write the currents  $I_1, I_2$ .
2. Calculate  $I_1$  and  $I_2$  using the voltage  $V$  measured in Experiment 3.2.2.


Calculate  $I_1, I_2$  with the measured  $V$  in Experiment 3.2.2.

# Exercise 3.2 (Answers)

Exercise 3.2 (Answers)



# Exercise 3.2 (Answers)

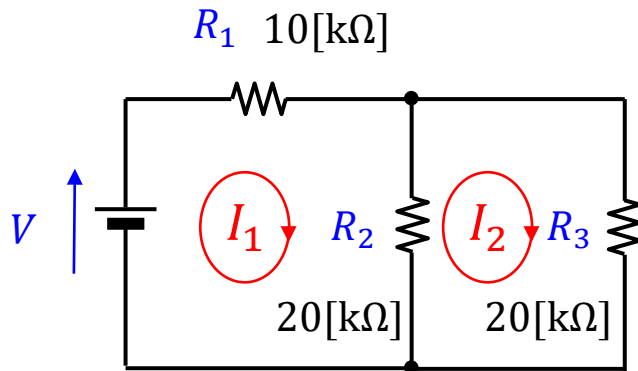

KVL gives that

$$V = (R_1 + R_2)I_1 - R_2I_2$$
$$0 = -R_2I_1 + (R_2 + R_3)I_2$$

Then


$$\begin{pmatrix} V \\ 0 \end{pmatrix} = \begin{pmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{pmatrix}^{-1} \begin{pmatrix} V \\ 0 \end{pmatrix}$$

$$I_1 = \frac{R_2 + R_3}{R_1R_2 + R_2R_3 + R_3R_1} V$$

$$I_2 = \frac{R_2}{R_1R_2 + R_2R_3 + R_3R_1} V$$

# Exercise 3.2 (Answers)

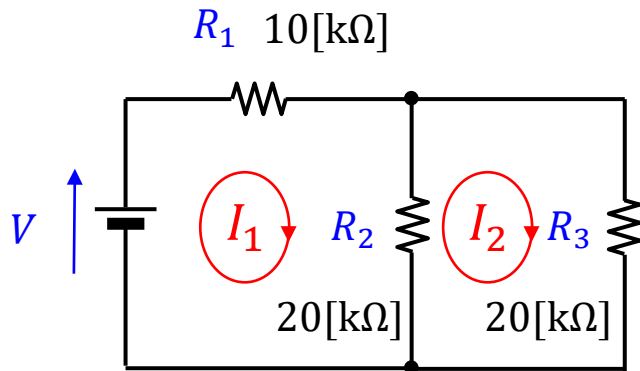

The measured values in Exp. 3.2.2:

$$V = 3.88[\text{V}]$$

$$I_1 = 194 [\mu\text{A}]$$

$$I_2 = 97 [\mu\text{A}]$$

Given that  $R_1 = 10[\text{k}\Omega]$ ,  $R_2 = R_3 = 20[\text{k}\Omega]$ , and the measured  $V = 3.88[\text{V}]$ , then


$$I_1 = \frac{3.88[\text{V}]}{20[\text{k}\Omega]} = 194 [\mu\text{A}]$$

$$I_2 = \frac{3.88[\text{V}]}{40[\text{k}\Omega]} = 97 [\mu\text{A}]$$

# Exercise 3.5 (Homework)

Exercise 3.5 (Homework)

# Exercise 3.5 (Homework)

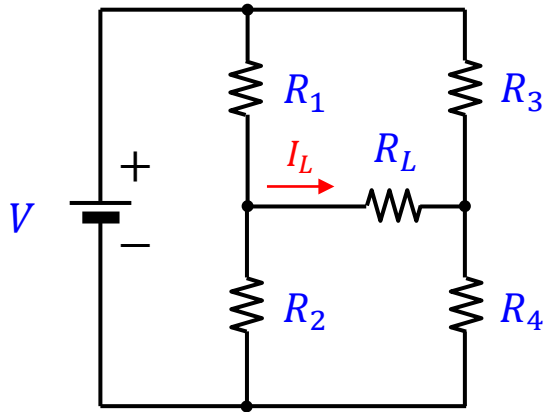


Show that if  $R_2 R_3 = R_2 R_4$ , then  $I_L = 0$ .


# Exercise 3.5 (Answer)

Exercise 3.5 (Answer)

# Exercise 3.5 (Answer)



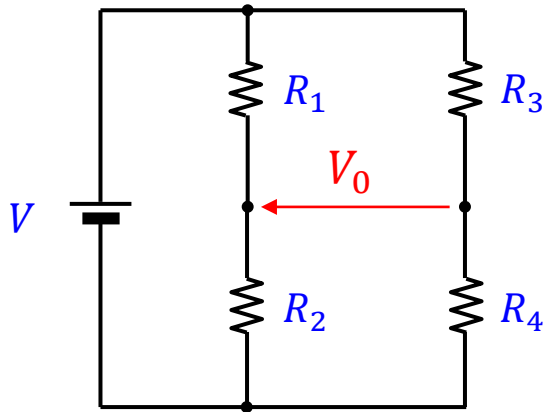

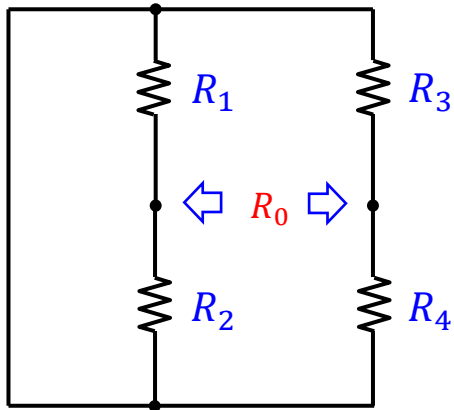
$$\begin{aligned} V_0 &= \frac{R_3}{R_1 + R_3} V - \frac{R_4}{R_2 + R_4} V \\ &= \frac{R_2 R_3 - R_2 R_4}{(R_1 + R_3)(R_2 + R_4)} V \end{aligned}$$



$$\begin{aligned} R_0 &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_3}} + \frac{1}{\frac{1}{R_2} + \frac{1}{R_4}} \\ &= \frac{R_1 R_3}{R_1 + R_3} + \frac{R_2 R_4}{R_2 + R_4} \end{aligned}$$

# Exercise 3.5 (Answer)

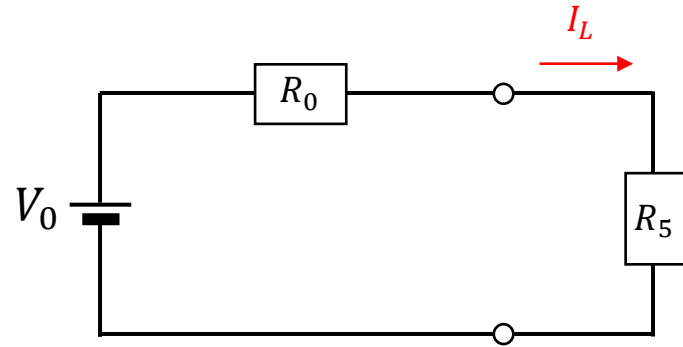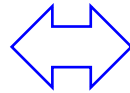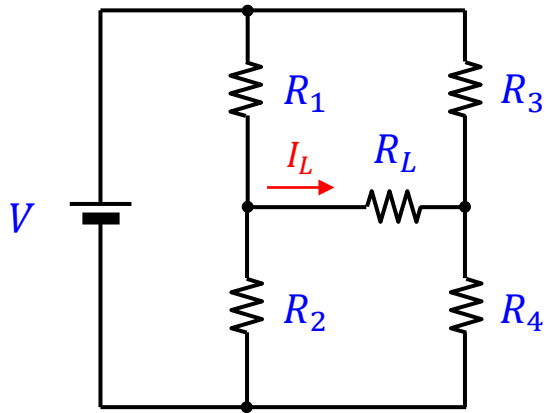

if  $R_2 R_3 = R_2 R_4$ ,


then  $V_0 = 0$  and  $I_L = 0$

# Exercise 4.4.1 (Homework)


Exercise 4.4.1 (Homework)



# Exercise 4.4.1 (Homework)

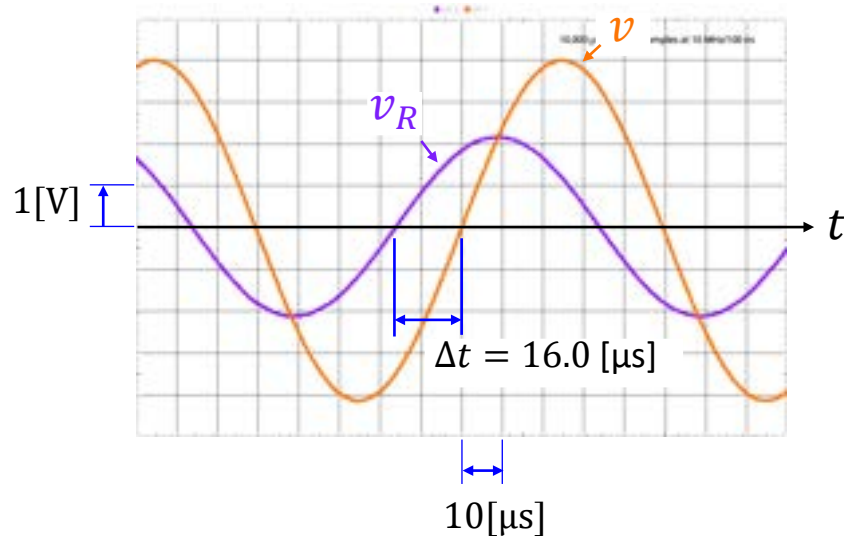

(a)  $f = 10[\text{kHz}]$

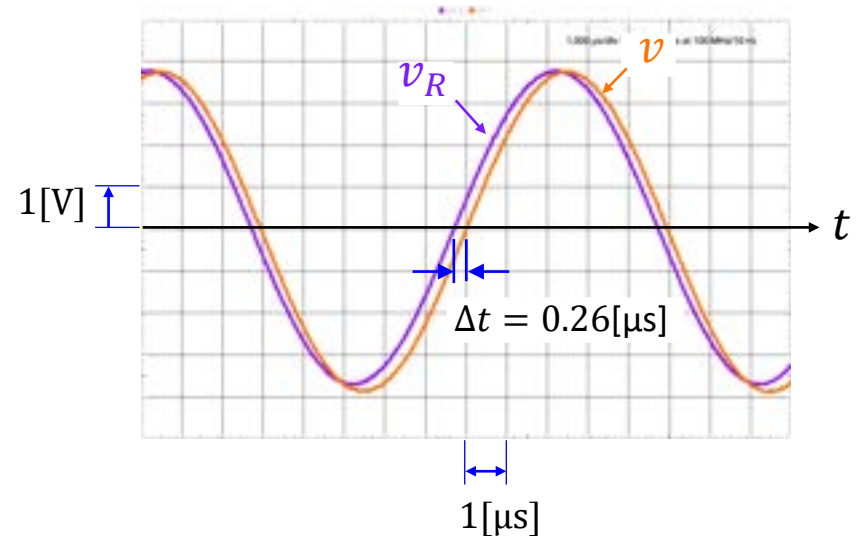

(b)  $f = 100[\text{kHz}]$

Calculate the phase shifts  $\theta_S$  of  $v$  relative to  $v_R$  in (a) and (b). Answer in  $[\circ]$  and  $[\text{rad}]$ .

# Exercise 4.4.1 (Answers)

Exercise 4.4.1 (Answers)

# Exercise 4.4.1 (Answers)

(a)  $f = 10[\text{kHz}]$

$$T = \frac{1}{f} = \frac{1}{10000} = 100 [\mu\text{s}]$$

$$\theta_s = -\frac{\Delta t}{T} \times 360 [^\circ] = -\frac{16.0 [\mu\text{s}]}{100 [\mu\text{s}]} \times 360 [^\circ] = -57.6 [^\circ]$$

$$\theta_s = -\frac{\Delta t}{T} \times 2\pi [\text{rad}] = -\frac{16.0 [\mu\text{s}]}{100 [\mu\text{s}]} \times 2\pi [\text{rad}] = -0.320\pi [\text{rad}]$$

(b)  $f = 100[\text{kHz}]$

$$T = \frac{1}{f} = \frac{1}{100000} = 10 [\mu\text{s}]$$


$$\theta_s = -\frac{\Delta t}{T} \times 360 [^\circ] = -\frac{0.26 [\mu\text{s}]}{10 [\mu\text{s}]} \times 360 [^\circ] = -9.4 [^\circ]$$

$$\theta_s = -\frac{\Delta t}{T} \times 2\pi [\text{rad}] = -\frac{0.26 [\mu\text{s}]}{10 [\mu\text{s}]} \times 2\pi [\text{rad}] = -0.052\pi [\text{rad}]$$


# Exercise 4.4.2 (Homework)

Exercise 4.4.2 (Homework)

# Exercise 4.4.2 (Homework)

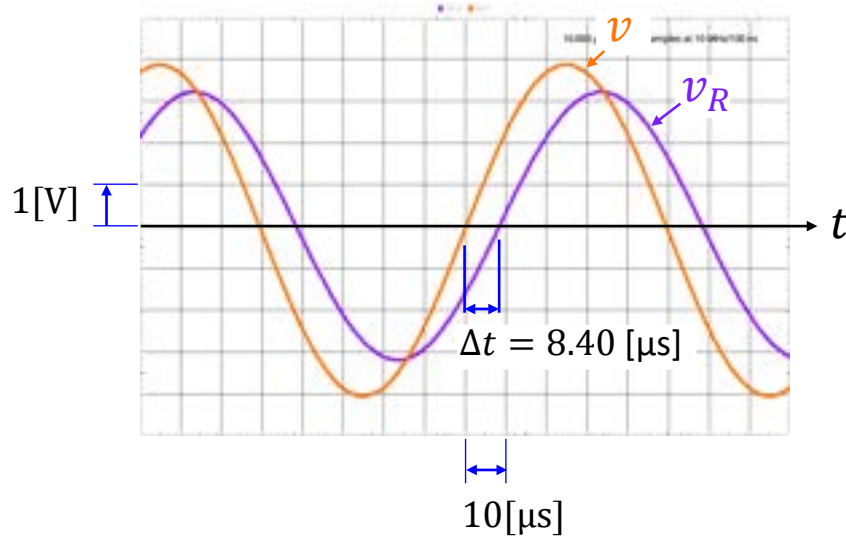

(a)  $f = 10[\text{kHz}]$

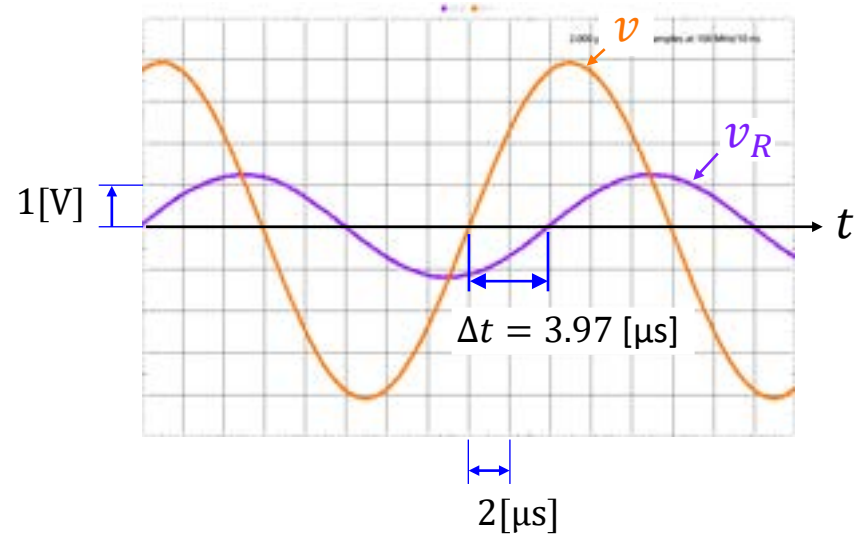

(b)  $f = 50[\text{kHz}]$

Calculate the phase shifts  $\theta_s$  of  $v$  relative to  $v_R$  in (a) and (b). Answer in  $[\circ]$  and  $[\text{rad}]$ .

# Exercise 4.4.2 (Answers)

Exercise 4.4.2 (Answers)

# Exercise 4.4.2 (Answers)

(a)  $f = 10[\text{kHz}]$

$$T = \frac{1}{f} = \frac{1}{10000} = 100 [\mu\text{s}]$$

$$\theta_s = \frac{\Delta t}{T} \times 360 [^\circ] = \frac{8.40 [\mu\text{s}]}{100 [\mu\text{s}]} \times 360 [^\circ] = 30.2 [^\circ]$$

$$\theta_s = \frac{\Delta t}{T} \times 2\pi [\text{rad}] = \frac{8.40 [\mu\text{s}]}{100 [\mu\text{s}]} \times 2\pi [\text{rad}] = 0.168\pi [\text{rad}]$$

(b)  $f = 50[\text{kHz}]$

$$T = \frac{1}{f} = \frac{1}{50000} = 20 [\mu\text{s}]$$

$$\theta_s = \frac{\Delta t}{T} \times 360 [^\circ] = \frac{3.97 [\mu\text{s}]}{20 [\mu\text{s}]} \times 360 [^\circ] = 71.5 [^\circ]$$

$$\theta_s = \frac{\Delta t}{T} \times 2\pi [\text{rad}] = \frac{3.97 [\mu\text{s}]}{20 [\mu\text{s}]} \times 2\pi [\text{rad}] = 0.397\pi [\text{rad}]$$

# Exercise 5.1.1 (Homework)

Exercise 5.1.1 (Homework)



# Exercise 5.1 (Homework)

AC current

$$i = I_m \sin \omega t$$

$I_m$ : Amplitude


Show that

$$I_e = \frac{I_m}{\sqrt{2}}$$

$I_e$ : Effective value of AC current

An AC current is expressed with  $i = I_m \sin \omega t$ , where  $I_m$  is the amplitude. Show that the effective value of the AC current  $I_e = I_m/\sqrt{2}$ .

# Exercise 5.1 (Homework)

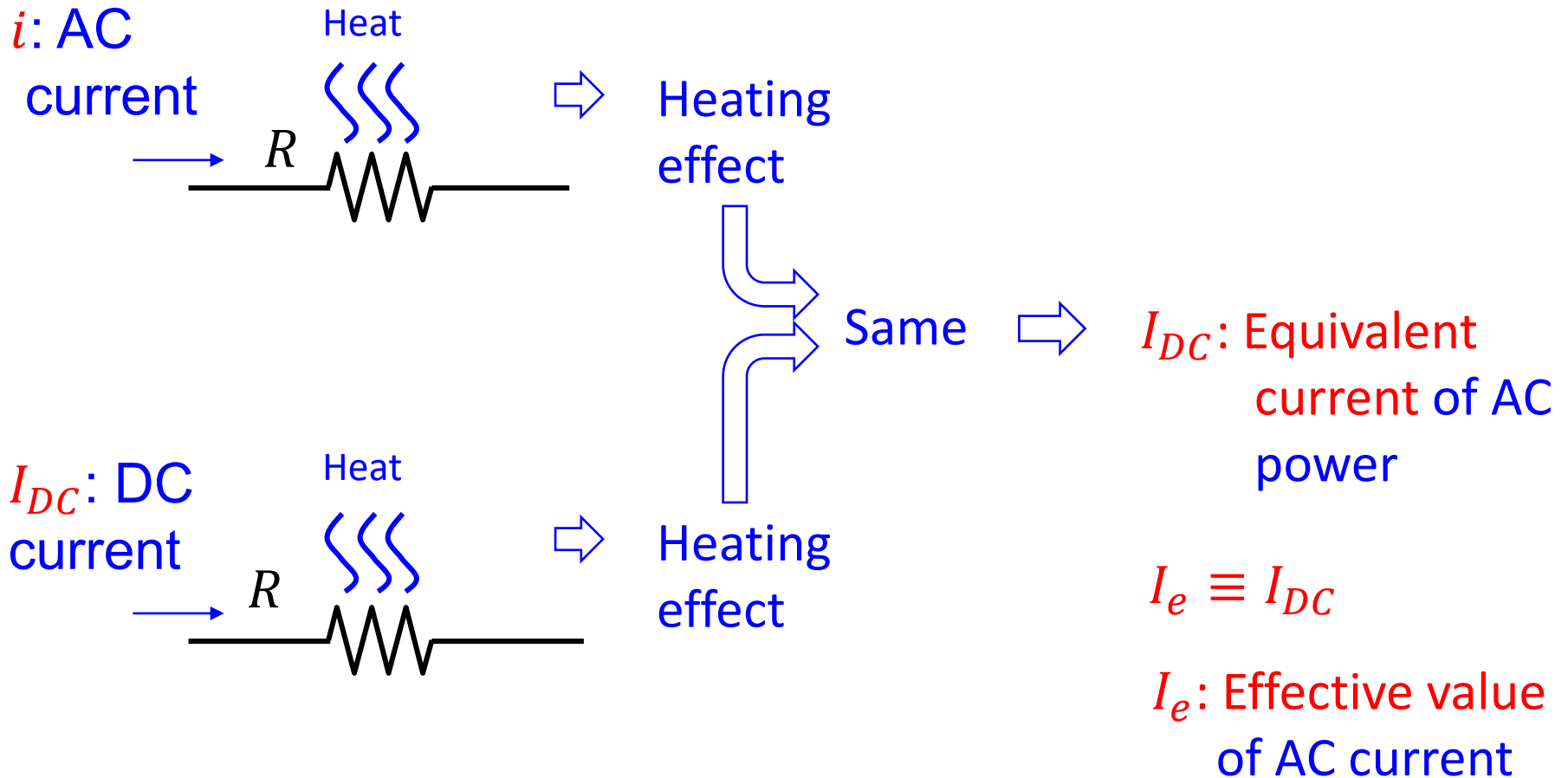


The effective value of AC current is defined as the DC current that gives the same heating effect as the AC current.

# Exercise 5.1 (Answer)

Exercise 5.1 (Answer)

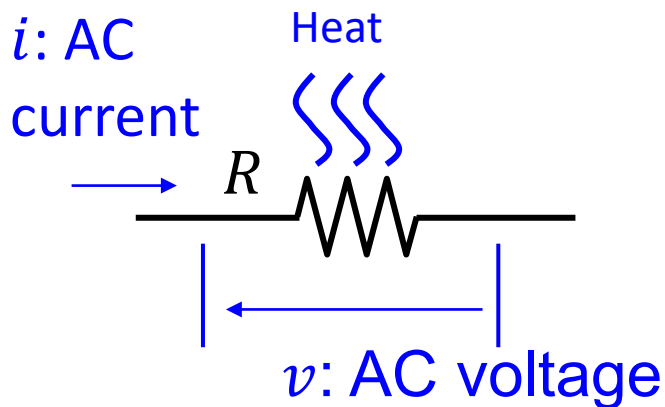
# Exercise 5.1 (Answer)

Heating effect = Average power consumed by the resistor  $P_{ave}$




$$\begin{aligned} P_{ave} &= \frac{1}{T} \int_0^T vi \, dt && \leftarrow v = Ri \\ &= \frac{1}{T} \int_0^T Ri^2 \, dt && \leftarrow i = I_m \sin \omega t \\ &= \frac{RI_m^2}{T} \int_0^T \sin^2 \omega t \, dt && \leftarrow \cos 2\theta = 1 - 2\sin^2 \theta \\ &= \frac{RI_m^2}{T} \int_0^T \frac{1 - \cos 2\omega t}{2} \, dt \\ &= \frac{RI_m^2 T}{T} \frac{1}{2} \\ &= \frac{RI_m^2}{2} \end{aligned}$$


# Exercise 5.1 (Answer)

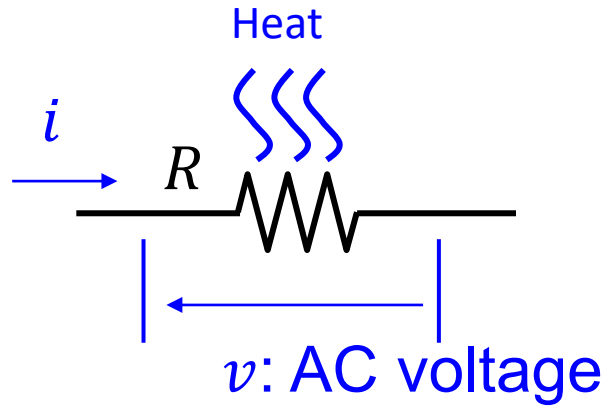


$$P_{ave} = \frac{RI_m^2}{2}$$

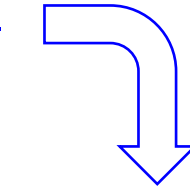
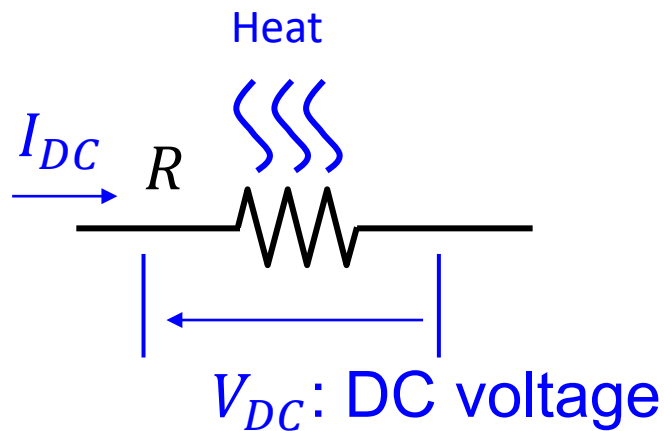
$$RI_{DC}^2 = \frac{RI_m^2}{2} \Rightarrow I_{DC} = \frac{I_m}{\sqrt{2}}$$



$$P_{DC} = RI_{DC}^2$$

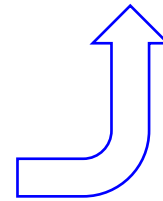


$$\text{III}$$
$$I_e = \frac{I_m}{\sqrt{2}}$$

# Exercise 5.4 (Homework)

Exercise 5.4 (Homework)

# Exercise 5.4 (Homework)

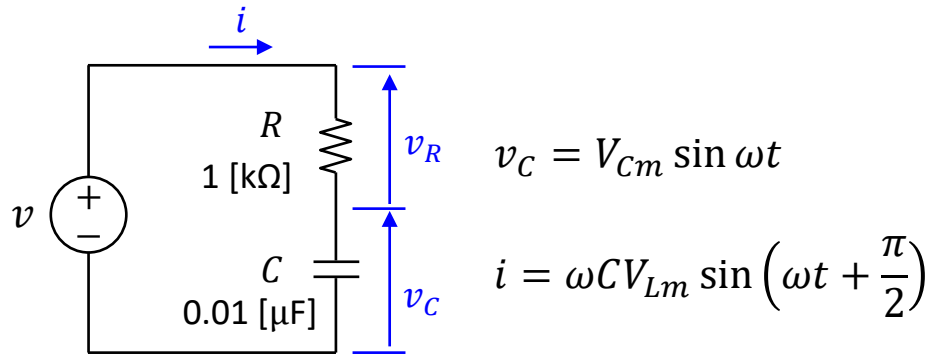


Results in Experiment 5.4.1.  $f = 10$  [kHz].

1. Find  $\omega C$ , where  $C = 0.01$  [ $\mu\text{F}$ ].

2. Find  $I_m$ , if  $V_{Cm} = 3.4$  [V].

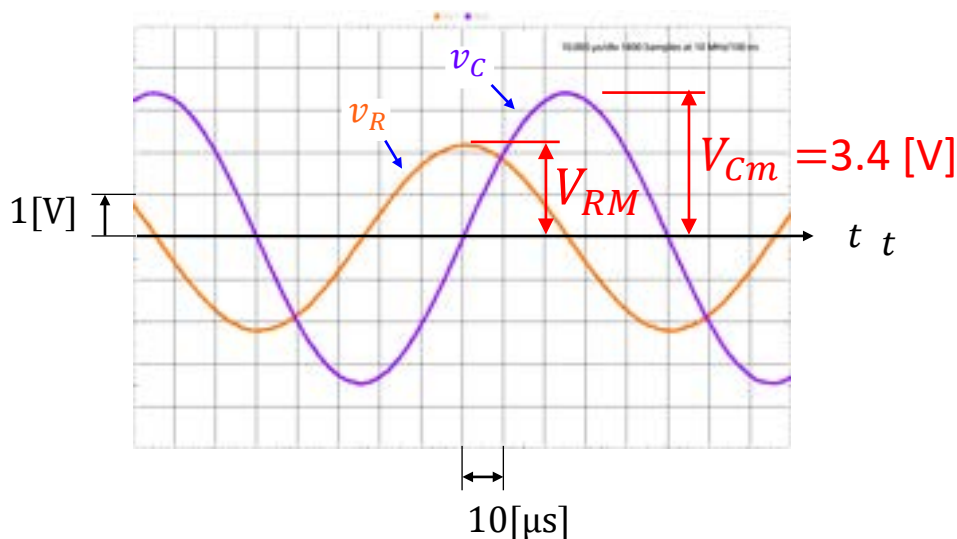3. Find  $V_{Rm}$  using  $I_m$ , and compare it to the reading from  $v_R$ .




You can round the answers to 2 significant figures

# Exercise 5.4 (Answers)

Exercise 5.4 (Answers)



# Exercise 5.4 (Answers)

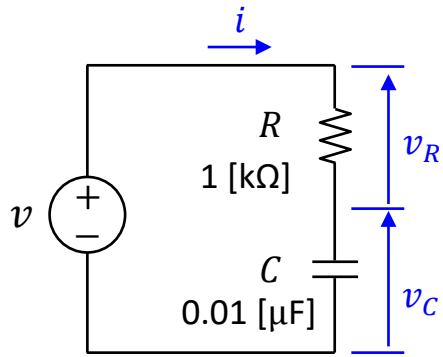


1. Find  $\omega C$ , where  $C = 0.01 \text{ [}\mu\text{F}\text{]}$ .

$$\begin{aligned}\omega C &= 2\pi f C \\ &= 2 \times \pi \times 10 \times 10^3 \text{ [Hz]} \times 0.01 \times 10^{-6} \text{ [F]} \\ &= 6.3 \times 10^{-4} \text{ [}\Omega\text{]}\end{aligned}$$

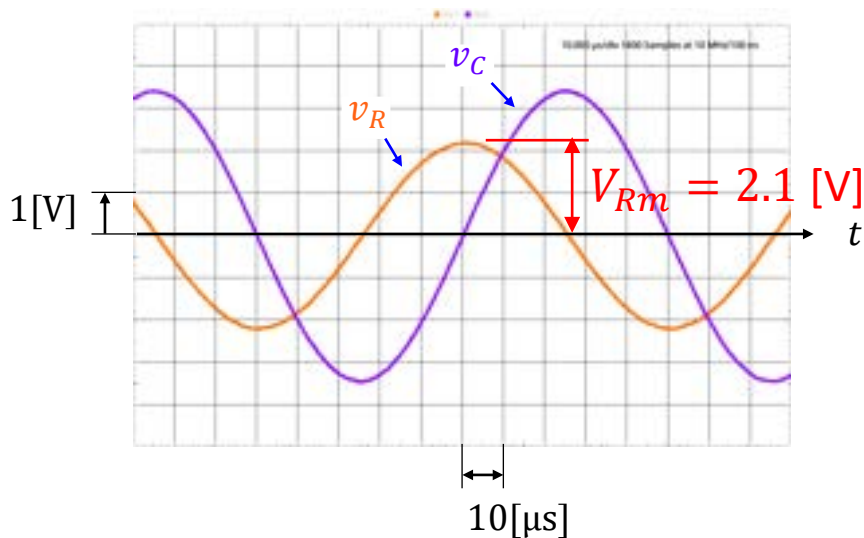2. Find  $I_m$ , if  $V_{Cm} = 3.4 \text{ [V]}$ .

$$I_m = \omega C V_{Cm} = 6.3 \times 10^{-4} \times 3.4 = 2.1 \times 10^{-3} \text{ [A]}$$




3. Find  $V_{Rm}$  using  $I_m$ , and compare it to the reading from  $v_R$ .

$$V_{Rm} = R I_m = 10^3 \text{ [}\Omega\text{]} \times 2.1 \times 10^{-3} \text{ [A]} = 2.1 \text{ [V]}$$

# Exercise 6.6 (Homework)

Exercise 6.6 (Homework)


# Exercise 6.6 (Homework)

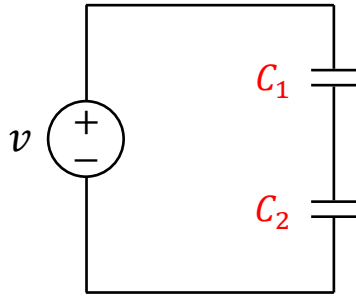

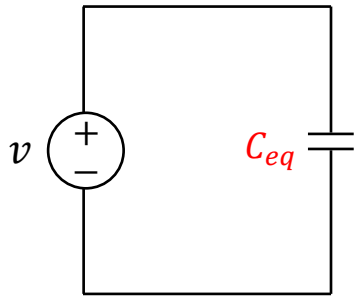(a) Capacitors in series

Show that

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$




(b) Equivalent circuit


# Exercise 6.6 (Answer)

Exercise 6.6 (Answer)

# Exercise 6.6 (Answer)

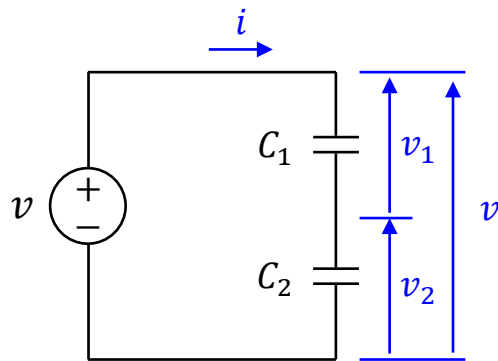

(a) Capacitors in series

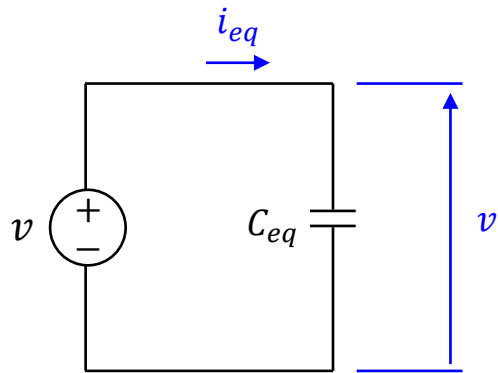

(b) Equivalent circuit

$$v_1 = \frac{1}{C_1} \int i dt, v_2 = \frac{1}{C_2} \int i dt$$

Kirchhoff's voltage Law

$$v = v_1 + v_2$$
$$= \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt$$

$$= \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \int i dt$$

$$v = \frac{1}{C_{eq}} \int i_{eq} dt$$

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$


$C_{eq}$ : Combined capacitance

$C_{eq}$  is obtained as  $1/(1/C_1 + 1/C_2)$ .


# Exercise 6.7 (Homework)

Exercise 6.7 (Homework)

# Exercise 6.7

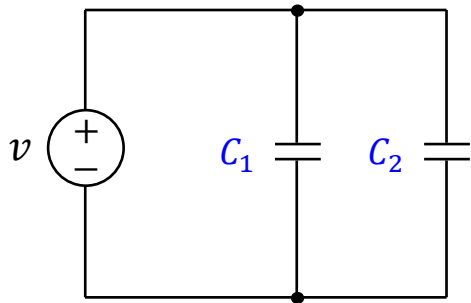

(a) Capacitors in parallel

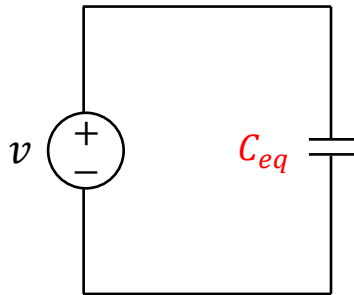

(b) Equivalent circuit

Show that


$$C_{eq} = C_1 + C_2$$

# Exercise 6.7 (Answer)


Exercise 6.7 (Answer)



# Exercise 6.7 (Answer)

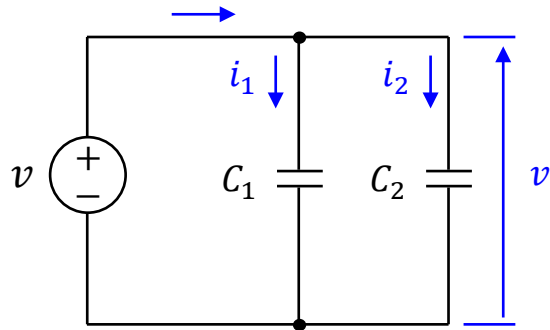

(a) Capacitors in parallel

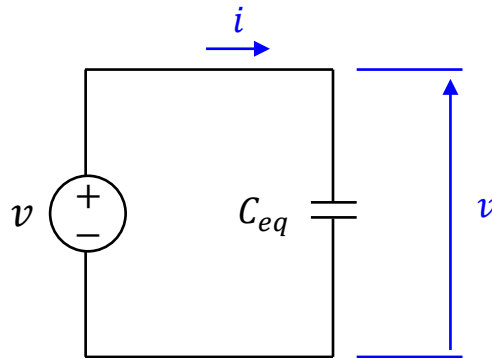

(b) Equivalent circuit

$$i_1 = C_1 \frac{dv}{dt}$$
$$i_2 = C_2 \frac{dv}{dt}$$

Kirchhoff's current Law

$$i = i_1 + i_2$$
$$= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt}$$
$$= (C_1 + C_2) \frac{dv}{dt}$$

$$i = C_{eq} \frac{dv}{dt}$$

$$C_{eq} = C_1 + C_2$$

$C_{eq}$ : Combined Capacitance

# Exercise 7.1 (Homework)

Exercise 7.1 (Homework)

# Exercise 7.1 (Homework)

1.  $Z_1 = \frac{\sqrt{3}}{2} + j\frac{1}{2}, Z_2 = \frac{1}{2} + j\frac{\sqrt{3}}{2}.$

- (1) Convert  $Z_1$  and  $Z_2$  into polar form.
- (2) Find  $Z_1 + Z_2$  in polar form.
- (3) Plot  $Z_1, Z_2,$  and  $Z_1 + Z_2$  in complex plane.

2.  $Z_1 = \frac{1}{\sqrt{2}} + j\frac{1}{\sqrt{2}}, Z_2 = \frac{1}{\sqrt{2}} + j\frac{1}{\sqrt{2}}.$

- (1) Convert  $Z_1$  and  $Z_2$  into polar form.
- (2) Find  $Z_1 \times Z_2$  in polar form.
- (3) Plot  $Z_1, Z_2,$  and  $V_1 \times V_2$  in complex plane.

3.  $Z_1 = \frac{1}{2} + j\frac{\sqrt{3}}{2}, Z_2 = \sqrt{3} + j.$

- (1) Convert  $Z_1$  and  $Z_2$  into polar form.
- (2) Find  $\frac{Z_1}{Z_2}$  in polar form.
- (3) Plot  $Z_1, Z_2,$  and  $\frac{Z_1}{Z_2}$  in complex plane.

# Exercise 7.1 (Answers)

Exercise 7.1 (Answers)

# Exercise 7.1 (Homework)


1.  $Z_1 = \frac{\sqrt{3}}{2} + j\frac{1}{2}$ ,  $Z_2 = \frac{1}{2} + j\frac{\sqrt{3}}{2}$ .

(1)  $Z_1 = \sqrt{(\sqrt{3}/2)^2 + (1/2)^2}(\cos 30^\circ + j \sin 30^\circ) = \cos 30^\circ + j \sin 30^\circ$

$Z_2 = \sqrt{(1/2)^2 + (\sqrt{3}/2)^2}(\cos 60^\circ + j \sin 60^\circ) = \cos 60^\circ + j \sin 60^\circ$

(2)  $Z_1 + Z_2 = \frac{1}{2} + \frac{\sqrt{3}}{2} + j\left(\frac{1}{2} + \frac{\sqrt{3}}{2}\right) = \left(\frac{1}{2} + \frac{\sqrt{3}}{2}\right)(1 + j) = \sqrt{2}\left(\frac{1}{2} + \frac{\sqrt{3}}{2}\right)(\cos 45^\circ + j \sin 45^\circ)$

(3)

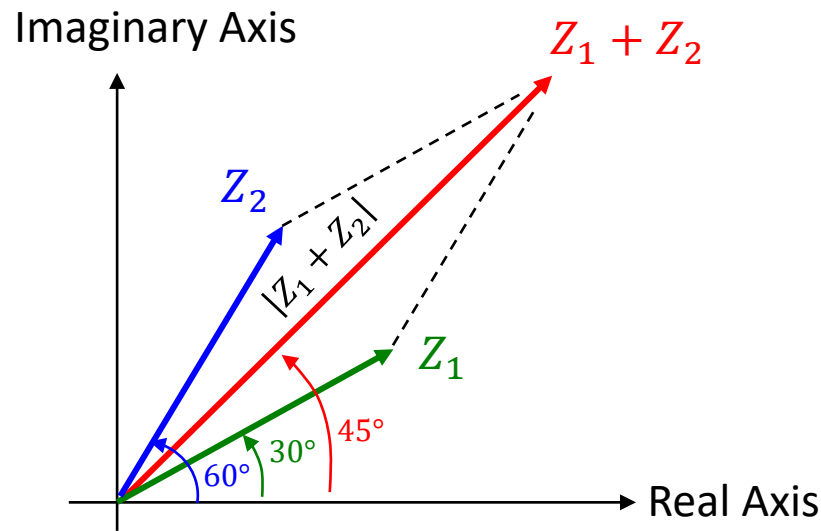


# Exercise 7.1 (Homework)

$$2. Z_1 = \frac{1}{\sqrt{2}} + j\frac{1}{\sqrt{2}}, Z_2 = \frac{1}{\sqrt{2}} + j\frac{1}{\sqrt{2}}$$

$$(1) Z_1 = Z_2 = \sqrt{\left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2} (\cos 45^\circ + j \sin 45^\circ) = \cos 45^\circ + j \sin 45^\circ$$

$$(2) Z_1 \times Z_2 = \left(\frac{1}{\sqrt{2}} + j\frac{1}{\sqrt{2}}\right) \times \left(\frac{1}{\sqrt{2}} + j\frac{1}{\sqrt{2}}\right) = \frac{1}{2} - \frac{1}{2} + j\left(\frac{1}{2} + \frac{1}{2}\right) = j = \cos 90^\circ + j \sin 90^\circ$$

(3)

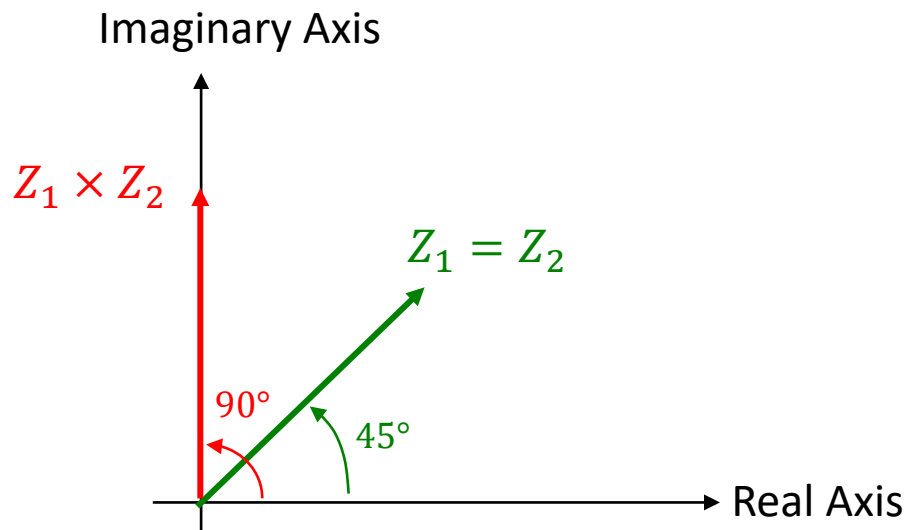


# Exercise 7.1 (Homework)

3.  $Z_1 = \frac{1}{2} + j\frac{\sqrt{3}}{2}$ ,  $Z_2 = \sqrt{3} + j$ .

(1)  $Z_1 = \cos 60^\circ + j \sin 60^\circ$ ,  $Z_2 = 2(\cos 30^\circ + j \sin 30^\circ)$

(2)  $\frac{Z_1}{Z_2} = \frac{\frac{1}{2} + j\frac{\sqrt{3}}{2}}{\sqrt{3} + j} = \frac{\left(\frac{1}{2} + j\frac{\sqrt{3}}{2}\right)(\sqrt{3} - j)}{(\sqrt{3} + j)(\sqrt{3} - j)} = \frac{\frac{\sqrt{3}}{2} + \frac{\sqrt{3}}{2} + j\left(\frac{3}{2} - \frac{1}{2}\right)}{3 + 1} = \frac{1}{2}\left(\frac{\sqrt{3}}{2} + j\frac{1}{2}\right) = \frac{1}{2}(\cos 30^\circ + j \sin 30^\circ)$

(3)

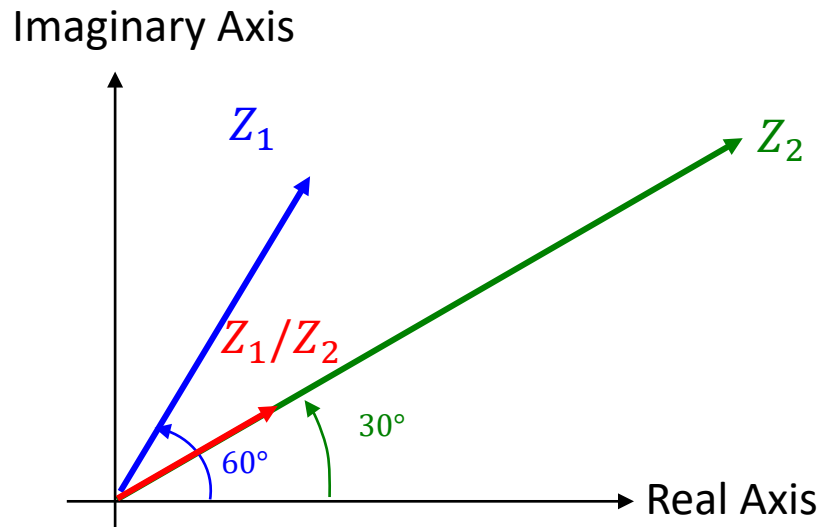


# Exercise 7.4 (Homework)

Exercise 7.4 (Homework)



# Exercise 7.4 (Homework)

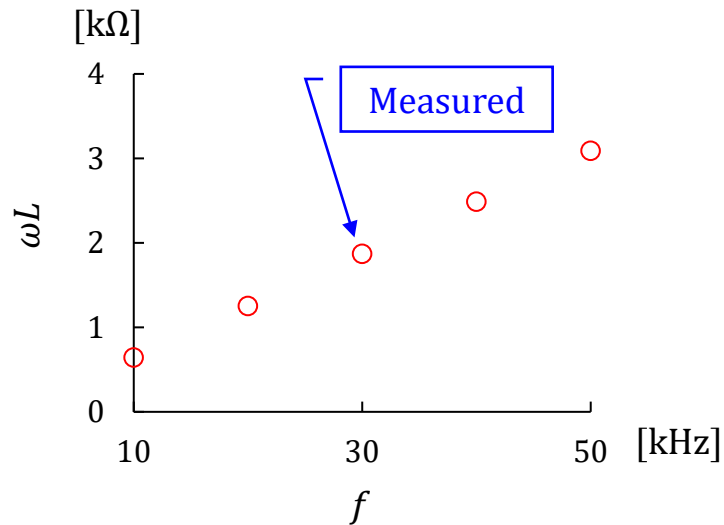

Inductive Reactance

$$L = 10 \text{ [mH]}$$

1. Calculate  $\omega L$  at  $f = 10, 20, 30, 40, 50$  [kHz].
2. Draw a line of  $\omega L$ .

# Exercise 7.4 (Answers)

Exercise 7.4 (Answers)


# Exercise 7.4 (Answers)

$$f = 10 \text{ [kHz]}$$

$$\omega L = 2\pi fL = 2 \times \pi \times 10^4 \text{ [Hz]} \times 0.01 \text{ [H]} = 628 \text{ [\Omega]}$$

Nominal values of  $\omega L$

$f$ [kHz]	$\omega L$ [k $\Omega$ ]
10	0.63
20	1.26
30	1.88
40	2.51
50	3.14

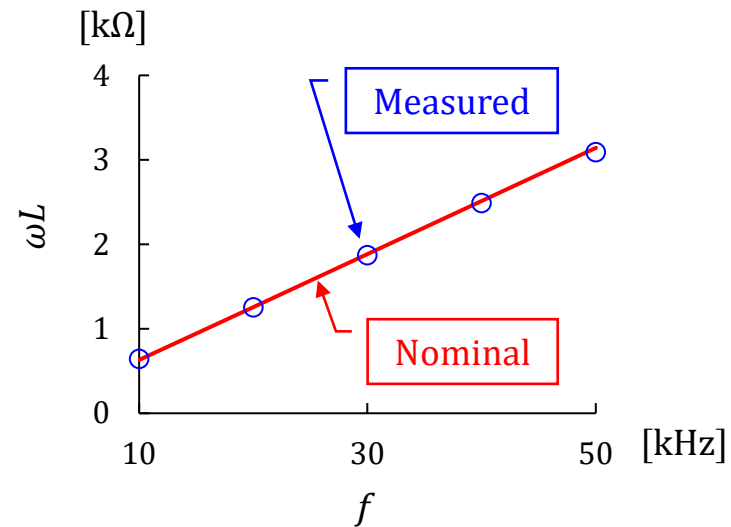


Inductive Reactance

# Exercise 7.5 (Homework)

Exercise 7.5 (Homework)

# Exercise 7.5 (Homework)

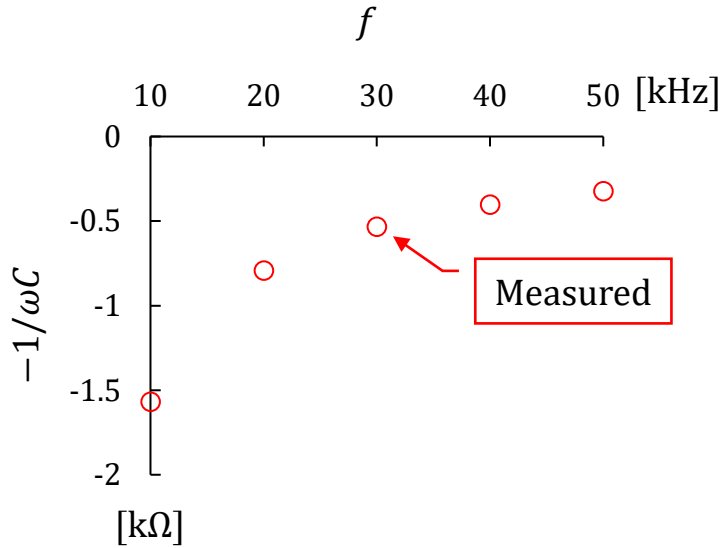

Capacitive Reactance

The nominal value of capacitance  $C = 0.01$  [ $\mu\text{F}$ ]

1. Calculate the nominal values of capacitive reactance  $-1/\omega C$  at  $f = 10, 20, 30, 40, 50$  [kHz].
2. Draw a line that interpolates the nominal values of  $-1/\omega C$ .

# Exercise 7.5 (Answers)

Exercise 7.5 (Answers)


# Experiment 7.5 (Answer)

$$f = 10 \text{ [kHz]}$$

$$-\frac{1}{\omega C} = -\frac{1}{2 \times \pi \times 10^4 \text{ [Hz]} \times 0.01 \times 10^{-6} \text{ [F]}} = -1.59 \text{ [k}\Omega\text{]}$$

Nominal Values of  $-1/\omega C$

$f$ [kHz]	$-1/\omega C$ [k $\Omega$ ]
10	-1.59
20	-0.796
30	-0.531
40	-0.398
50	-0.318

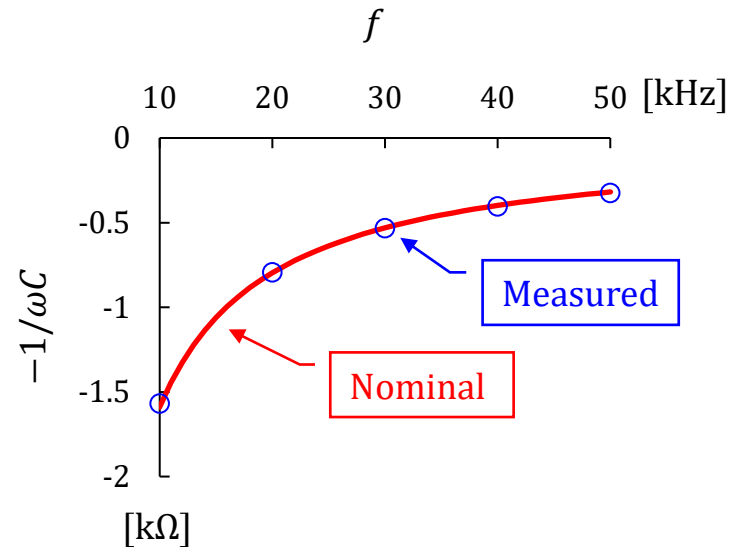


Capacitive Reactance

# Exercise 8.5.1 (Homework)

Exercise 8.5.1 (Homework)



# Exercise 8.5.1 (Homework)

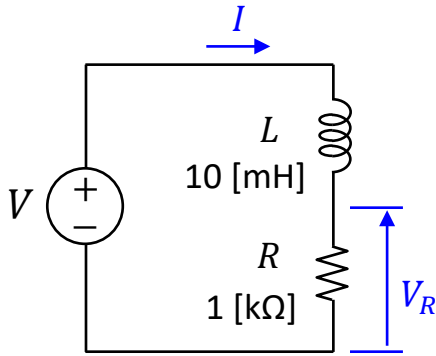

$$Z = |Z|(\cos \psi + j \sin \psi)$$

$$|Z| = \sqrt{R^2 + (\omega L)^2} \quad \psi = \tan^{-1} \frac{\omega L}{R}$$

If  $V = V_e(\cos \theta + j \sin \theta)$ , then

$$\begin{aligned} I &= \frac{V}{Z} \\ &= \frac{V_e(\cos \theta + j \sin \theta)}{|Z|(\cos \psi + j \sin \psi)} \quad \leftarrow \text{Eq. (7.4)} \\ &= \frac{V_e}{|Z|} \{\cos(\theta - \psi) + j \sin(\theta - \psi)\} \end{aligned}$$

If  $f = 10 \text{ [kHz]}$ ,  $V_e = 2.96 \text{ [V]}$ , then  $V_{Re} = ?$

If  $f = 10 \text{ [kHz]}$ ,  $V_e = 2.96 \text{ [V]}$  as in Experiment 8.5, then what is  $V_{Re}$ ?

# Exercise 8.5.1 (Answer)

Exercise 8.5.1 (Answer)

# Exercise 8.5.1 (Answer)

$$\begin{aligned}V_R &= RI \\&= R \frac{V}{Z} \\&= R \frac{V_e}{|Z|} \{\cos(\theta - \psi) + j \sin(\theta - \psi)\}\end{aligned}$$


$$\begin{aligned}V_{Re} &= R \frac{V_e}{|Z|} \\&= R \frac{V_e}{\sqrt{R^2 + (\omega L)^2}} \\&= 10^3 [\Omega] \times \frac{2.96 [\text{V}]}{\sqrt{(10^3 [\Omega])^2 + (2 \times \pi \times 10^4 [\text{Hz}] \times 0.01 [\text{H}])^2}} \\&= 2.51 [\text{V}]\end{aligned}$$

The result in Experiment 8.5 was that  $V_{Re} = 2.40 [\text{V}]$  at  $f = 10 [\text{kHz}]$ . This means that the amount of actual current is smaller than the nominal value. This is because the magnitude of actual impedance was larger than the nominal value.

# Exercise 8.10 (Homework)

Exercise 8.10 (Homework)

# Exercise 8.10 (Homework)

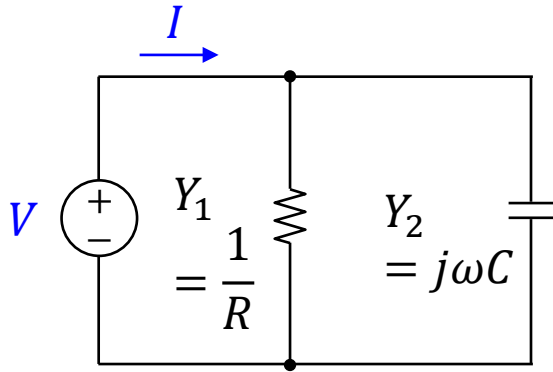

This is an  $R - C$  parallel circuit. The admittance of the capacitor is  $j\omega C$ , and that of the resistor is  $1/R$ .


1. Write the composite admittance  $Y$  of this circuit in the polar form.
2. If  $R = 1$  [ $k\Omega$ ],  $C = 0.01$  [ $\mu\text{F}$ ], and  $f = 15.9$  [ $\text{kHz}$ ], find the admittance  $Y$  in the polar form.

You can round the answer to 2 significant figures.

# Exercise 8.10 (Answers)

Exercise 8.10 (Answers)

# Exercise 8.10 (Answers)

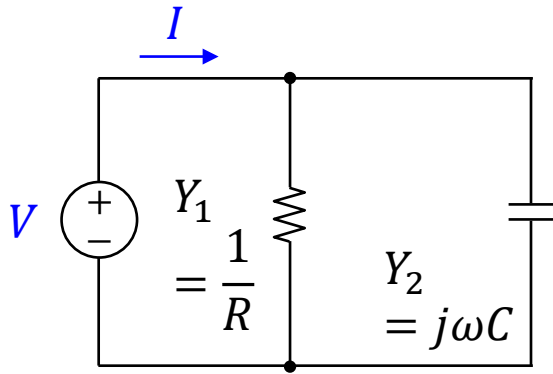

1. Composite Admittance

$$Y = Y_1 + Y_2 = \frac{1}{R} + j\omega C = |Y|(\cos \varphi + j \sin \varphi)$$

$$|Y| = \sqrt{\left(\frac{1}{R}\right)^2 + (\omega C)^2} \quad \varphi = \tan^{-1} \omega CR$$

2.  $R = 1$  [k $\Omega$ ],  $C = 0.01$  [ $\mu$ F], and  $f = 15.9$  [kHz]

$$\begin{aligned} |Y| &= \sqrt{\left(\frac{1}{1000}\right)^2 + (2 \times \pi \times 15.9 \times 10^3 \times 0.01 \times 10^{-6})^2} = \sqrt{(10^{-3})^2 + (1.0 \times 10^{-3})^2} \\ &= 1.4 \times 10^{-3} \end{aligned}$$

$$\psi = \tan^{-1} 2 \times \pi \times 15.9 \times 10^3 \times 0.01 \times 10^{-6} \times 10^3 = \tan^{-1} 1.0 = 45^\circ$$



$$Y = 1.4(\cos 45^\circ + j \sin 45^\circ) \text{ [mS]}$$

# Exercise 9.3 (Homework)

## Exercise 9.3 (Homework)



# Exercise 9.3

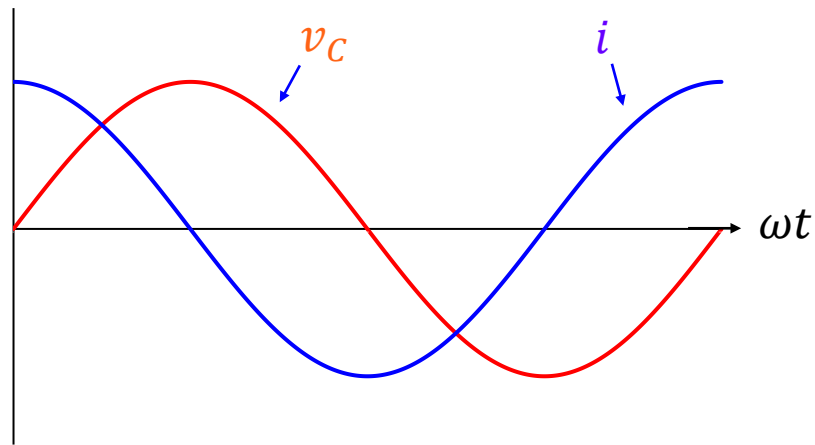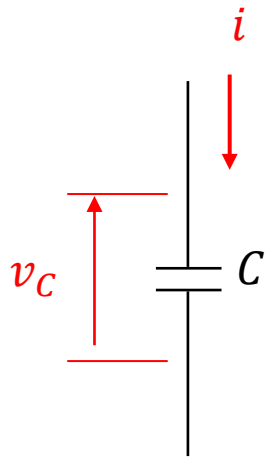

1. The voltage  $v_C$  and the current  $i$  are given by

$$v_C = \sqrt{2}V_{Ce} \sin \omega t$$

$$i = \sqrt{2}I_e \cos \omega t.$$

Develop the power  $p = v_C i$ .



2. Draw the waveform of  $p$ .
3. Find the average power of  $p$ .
4. The amplitude of  $p$  is denoted by  $P_{Cm}$  and  $P_{Cm} = V_{Ce} I_e$ . The unit of  $P_{Cm}$  is [Var]. Show that  $P_{Cm}$  is

$$\begin{aligned} P_{Cm} &= \frac{I_e^2}{\omega C} \\ &= \omega C V_{Ce}^2 \end{aligned}$$

# Exercise 9.3 (Homework)

Exercise 9.3 (Homework)

# Exercise 9.3

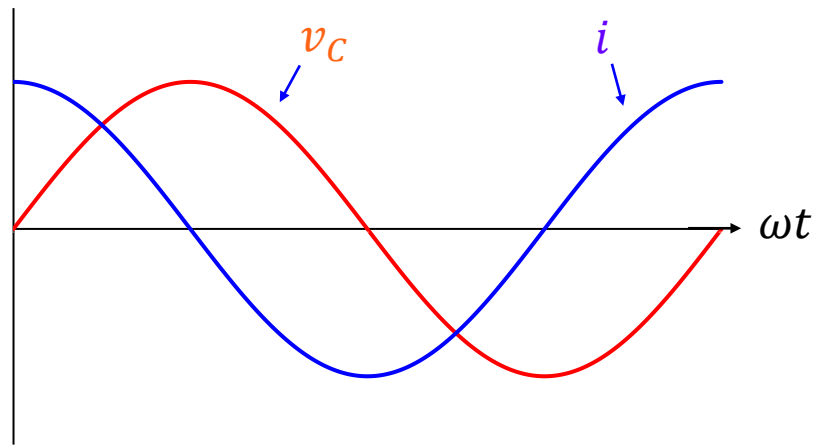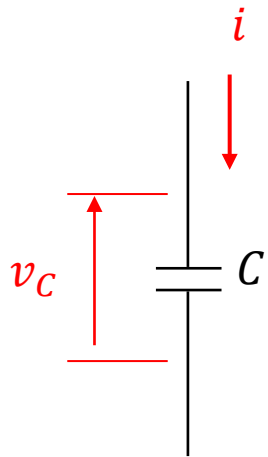

1. The voltage  $v_C$  and the current  $i$  are given by

$$v_C = \sqrt{2}V_{Ce} \sin \omega t$$

$$i = \sqrt{2}I_e \cos \omega t.$$

Develop the power  $p = v_C i$ .


2. Draw the waveform of  $p$ .
3. Find the average power of  $p$ .
4. The amplitude of  $p$  is denoted by  $P_{Cm}$  and  $P_{Cm} = V_{Ce} I_e$ . The unit of  $P_{Cm}$  is [Var]. Show that  $P_{Cm}$  is

$$\begin{aligned} P_{Cm} &= \frac{I_e^2}{\omega C} \\ &= \omega C V_{Ce}^2 \end{aligned}$$

# Exercise 9.3 (Answer)

Exercise 9.3 (Answer)

# Exercise 9.3 (Answer)

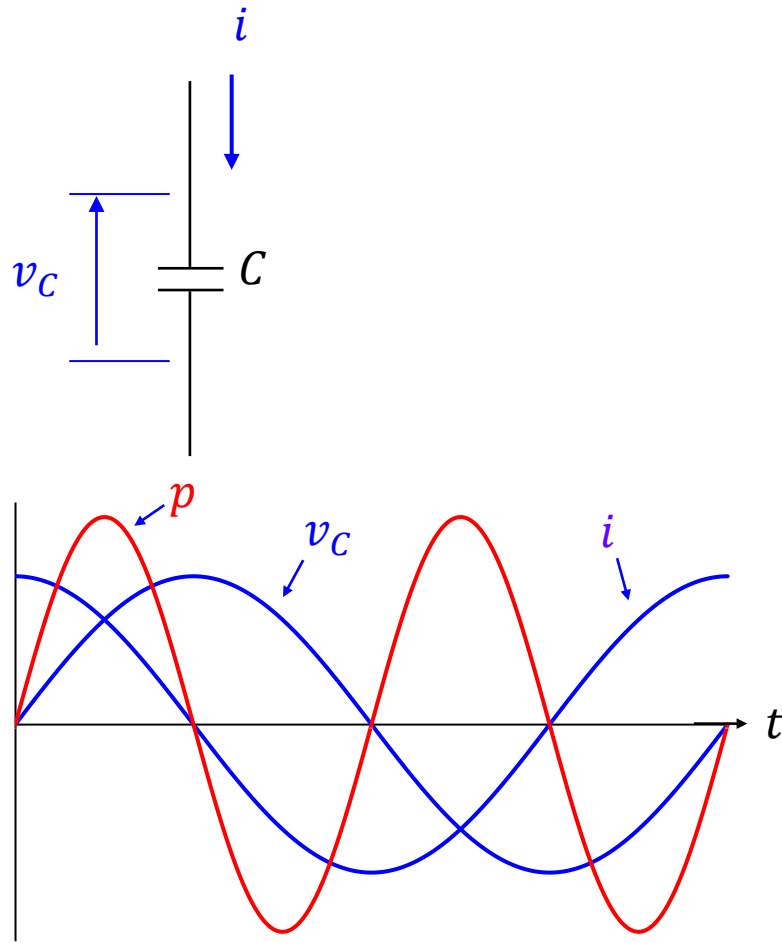

1.

$$\begin{aligned} p &= v_C i \\ &= \sqrt{2}V_{Ce} \sin \omega t \times \sqrt{2}I_e \cos \omega t \\ &= 2V_{Ce}I_e \sin \omega t \cos \omega t \\ &= V_{Ce}I_e \sin 2\omega t \end{aligned}$$

3.

$$\begin{aligned} P_C &= \frac{1}{2\pi} \int_0^{2\pi} p d\omega t \\ &= \frac{1}{2\pi} \int_0^{2\pi} V_{Ce}I_e \sin 2\omega t d\omega t \\ &= 0 \end{aligned}$$


4.

$$\begin{aligned} P_{Cm} &= V_{Ce}I_e \leftarrow V_C = \frac{I_e}{\omega C} \\ &= \frac{I_e^2}{\omega C} \leftarrow I_e = \omega C V_{Ce} \\ &= \omega C V_{Ce}^2 \end{aligned}$$


# Exercise 9.6.1 (Homework)

Exercise 9.6.1 (Homework)

# Exercise 9.6.1 (Homework)

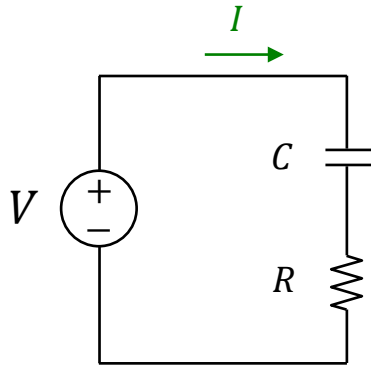
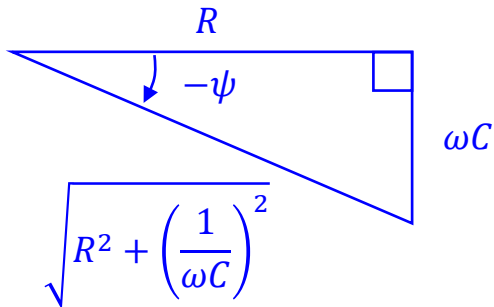
$$\psi = -\tan^{-1} \frac{1}{\omega CR}$$




$$\cos \psi = \frac{R}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}}$$

$$\sin \psi = -\frac{\frac{1}{\omega C}}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}}$$

In the case of  $R - C$  series circuit,  $\cos \psi$  and  $\sin \psi$  are given by these equations.

# Exercise 9.6.1 (Homework)

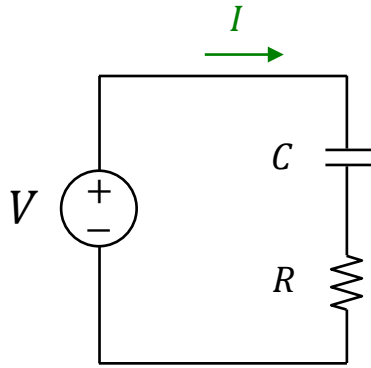

Show that the active power  $P_{act}$  and the reactive power  $P_r$  are given by the following equations:

$$P_{act} = \left\{ \begin{array}{l} RI_e^2 \\ \frac{R}{R^2 + (1/\omega C)^2} V_e^2 \end{array} \right.$$


$$P_r = \left\{ \begin{array}{l} -(1/\omega C)I_e^2 \\ -\frac{1/\omega C}{R^2 + (1/\omega C)^2} V_e^2 \end{array} \right.$$



# Exercise 9.6.1 (Answers)

Exercise 9.6.1 (Answers)

# Exercise 9.6.1 (Answers)

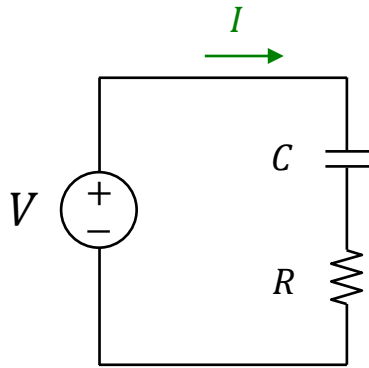

$$P_{act} = V_e I_e \cos \psi$$

$$\leftarrow \cos \psi = \frac{R}{\sqrt{R^2 + (1/\omega C)^2}}$$

$$= V_e I_e \frac{R}{\sqrt{R^2 + (1/\omega C)^2}}$$

$$\leftarrow V_e = \sqrt{R^2 + (1/\omega C)^2} I_e$$

$$= R I_e^2$$

$$\leftarrow I_e = \frac{V_e}{\sqrt{R^2 + (1/\omega C)^2}}$$

$$= \frac{R}{R^2 + (1/\omega C)^2} V_e^2$$

$$P_r = V_e I_e \sin \psi$$

$$\leftarrow \sin \psi = -\frac{1/\omega C}{\sqrt{R^2 + (1/\omega C)^2}}$$

$$= -V_e I_e \frac{1/\omega C}{\sqrt{R^2 + (1/\omega C)^2}}$$


$$= \begin{cases} -(1/\omega C) I_e^2 \\ -\frac{1/\omega C}{R^2 + (1/\omega C)^2} V_e^2 \end{cases}$$

# Exercise 9.6.2 (Homework)

Exercise 9.6.2 (Homework)

# Exercise 9.6.2 (Homework)

Measured values in Experiment 9.6.1

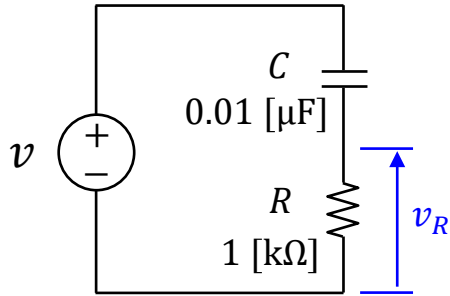


$f$ [kHz]	$P_{act}/V_e^2$ (Measured)	$P_r/V_e^2$ (Measured)
10	0.293	-0.450
20	0.613	-0.482
30	0.773	-0.412
40	0.856	-0.347
50	0.898	-0.296


Nominal values:

$$\frac{P_{act}}{V_e^2} = \frac{R}{R^2 + (1/\omega C)^2}$$
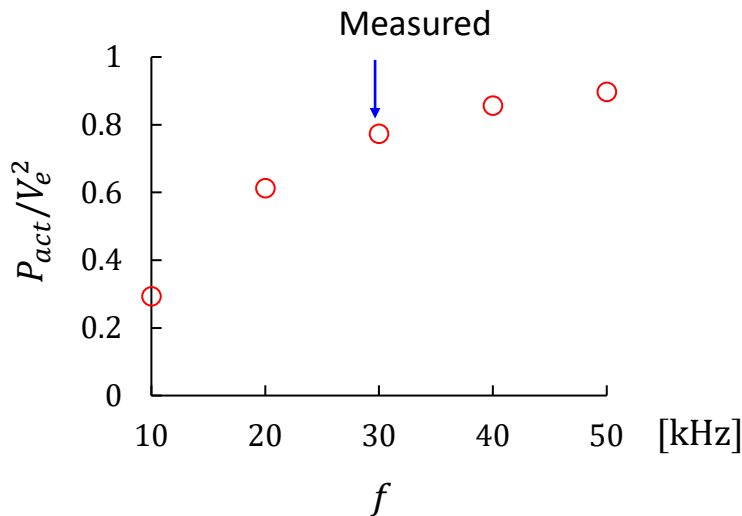
$$\frac{P_r}{V_e^2} = -\frac{1/\omega C}{R^2 + (1/\omega C)^2}$$



(a) Active Power

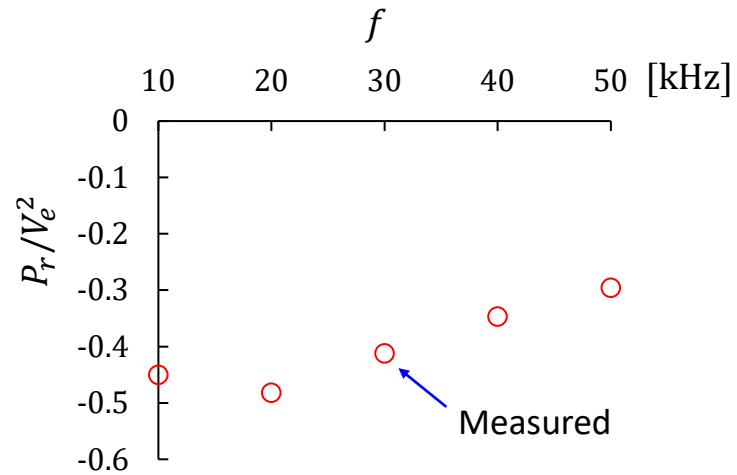


(b) Reactive Power

Find the nominal values of  $P_{act}/V_e^2$  and  $P_r/V_e^2$  using these equations. Then compare the measured values to the nominal ones.

## Exercise 9.6.2 (Answers)

Exercise 9.6.2 (Answers)

# Exercise 9.6.2 (Answers)

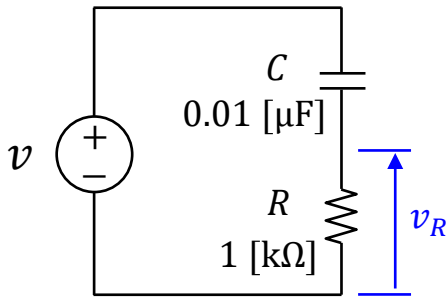

$$f = 10 \text{ [kHz]}$$


$$\begin{aligned} \frac{P_{act}}{V_e^2} &= \frac{R}{R^2 + (1/\omega C)^2} \\ &= \frac{1000[\Omega]}{1000^2 + (1/(2 \times \pi \times 10^4[\text{Hz}] \times 0.01 \times 10^{-6}[\text{F}]))^2} \\ &= 0.283 \end{aligned}$$

$$\begin{aligned} \frac{P_r}{V_e^2} &= -\frac{1/\omega C}{R^2 + (1/\omega C)^2} \\ &= -\frac{1/(2 \times \pi \times 10^4 \times 0.01 \times 10^{-6})}{1000^2 + (1/(2 \times \pi \times 10^4 \times 0.01 \times 10^{-6}))^2} \\ &= 0.450 \end{aligned}$$


$f$ [kHz]	$P_{act}/V_e^2$ (Measured)	$P_{act}/V_e^2$ (Nominal)	$P_r/V_e^2$ (Measured)	$P_r/V_e^2$ (Nominal)
10	0.293	0.283	-0.450	-0.450
20	0.613	0.612	-0.482	-0.487
30	0.773	0.780	-0.412	-0.414
40	0.856	0.863	-0.347	-0.344
50	0.898	0.908	-0.296	-0.289

These equations show examples of the calculation at  $f = 10$  [kHz]. The table shows the results.


# Exercise 9.6.2 (Answers)

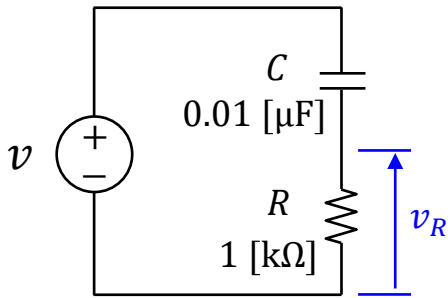

$f$ [kHz]	$P_{act}/V_e^2$ (Measured)	$P_{act}/V_e^2$ (Nominal)	$P_r/V_e^2$ (Measured)	$P_r/V_e^2$ (Nominal)
10	0.293	0.283	-0.450	-0.450
20	0.613	0.612	-0.482	-0.487
30	0.773	0.780	-0.412	-0.414
40	0.856	0.863	-0.347	-0.344
50	0.898	0.908	-0.296	-0.289

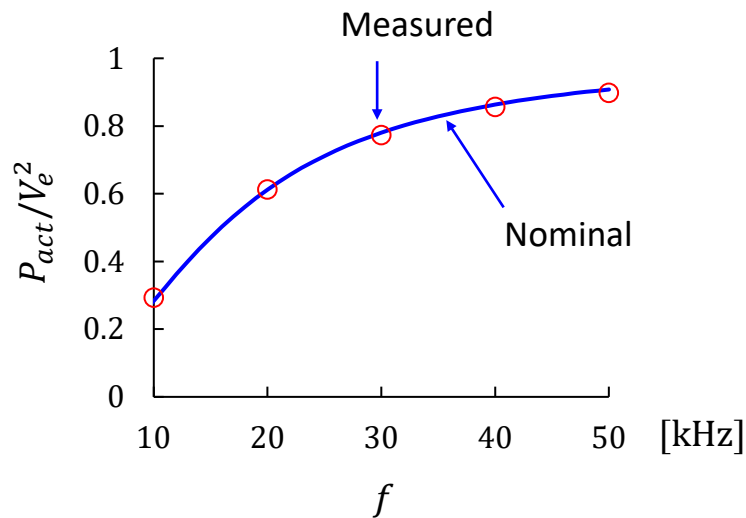

(a) Active Power

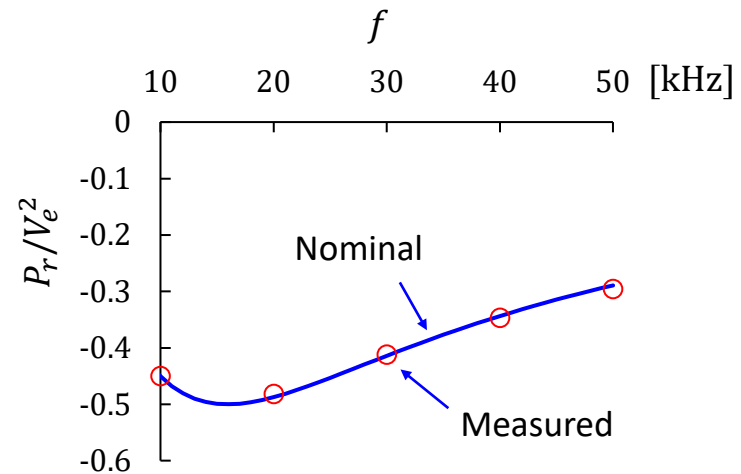

(b) Reactive Power


The measured values met the nominal values well. The resistance component of the capacitor was small.

# Exercise 10.1.2 (Homework)


Exercise 10.1.2 (Homework)



# Exercise 10.1.2 (Homework)

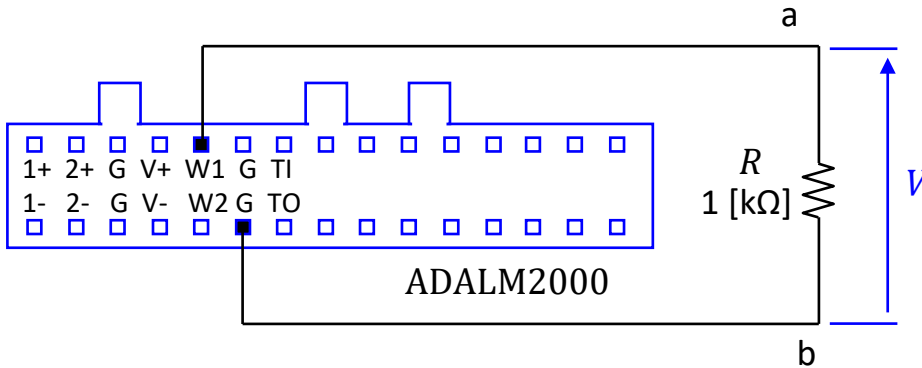

(a) Experimental circuit

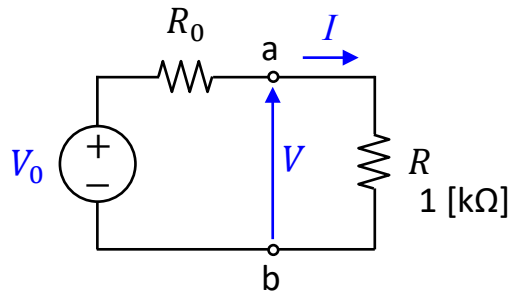

(b) Equivalent Circuit of Signal Generator


This exercise is to find the internal resistor  $R_0$  of the Signal Generator(SG). (a) shows an experimental circuit to measure  $R_0$ . (b) shows its equivalent circuit. The SG is represented by a practical voltage source having the source voltage  $V_0$ , and the internal resistance  $R_0$ . Assume that the measured effective values of  $V_0$  and  $V$  were

$V_{0e}$ [V]	$V_e$ [V]
2.85	2.71

1. Find the internal resistance  $R_0$ .

Pause the video and find the internal resistance  $R_0$  of the signal generator.

# Exercise 10.1.2 (Homework)

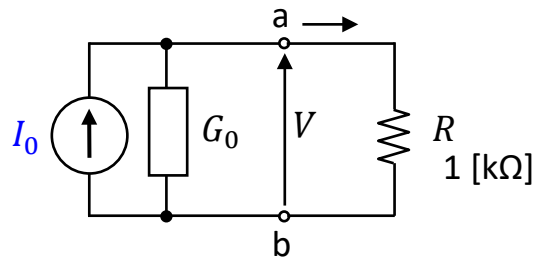

(c) Equivalent Circuit

(c) shows another equivalent circuit of the SG. This circuit employs the current source  $I_0$  and the internal conductance  $G_0$ .


2. Find the current source  $I_0$ , and internal conductance  $G_0$ .

Pause the video and find the current source  $I_0$ , and internal conductance  $G_0$ .

# Exercise 10.1.2 (Answers)

Exercise 10.1.2 (Answers)


# Exercise 10.1.2 (Answers)

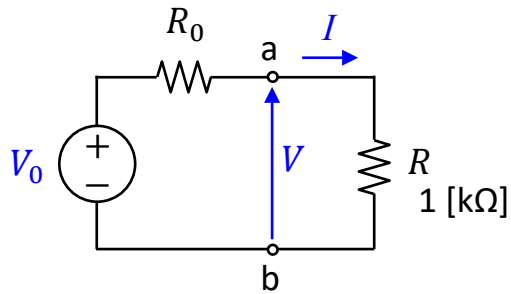

$$I = \frac{V_0}{R_0 + R}$$

$$V = RI$$
$$= \frac{R}{R_0 + R} V_0$$
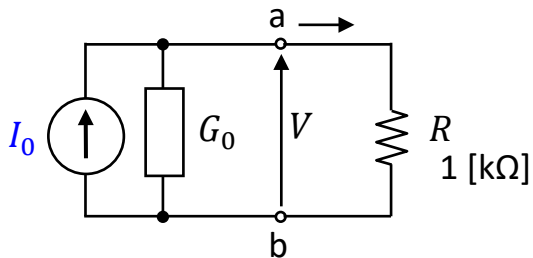
$$\rightarrow R_0 = \frac{1 - \frac{V}{V_0}}{\frac{V}{V_0}} R$$
$$= \frac{1 - \frac{2.71}{2.85}}{\frac{2.71}{2.85}} \times 1000$$
$$= 51.7 \text{ [}\Omega\text{]}$$




$$I_0 = \frac{V_0}{R_0} = \frac{2.86 \text{ [V]}}{51.7 \text{ [}\Omega\text{]}} = 55.3 \text{ [mA]}$$

$$G_0 = \frac{1}{R_0} = \frac{1}{51.7 \text{ [}\Omega\text{]}} = 19.3 \text{ [mS]}$$

# Exercise 10.2 (Homework)

Exercise 10.2 (Homework)

# Exercise 10.2 (Homework)

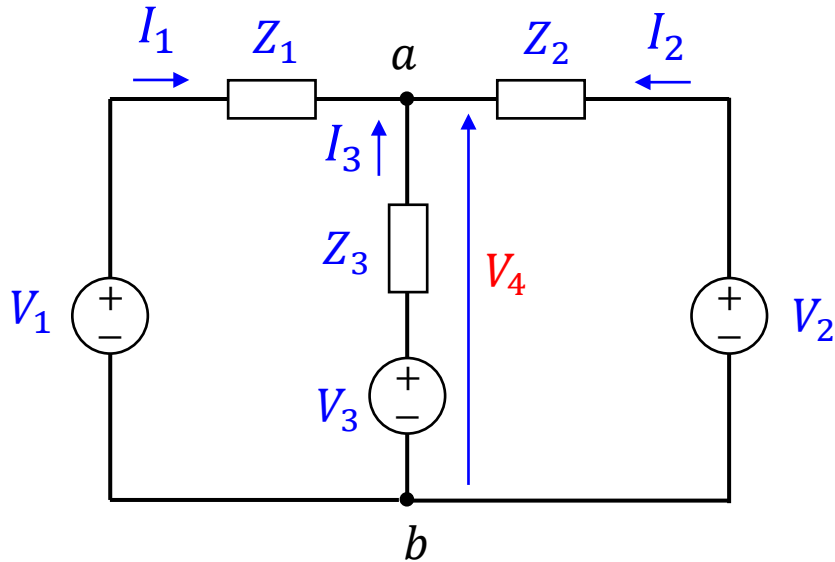


Derive  $V_4$  as a function of  $Z_1$ ,  $Z_2$ ,  $Z_3$ ,  $V_1$ ,  $V_2$  and  $V_3$ .

Derive  $V_4$  as a function of  $Z_1$ ,  $Z_2$ ,  $Z_3$ ,  $V_1$ ,  $V_2$  and  $V_3$ , by applying the Node Voltage Method.

# Exercise 10.2 (Answer)

Exercise 10.2 (Answer)

# Exercise 10.2 (Answer)

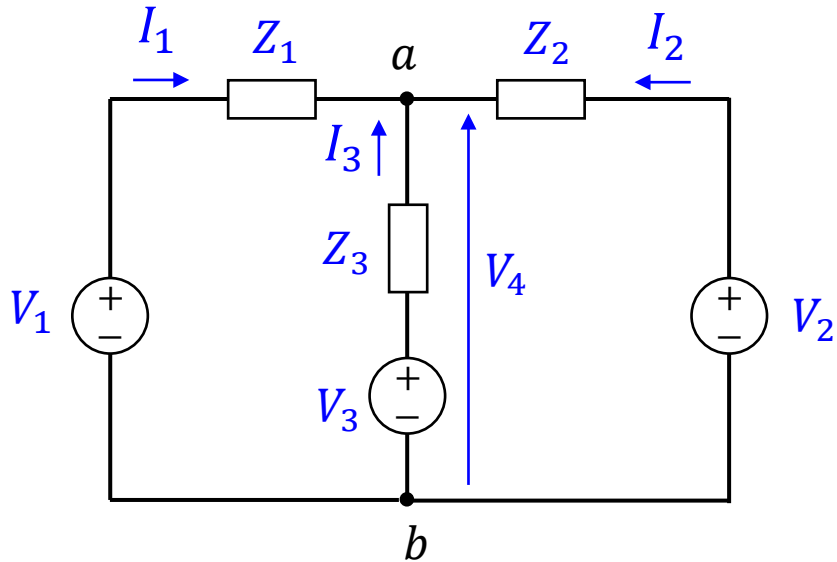

$$I_1 = \frac{V_1 - V_4}{Z_1}$$

$$I_2 = \frac{V_2 - V_4}{Z_2}$$

$$I_3 = \frac{V_3 - V_4}{Z_3}$$

KCL

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_1 - V_4}{Z_1} + \frac{V_2 - V_4}{Z_2} + \frac{V_3 - V_4}{Z_3} = 0$$


$$V_4 = \frac{\frac{V_1}{Z_1} + \frac{V_2}{Z_2} + \frac{V_3}{Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$



## Exercise 10.3.2 (Homework)

Exercise 10.3.2 (Homework)

# Exercise 10.3.2 (Homework)

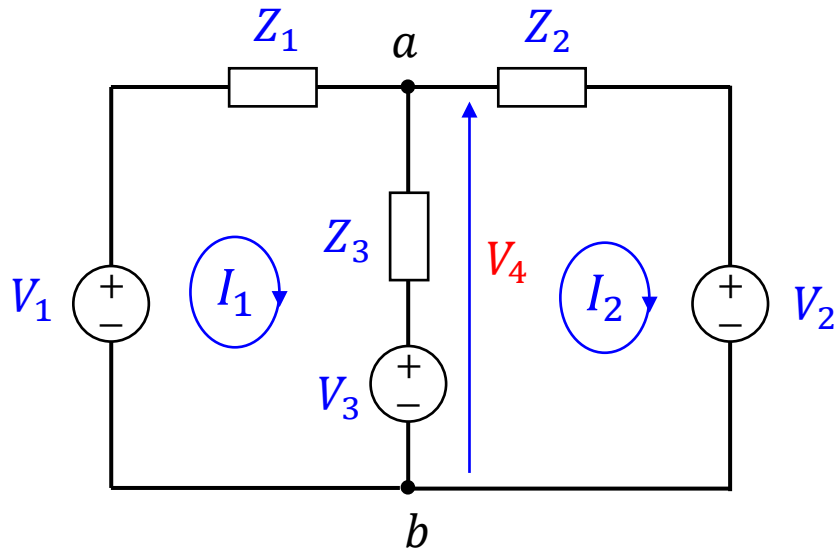


Derive  $V_4$  as a function of  $Z_1$ ,  $Z_2$ ,  $Z_3$ ,  $V_1$ ,  $V_2$  and  $V_3$ .

Derive  $V_4$  as a function of  $Z_1$ ,  $Z_2$ ,  $Z_3$ ,  $V_1$ ,  $V_2$  and  $V_3$ , by applying the Mesh Current Method.

# Exercise 10.3.2 (Answer)

Exercise 10.3.2 (Answer)

# Exercise 10.3.2 (Homework)

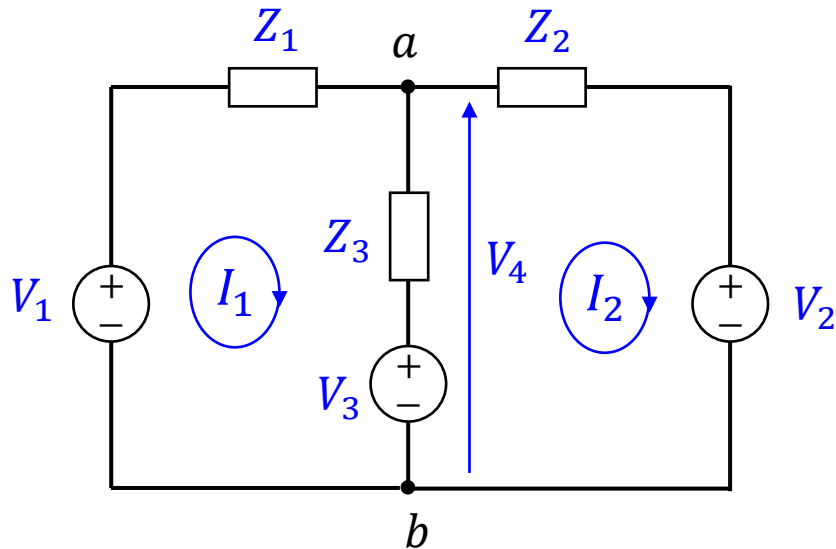

KVL


$$\text{Loop 1: } V_1 - V_3 = (Z_1 + Z_3)I_1 - Z_3I_2$$

$$\text{Loop 2: } -V_2 + V_3 = -Z_3I_1 + (Z_2 + Z_3)I_2$$

$$\begin{pmatrix} V_1 - V_3 \\ -V_2 + V_3 \end{pmatrix} = \begin{pmatrix} Z_1 + Z_3 & -Z_3 \\ -Z_3 & Z_2 + Z_3 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} Z_1 + Z_3 & -Z_3 \\ -Z_3 & Z_2 + Z_3 \end{pmatrix}^{-1} \begin{pmatrix} V_1 - V_3 \\ -V_2 + V_3 \end{pmatrix}$$

# Exercise 10.3.2 (Homework)

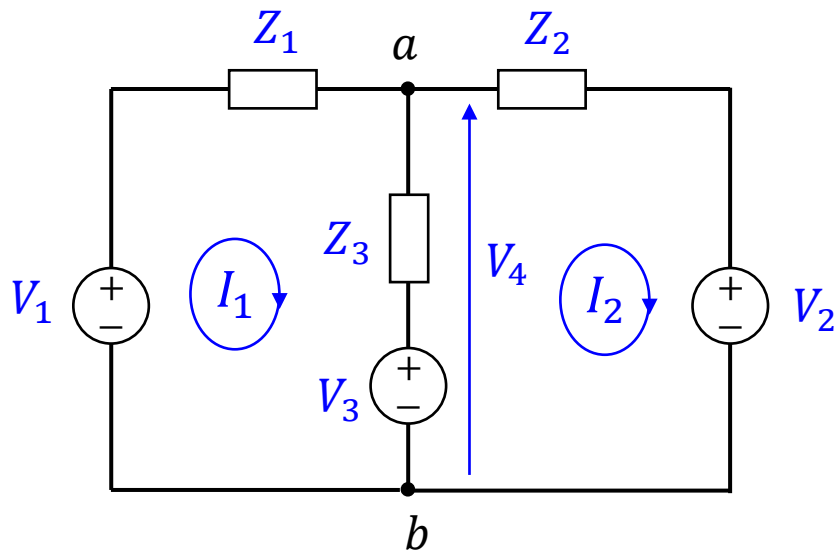

$$I_1 = \frac{(Z_2 + Z_3)(V_1 - V_3) + Z_3(-V_2 + V_3)}{(Z_1 + Z_3)(Z_2 + Z_3) - Z_3^2}$$

$$= \frac{(Z_2 + Z_3)V_1 - Z_3V_2 - Z_2V_3}{Z_1Z_2 + Z_2Z_3 + Z_3Z_1}$$

$$V_4 = V_1 - Z_1I_1$$

$$= V_1 - Z_1 \frac{(Z_2 + Z_3)V_1 - Z_3V_2 - Z_2V_3}{Z_1Z_2 + Z_2Z_3 + Z_3Z_1}$$


$$= \frac{Z_2Z_3V_1 + Z_1Z_3V_2 + Z_1Z_2V_3}{Z_1Z_2 + Z_2Z_3 + Z_3Z_1}$$

$$= \frac{\frac{V_1}{Z_1} + \frac{V_2}{Z_2} + \frac{V_3}{Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$

# Exercise 10.4.2 (Homework)

Exercise 10.4.2 (Homework)

# Exercise 10.4.2 (Homework)

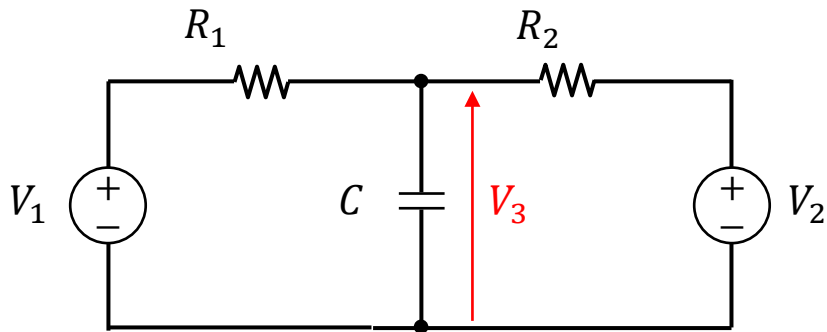

1. Derive the voltage  $V_3$  as a function of  $R_1$ ,  $R_2$ ,  $C$ ,  $V_1$ , and  $V_2$ .
2.  $R_1 = R_2 = R = 1$  [k $\Omega$ ],  $C = 0.01$  [ $\mu$ F], and

$$v_1 = V_{1m} \sin \omega t$$

$$v_2 = V_{2m} \sin \left( \omega t - \frac{\pi}{2} \right)$$

where  $V_{1m} = 4$  [V] ( $V_{1,p-p} = 8$  [V]),  
 $V_{2m} = 2$  [V] ( $V_{2,p-p} = 4$  [V]) and  
 $f = 15.9$  [kHz].

Show that

$$V_{3e} = \frac{2}{\sqrt{2}} \text{ [V]}, \psi_3 = -53^\circ$$


# Exercise 10.4.2 (Answers)

## Exercise 10.4.2 (Answers)

The answers to Exercise 10.4.2.




# Exercise 10.4.2 (Answers)

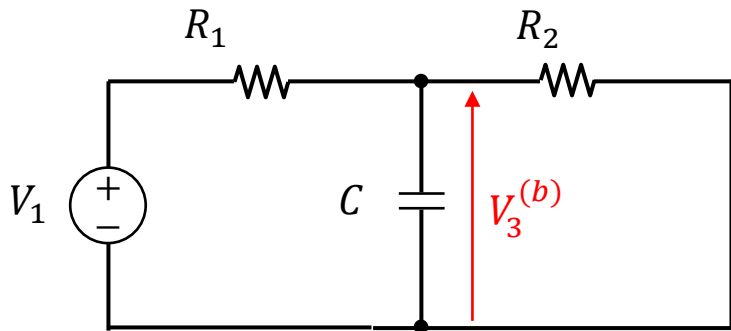

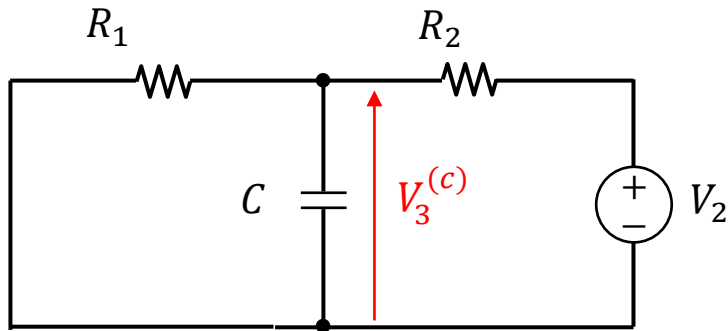
1.

$$V_3^{(b)} = \frac{\frac{1}{\frac{1}{R_2} + j\omega C}}{R_1 + \frac{1}{\frac{1}{R_2} + j\omega C}} V_1$$

$$= \frac{1}{1 + \frac{R_1}{R_2}(1 + j\omega CR_2)} V_1$$



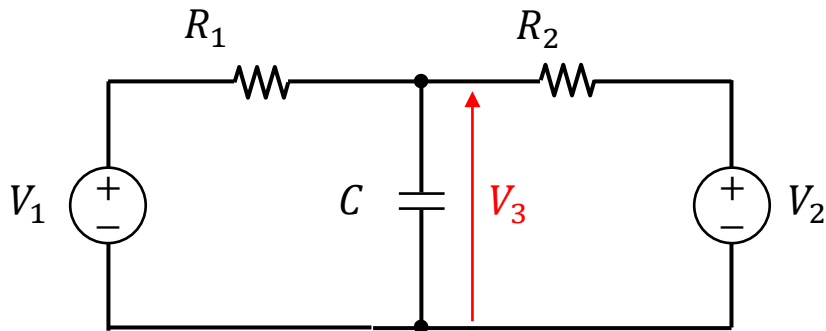
$$V_3^{(c)} = \frac{1}{1 + \frac{R_2}{R_1}(1 + j\omega CR_1)} V_2$$



$$V_3 = V_3^{(b)} + V_3^{(c)}$$

$$= \frac{1}{1 + \frac{R_1}{R_2}(1 + j\omega CR_2)} V_1 + \frac{1}{1 + \frac{R_2}{R_1}(1 + j\omega CR_1)} V_2$$

# Exercise 10.4.2 (Answers)

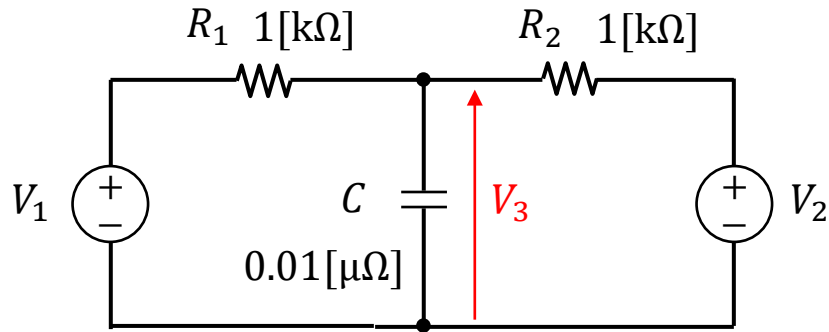

$$V_1 = V_{1e} = \frac{4}{\sqrt{2}}$$

$$V_2 = V_{2e} (\cos 90^\circ - j \sin 90^\circ) = -j \frac{2}{\sqrt{2}}$$

$$\begin{aligned} \omega CR &= 2 \times \pi \times 15.9 \times 10^3 \text{ [Hz]} \times 0.01 \times 10^{-6} \text{ [F]} \times 10^3 \text{ [}\Omega\text{]} \\ &= 1.0 \end{aligned}$$

$$\begin{aligned} V_3 &= \frac{1}{1 + \frac{R_1}{R_2} (1 + j\omega CR_2)} V_1 + \frac{1}{1 + \frac{R_2}{R_1} (1 + j\omega CR_1)} V_2 \\ &= \frac{V_1 + V_2}{1 + (1 + j)} \\ &= \frac{2}{\sqrt{2}} \frac{2 - j}{2 + j} \end{aligned}$$


$$V_{3e} = \frac{2}{\sqrt{2}}$$

$$\psi_3 = -\tan^{-1} \frac{1}{2} - \tan^{-1} \frac{1}{2} = -53^\circ$$

# Exercise 10.5.2 (Homework)

Exercise 10.5.2 (Homework)

# Exercise 10.5.2 (Homework)

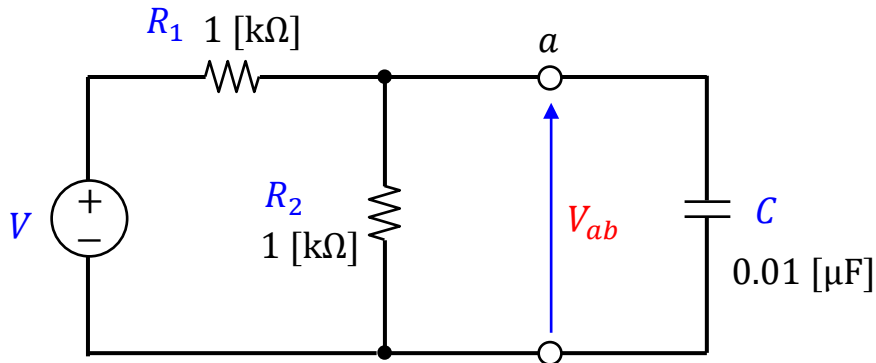

Original Circuit

1. Derive  $V_{ab}$  as a function of  $R_1$ ,  $R_2$ ,  $C$ , and  $V$  by applying Ho-Thévenin's Theorem.

2.  $v = V_m \sin \omega t$


where  $V_m = 4 \text{ [V]}$  ( $V_{p-p} = 8 \text{ [V]}$ ),  
 $f = 20 \text{ [kHz]}$ .

Find  $V_{ab}$ .

# Exercise 10.5.2 (Answer)

Exercise 10.5.2 (Answer)

# Exercise 10.5.2 (Answer)

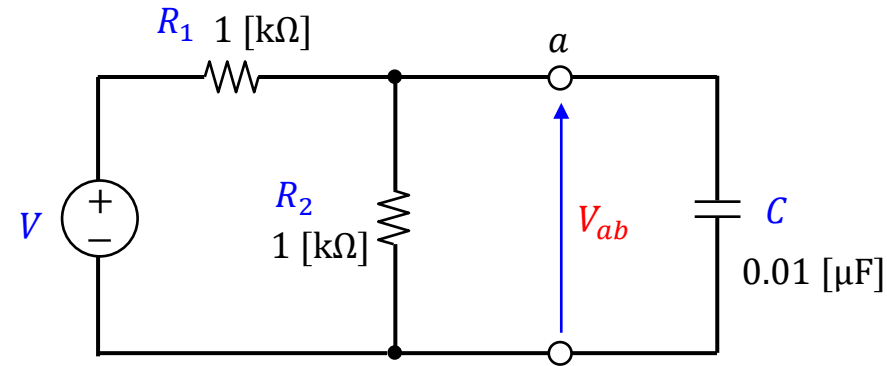


1.  $Z_1 = R_1, Z_2 = R_2, Z_L = -j \frac{1}{\omega C}.$

From the answer to Exercise 10.5.1,

$$\begin{aligned} V_{ab} &= \frac{Z_2 Z_L}{Z_1 Z_2 + Z_2 Z_L + Z_L Z_1} V \\ &= \frac{-j \frac{R_2}{\omega C}}{R_1 R_2 + (R_1 + R_2) \left(-j \frac{1}{\omega C}\right)} V \\ &= \frac{R_2}{R_1 + R_2 + j\omega C R_1 R_2} V \end{aligned}$$

# Exercise 10.5.2 (Answer)

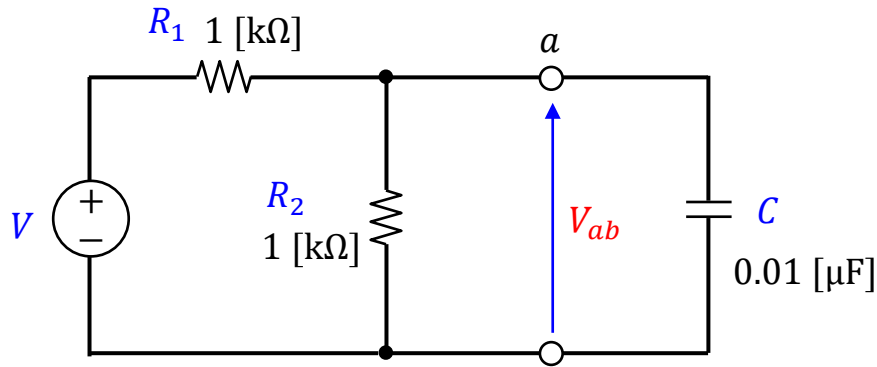

$$2. \quad V = \frac{4}{\sqrt{2}} \text{ [V]}$$

$$\begin{aligned} V_{abe} &= \frac{R_2}{\sqrt{(R_1 + R_2)^2 + (\omega C R_1 R_2)^2}} |V| \\ &= \frac{1000}{\sqrt{(2000 \text{ [}\Omega\text{]})^2 + (2 \times \pi \times 20 \times 10^3 \text{ [Hz]} \times 0.01 \times 10^{-6} \text{ [F]} \times 1000 \text{ [}\Omega\text{]} \times 1000 \text{ [}\Omega\text{]})^2}} \frac{4}{\sqrt{2}} \\ &= 1.20 \text{ [V]} \end{aligned}$$


$$\begin{aligned} \psi_{ab} &= -\tan^{-1} \frac{\omega C R_1 R_2}{R_1 + R_2} \\ &= -\tan^{-1} \frac{2 \times \pi \times 20 \times 10^3 \times 0.01 \times 10^{-6} \times 1000 \times 1000}{2000} \\ &= -32.1 \text{ [}^\circ\text{]} \end{aligned}$$

# Exercise 10.6 (Homework)

Exercise 10.6 (Homework)



# Exercise 10.6 (Homework)

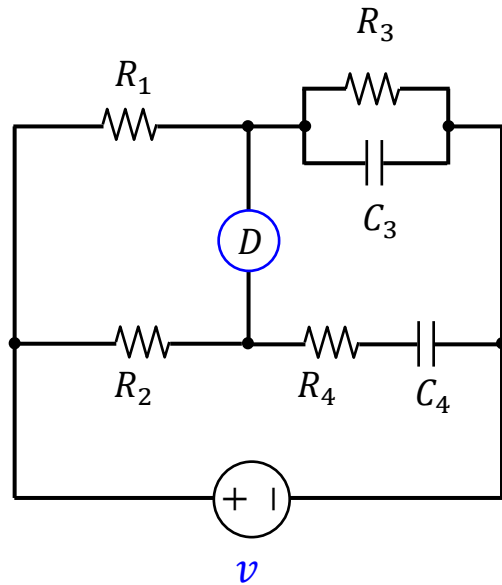


Derive the balanced condition of this bridge circuit.

# Exercise 10.6 (Answer)

Exercise 10.6 (Answer)

# Exercise 10.6 (Answer)

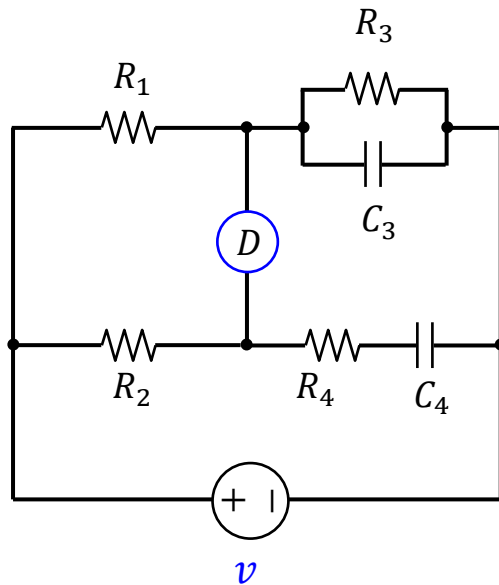

Balanced condition:

$$R_1 \left( R_4 - j \frac{1}{\omega C_4} \right) = R_2 \frac{1}{\frac{1}{R_3} + j\omega C_3}$$

$$\left( R_4 - j \frac{1}{\omega C_4} \right) \left( \frac{1}{R_3} + j\omega C_3 \right) = \frac{R_2}{R_1}$$

$$\frac{R_4}{R_3} + \frac{C_3}{C_4} + j \left( \omega C_3 R_4 - \frac{1}{\omega C_4 R_3} \right) = \frac{R_2}{R_1}$$

Real part:

$$\frac{R_4}{R_3} + \frac{C_3}{C_4} = \frac{R_2}{R_1}$$


Imaginary part:

$$\omega C_3 R_4 = \frac{1}{\omega C_4 R_3}$$

# Exercise 11.2.1 (Homework)

Exercise 11.2.1 (Homework)

# Exercise 11.2.1 (Homework)

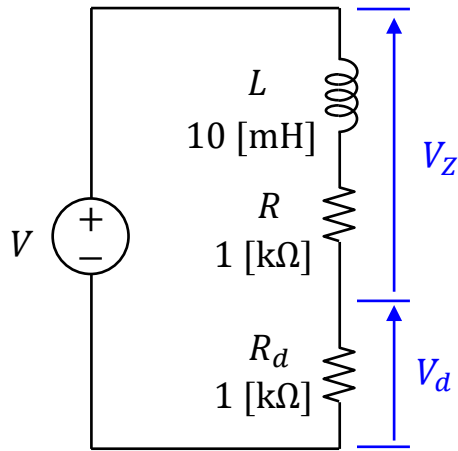

1. Derive  $G_Z = 20\log_{10}|Z|$ , and  $\psi_Z$  as functions of the frequency  $f$ .  
 $Z$  is the impedance of  $R - L$  series circuit.
2. Plot  $G_Z$  and  $\psi_Z$  in the range of  $0.1 \text{ [kHz]} \leq f \leq 1000 \text{ [kHz]}$ .

# Exercise 11.2.1 (Answer)

Exercise 11.2.1 (Answer)

# Experiment 11.2.1 (Answer)



$$Z = R + j\omega L$$

The unit of  $Z$ : [k $\Omega$ ]

$$\begin{aligned} 20\log_{10}|Z| &= 20\log_{10} \sqrt{\left(\frac{R}{1000[\Omega]}\right)^2 + \left(\frac{\omega L}{1000[\Omega]}\right)^2} \\ &= 20\log_{10} \sqrt{\left(\frac{1000[\Omega]}{1000[\Omega]}\right)^2 + \left(\frac{2 \times \pi \times f[\text{Hz}] \times 0.01[\text{H}]}{1000[\Omega]}\right)^2} \quad [\text{dB}] \end{aligned}$$

$$\begin{aligned} \psi_Z &= \tan^{-1} \frac{\omega L}{R} \\ &= \tan^{-1} \frac{2 \times \pi \times f[\text{Hz}] \times 0.01[\text{H}]}{1000 [\Omega]} \quad [^\circ] \end{aligned}$$

# Experiment 11.2.1 (Answer)

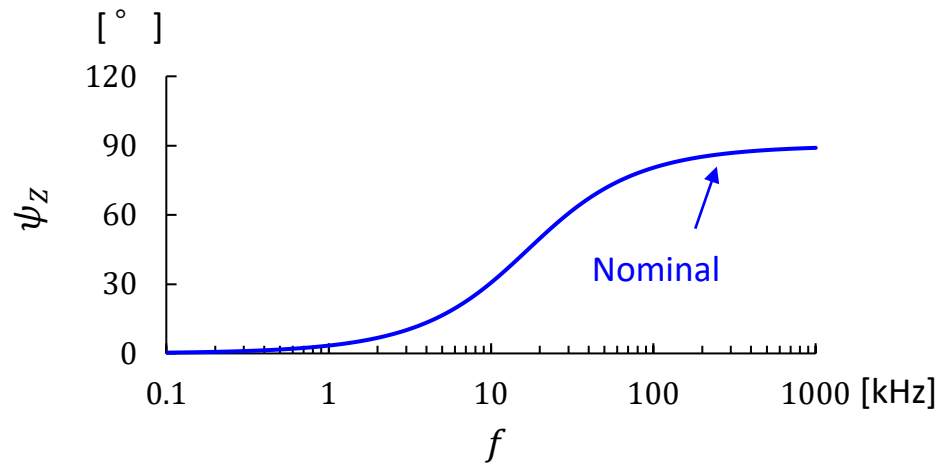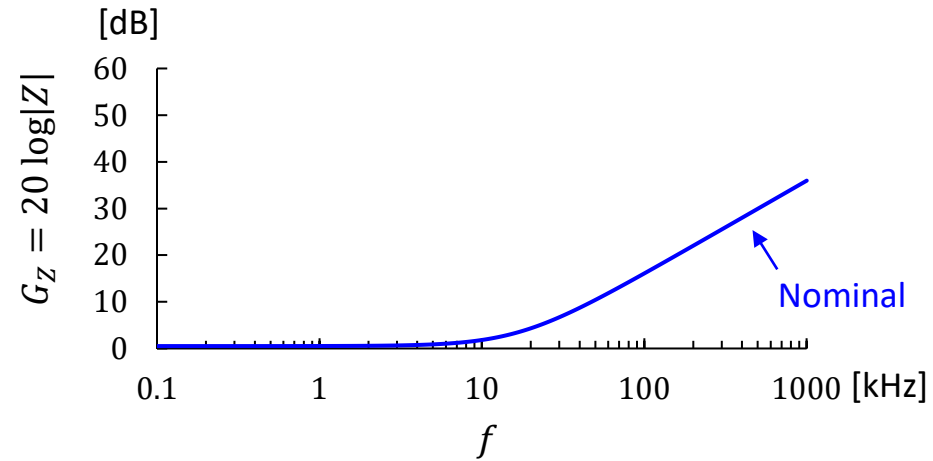




# Exercise 11.2.2 (Homework)

Exercise 11.2.2 (Homework)

# Exercise 11.2.2 (Homework)

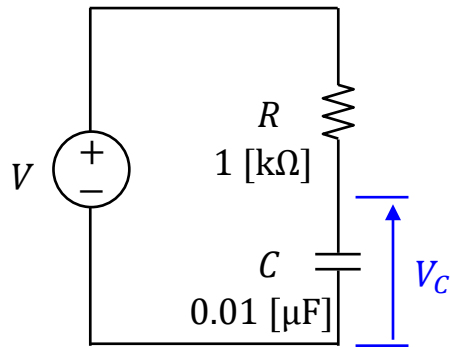


1. Derive  $G_Z = 20\log_{10} \left| \frac{V_C}{V} \right|$ , and  $\psi_{V_C-V}$  as functions of  $\omega$ .
2. Plot  $G_Z$  and  $\psi_Z$  in the range of  $0.1 \text{ [kHz]} \leq f \leq 1000 \text{ [kHz]}$ .

# Exercise 11.2.2 (Answer)

Exercise 11.2.2 (Answer)

# Exercise 11.2.2 (Answer)


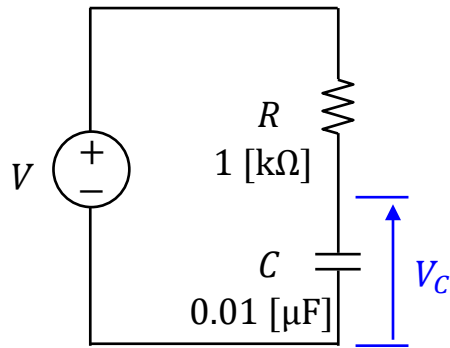


$$V_C = \frac{-j \frac{1}{\omega C}}{R - j \frac{1}{\omega C}} V$$
$$= \frac{1}{1 + j\omega CR} V$$

$$20 \log_{10} \frac{|V_C|}{|V|} = 20 \log_{10} \frac{1}{\sqrt{1 + (\omega CR)^2}}$$

$$\psi_{V_C - V} = -\tan^{-1} \omega CR$$


# Exercise 11.2.2 (Answer)

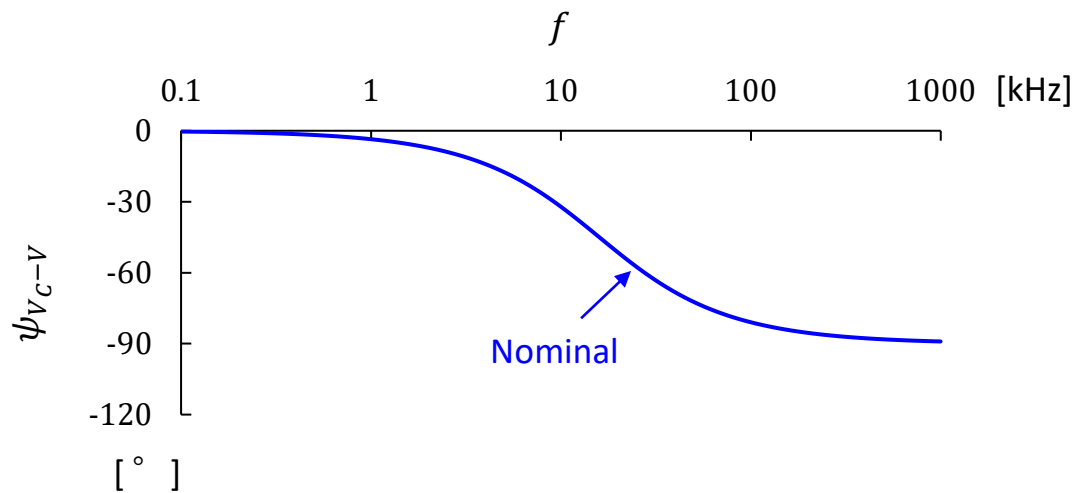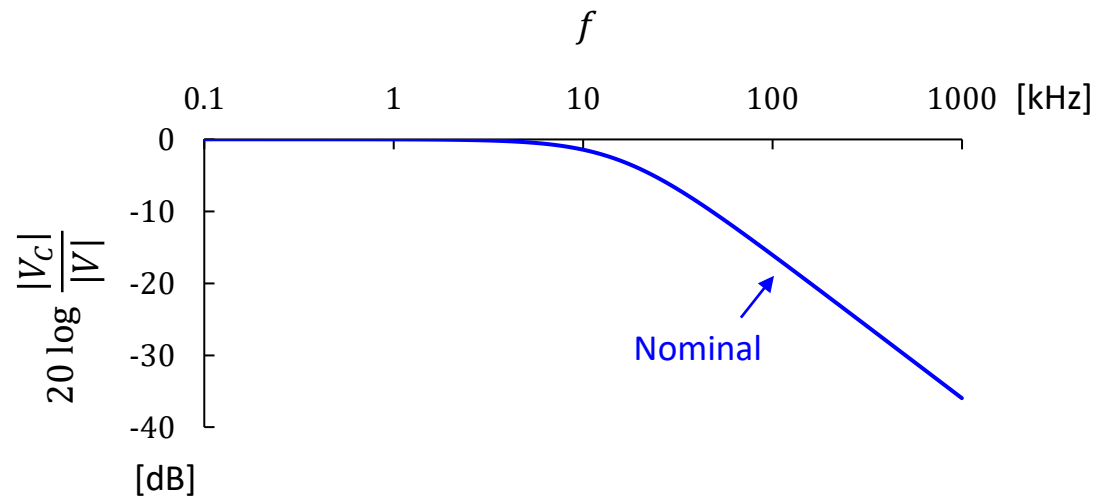

# Exercise 12.4 (Homework)

Exercise 12.4 (Homework)

# Exercise 12.4 (Homework)

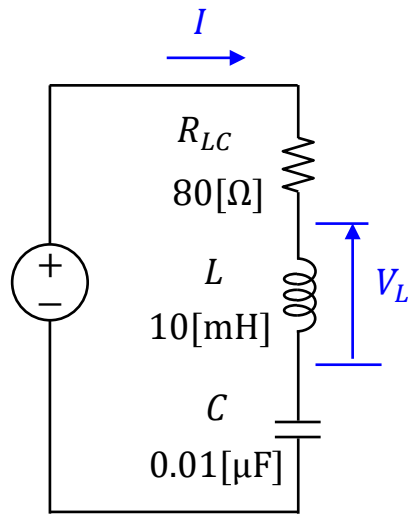

Equivalent Circuit

1. Derive the relationship between the ratio

$$G_{V_L} = 20 \log \frac{V_{Le}}{V_e} \quad [\text{dB}]$$

and the frequency  $f$ .


2. Derive the relationship between the phase angle of  $V_L$  relative to  $V$ ,  $\psi_{V_L-V}$ , and the frequency  $f$ .
3. Draw the plots of  $G_{V_C}$  and  $\psi_{V_L-V}$  in the range from 1 [kHz] to 100 [kHz].

# Exercise 12.4 (Answer)

Exercise 12.4 (Answer)



# Exercise 12.4 (Answer)

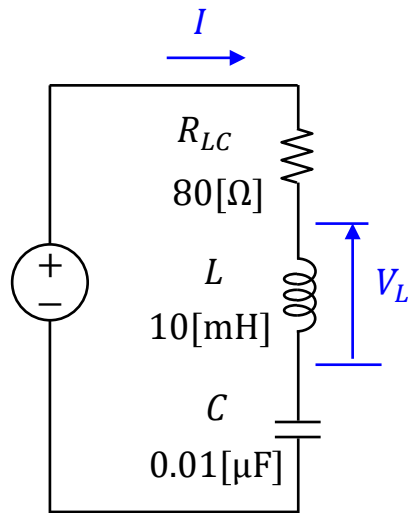

Equivalent Circuit

$$G_{V_C} = 20 \log \frac{V_{C_e}}{V_e}$$

$$V = \left\{ R + j \left( \omega L - \frac{1}{\omega C} \right) \right\} I$$


$$V_L = j\omega L I$$

$$V_L = \frac{j\omega L}{R + j \left( \omega L - \frac{1}{\omega C} \right)} V$$


$$G_{V_L} = 20 \log \frac{\omega L}{\sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}}$$

$$\psi_{V_L-V} = \frac{\pi}{2} - \tan^{-1} \frac{\omega L - \frac{1}{\omega C}}{R}$$


# Frequency Characteristics

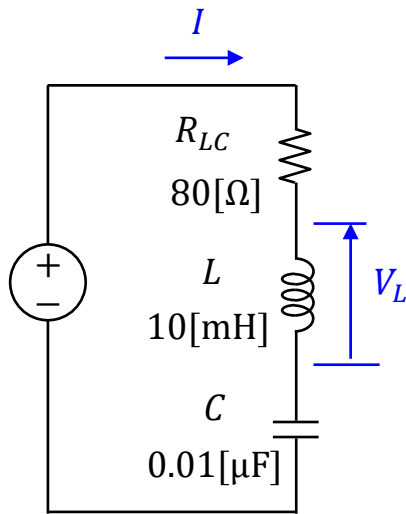

Equivalent Circuit

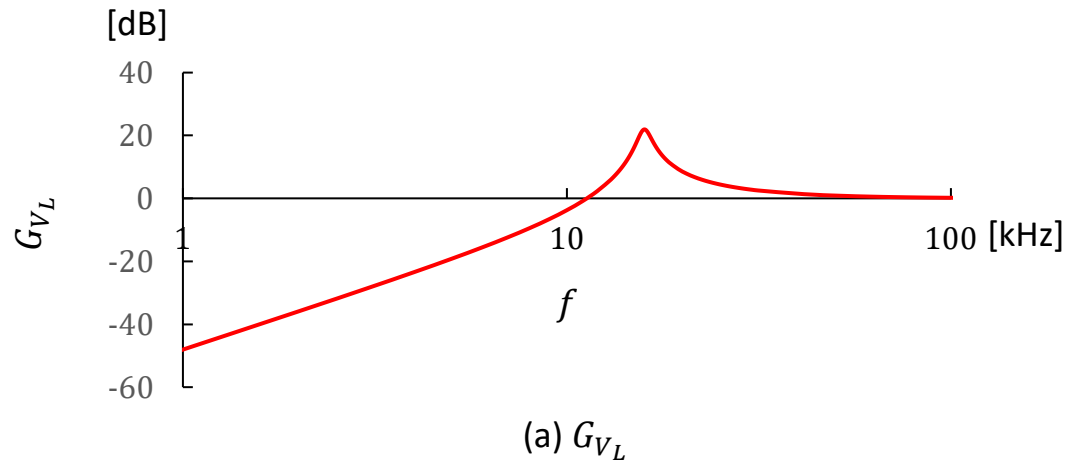

(a)  $G_{V_L}$

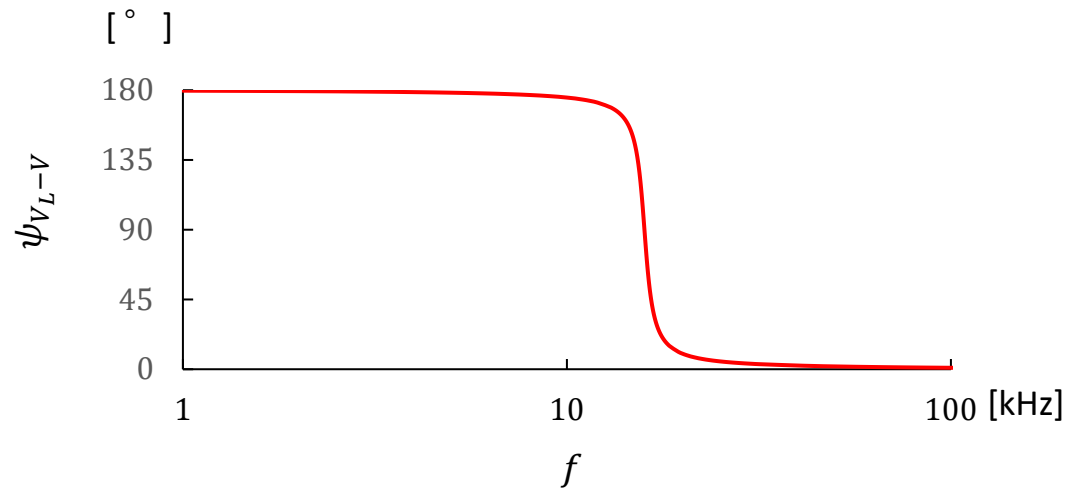


(b)  $\psi_{V_L-v}$

# Exercise 12.8.1 (Homework)

Exercise 12.8.1 (Homework)

# Exercise 12.8.1 (Homework)

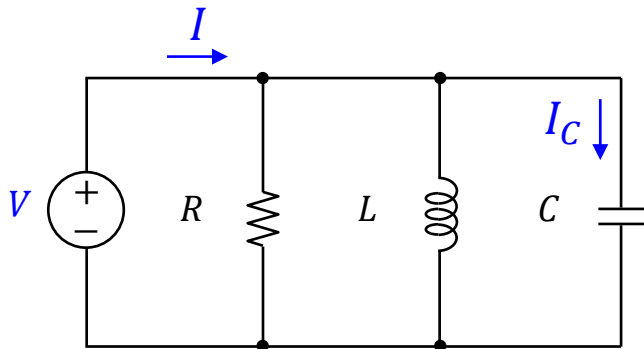


Assume that voltage  $V$  is applied to this circuit.

1. Write the relationship between the source current  $I$  and the voltage  $V$ .
2. Write the relationship between the capacitance current  $I_C$  and the voltage  $V$ .
3. Write the relationship between the capacitance current  $I_C$  and the source current  $I$ .
4. Write the relationship between the effective value of capacitance current  $I_{Ce}$  and that of the source current  $I_e$ .
5. Write the relationship between the ratio  $G_{I_C} = 20 \log I_{Ce}/I_e$  and the frequency  $f$ .
6. Write the phase angle of the capacitance current relative to the source current  $\psi_{I_C-I}$  as a function of frequency  $f$ .

# Exercise 12.8.1 (Answer)

Exercise 12.8.1 (Answer)

# Exercise 12.8.1 (Answer)

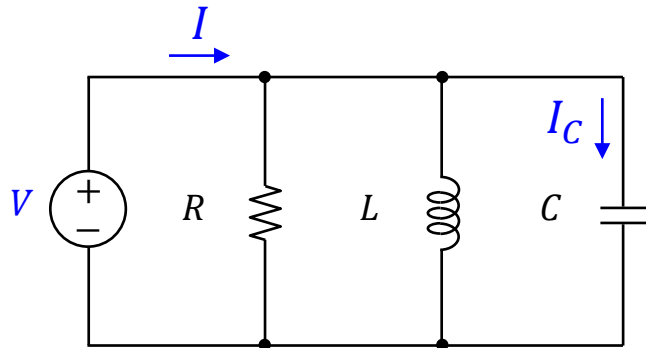

$$I = \left\{ \frac{1}{R} - j \left( \frac{1}{\omega L} - \omega C \right) \right\} V$$

$$I_C = j\omega C V$$

$$I_C = \frac{j\omega C}{\frac{1}{R} - j \left( \frac{1}{\omega L} - \omega C \right)} I \quad \rightarrow \quad \frac{I_{Ce}}{I_e} = \frac{\omega C}{\sqrt{\left( \frac{1}{R} \right)^2 + \left( \frac{1}{\omega L} - \omega C \right)^2}}$$


$$G_{I_C} = 20 \log \frac{\omega C}{\sqrt{\left( \frac{1}{R} \right)^2 + \left( \frac{1}{\omega L} - \omega C \right)^2}}$$

$$\psi_{I_C-I} = \frac{\pi}{2} + \tan^{-1} R \left( \frac{1}{\omega L} - \omega C \right)$$

# Exercise 13.2.2 (Homework)

Exercise 13.2.2 (Homework)

# Exercise 13.2.2 (Homework)

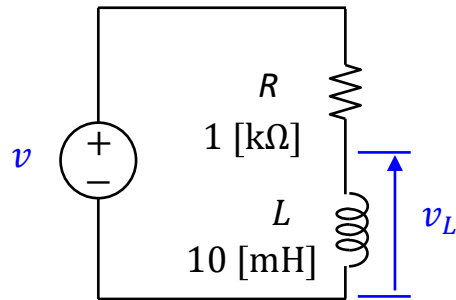


$$v = v_1 + v_3$$

$$v_1 = \sqrt{2}V_e \sin \omega t$$

$$v_3 = \frac{\sqrt{2}}{3}V_e \sin 3\omega t$$

$$f = 15.9 \text{ [kHz]}$$

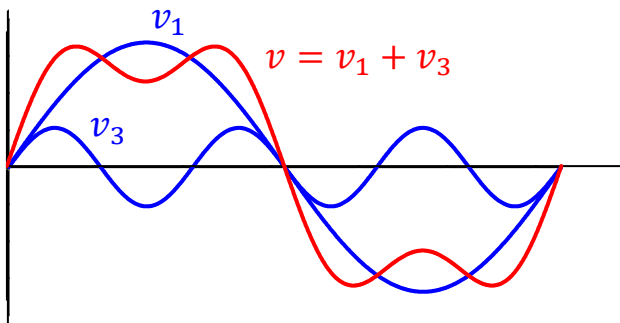

(1) Derive  $V_{L1}$  and  $V_{L3}$ .

(2) Derive  $v_{L1}$  and  $v_{L3}$ .


(3) Draw the waveform of  $v_L (= v_{L1} + v_{L3})$ .



# Exercise 13.2.2 (Answer)

Exercise 13.2.2 (Answer)

# Exercise 13.2.2 (Answer)

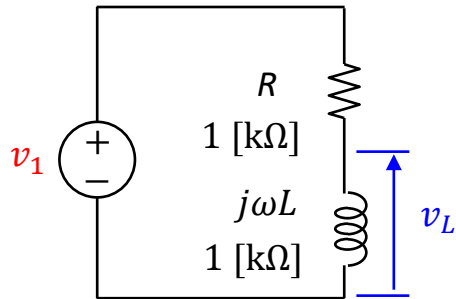


$$v_1 = \sqrt{2}V_e \sin \omega t$$

$$j\omega L = j2\pi \times 15.9 \times 10^3 \times 0.01 \\ = j \text{ [k}\Omega\text{]}$$

$$(1) \quad V_{L1} = \frac{j\omega L}{R + j\omega L} V_1 = \frac{j}{1 + j} V_e$$

$$(2) \quad v_{L1} = \sqrt{2} \frac{1}{\sqrt{2}} V_e \sin \left( \omega t + \frac{\pi}{4} \right) \\ = V_e \sin \left( \omega t + \frac{\pi}{4} \right)$$

# Exercise 13.2.2 (Answer)

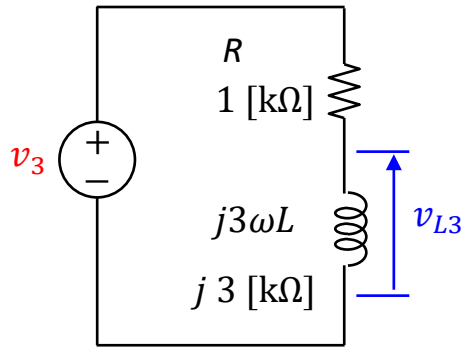


$$v_3 = \frac{\sqrt{2}}{3} V_e \sin 3\omega t$$

$$j3\omega L = j3 \times 2\pi \times 15.9 \times 10^3 \times 0.01 \\ = j3 \text{ [k}\Omega\text{]}$$

$$(1) \quad V_{L3} = \frac{j3\omega L}{R + j3\omega L} V_1 = \frac{j3}{1 + j3} \frac{V_e}{3}$$


$$(2) \quad v_{L3} = \frac{3}{\sqrt{10}} \frac{\sqrt{2}}{3} V_e \sin\left(\omega t + \frac{\pi}{2} - \tan^{-1} 3\right) \\ \approx \frac{1}{\sqrt{5}} V_e \sin(\omega t + 0.1\pi)$$

# Exercise 13.2.2 (Answer)

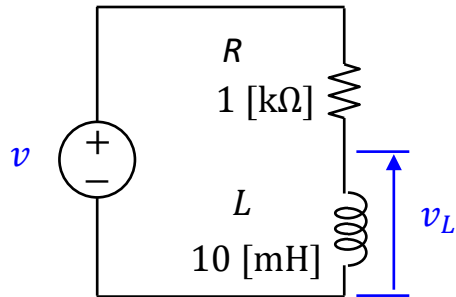


$$(3) \quad v_L = v_{L1} + v_{L3} \\ \approx V_e \sin\left(\omega t + \frac{\pi}{4}\right) + \frac{1}{\sqrt{5}} V_e \sin(\omega t + 0.1\pi)$$

$$V_e = 1$$

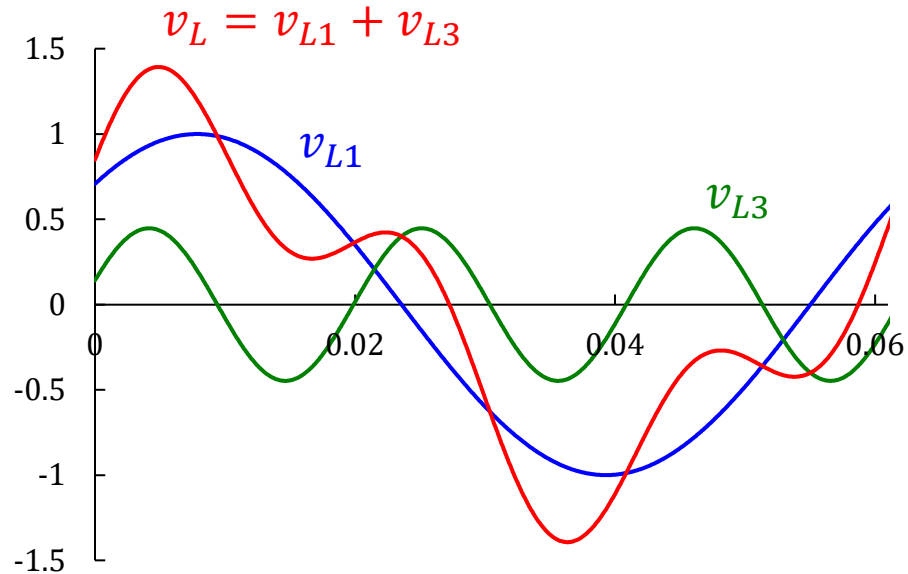

# For your reference

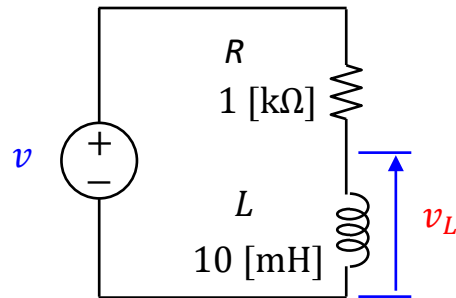


$$v = v_1 + v_3 + \dots + v_{999}$$

$$v_C = v_{C1} + v_{C3} + \dots + v_{C999}$$

$$v_{Lk} = \frac{k}{\sqrt{1+k^2}} \frac{\sqrt{2}}{k} V_e \sin\left(\omega t + \frac{\pi}{2} - \tan^{-1} k\right)$$

$$V_e = 1$$

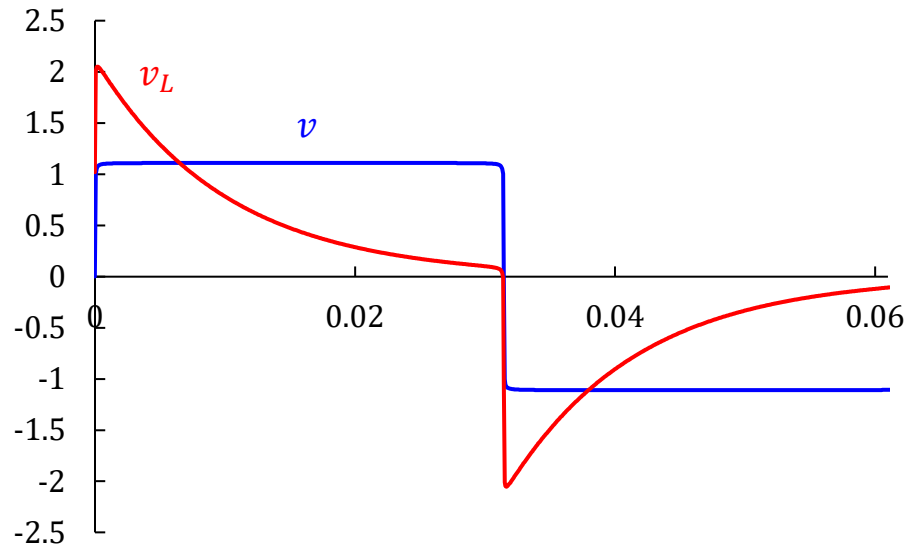


This is for your reference. If the harmonics up to 999<sup>th</sup> are summed, the inductance voltage  $v_L$  becomes like this one.

# Exercise 13.3.3 (Homework)

Exercise 13.3.3 (Homework)

# Exercise 13.3.3 (Homework)

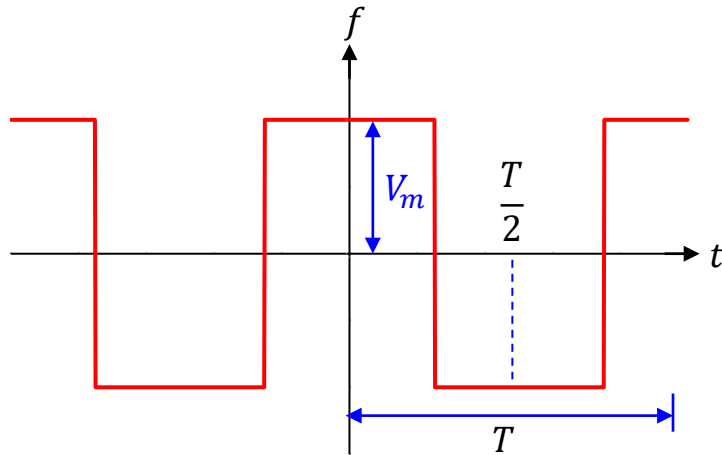


Find the Fourier series for this square wave.

# Exercise 13.3.3 (Answer)

Exercise 13.3.3 (Answer)



# Exercise 13.3.3 (Answer)

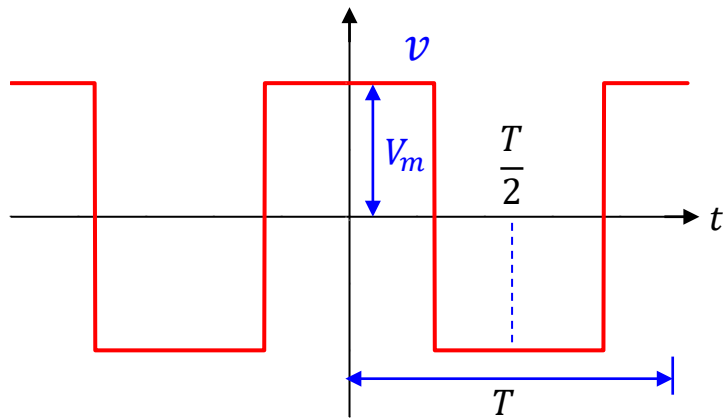

$$a_0 = \frac{1}{T} \int_0^T v dt$$
$$= 0$$

$$a_n = \frac{2}{T} \left( \int_0^{T/4} V_m \cos n\omega t dt - \int_{T/4}^{3T/4} V_m \cos n\omega t dt \right. \\ \left. + \int_{3T/4}^{T/4} V_m \cos n\omega t dt \right)$$
$$= \frac{4}{\pi} V_m \frac{\sin \frac{n\pi}{2}}{n}$$

$$b_n = \frac{2}{T} \int_0^T v \sin n\omega t dt$$
$$= 0$$

$$v = V_{m0} \cos \omega t - \frac{1}{3} V_{m0} \cos 3\omega t + \frac{1}{5} V_{m0} \cos 5\omega t - \dots$$

$$V_{m0} = \frac{4}{\pi} V_m$$

# Exercise 13.4.2 (Homework)

Exercise 13.4.2 (Homework)

# Exercise 13.4.2 (Homework)

Draw the frequency spectrum of the following two equations:

(1)

$$v = V_{m0} \sin \omega t - \frac{1}{3} V_{m0} \sin 3\omega t + \frac{1}{5} V_{m0} \sin 5\omega t - \dots$$

$$V_{m0} = \frac{4}{\pi} V_m$$

$$V_m = 1 \text{ [V]}, f = 1 \text{ [Hz]}.$$

(2)

$$v = V_{m0} \sin \omega t - \frac{1}{2} V_{m0} \sin 2\omega t + \frac{1}{3} V_{m0} \sin 3\omega t - \dots$$



$$V_{m0} = \frac{2}{\pi} V_m$$

$$V_m = 1 \text{ [V]}, f = 1 \text{ [Hz]}.$$

# Exercise 13.4.2 (Answer)



Exercise 13.4.2 (Answer)

# Exercise 13.4.2 (Answer)

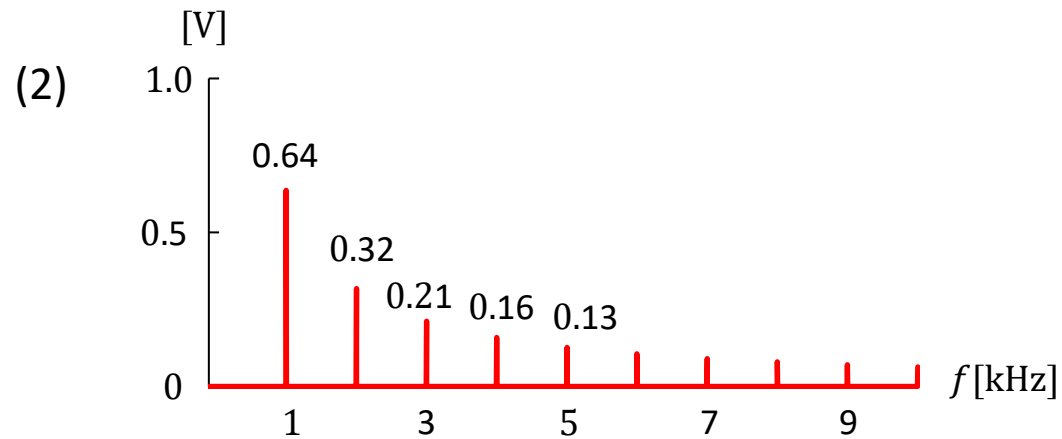
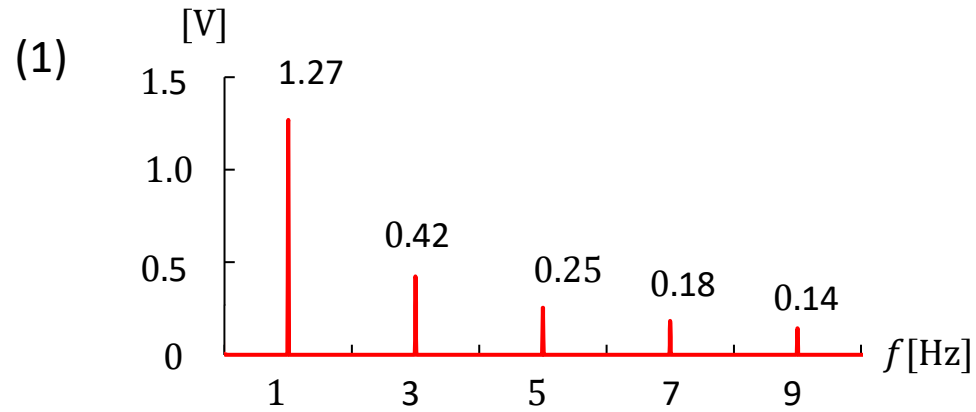


# For your reference

(1)

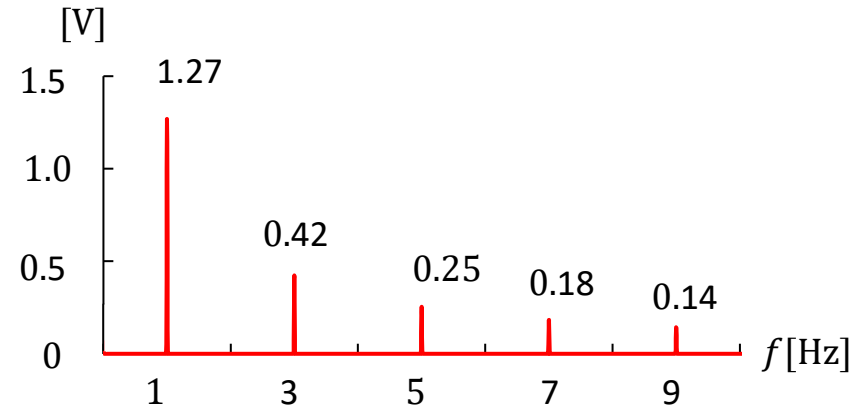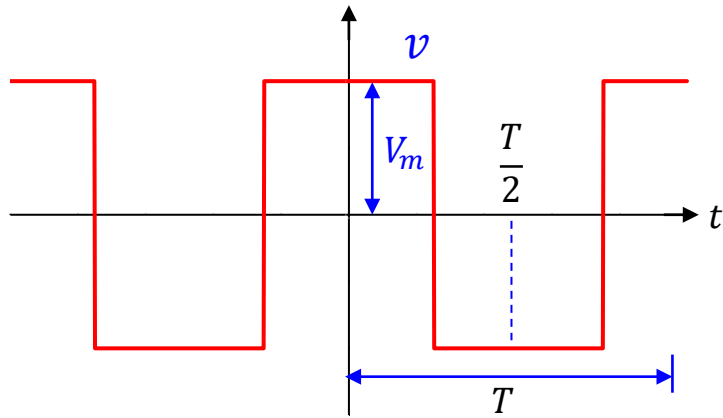


(2)

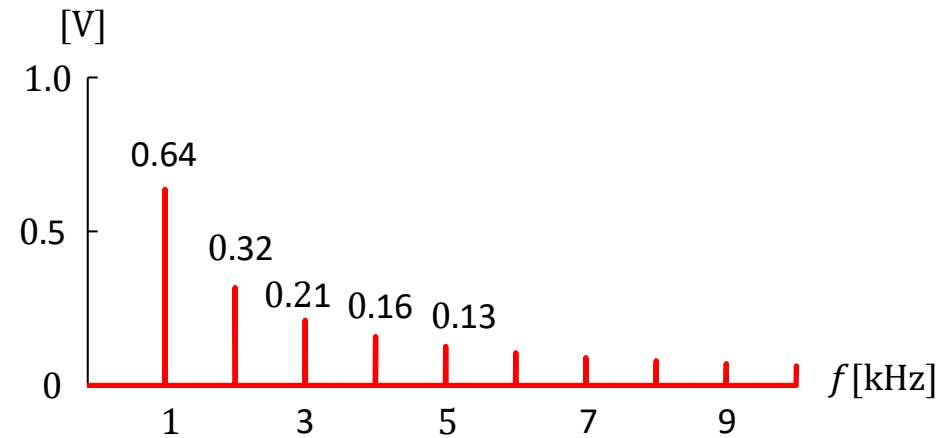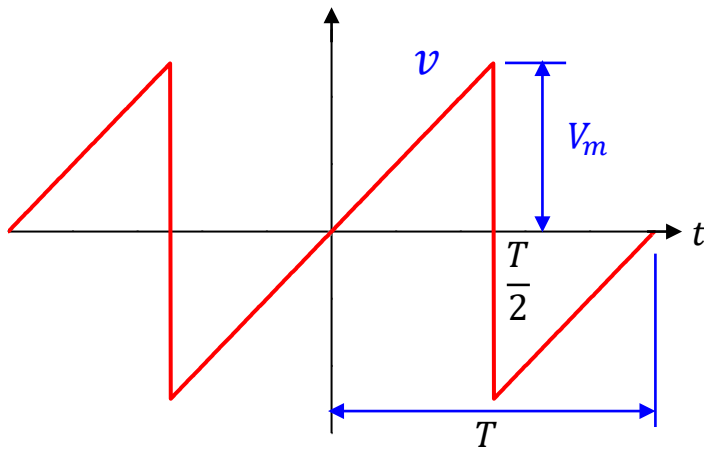

# Exercise 14.3 (Homework)


## Exercise 14.3 (Homework)

# Exercise 14.3 (Homework)

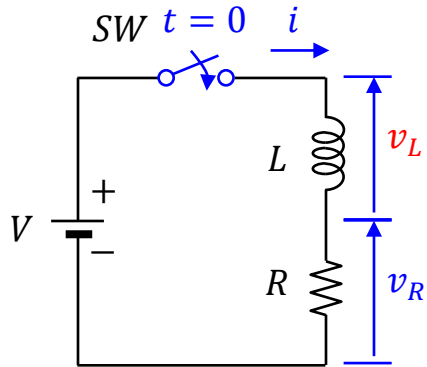

(1) Why do  $v_R$  increase and  $v_L$  decrease?

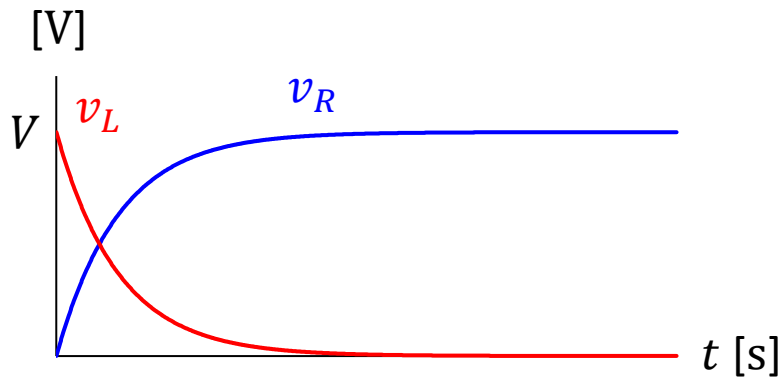(2) Why does  $\frac{dv_R}{dt}$  decrease?




Pause the video, and answer the questions.



# Exercise 14.3 (Answer)

Exercise 14.3 (Answer)

# Exercise 14.3 (Answer)

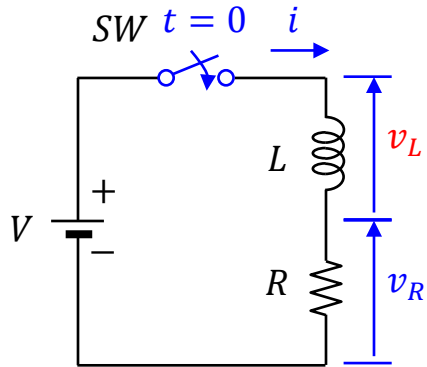


(1) Why do  $v_R$  increase and  $v_L$  decrease?


$$\frac{di}{dt} = \frac{v_L}{L} \Rightarrow i \text{ increases.}$$

$\Rightarrow v_R$  increases.

$\Rightarrow v_L$  decreases.

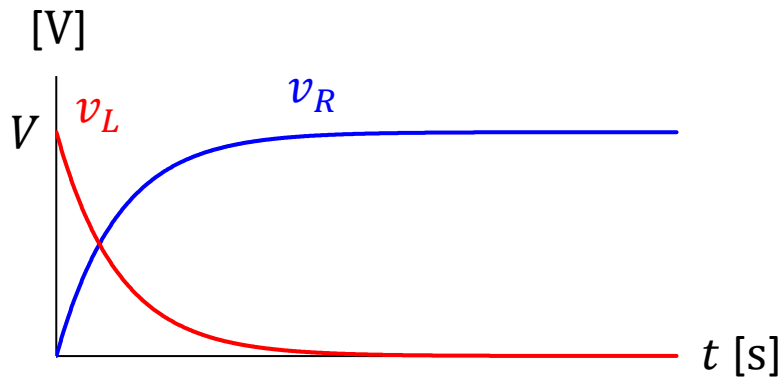


# Exercise 14.3 (Answer)

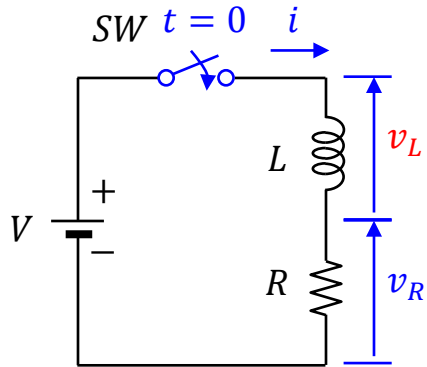

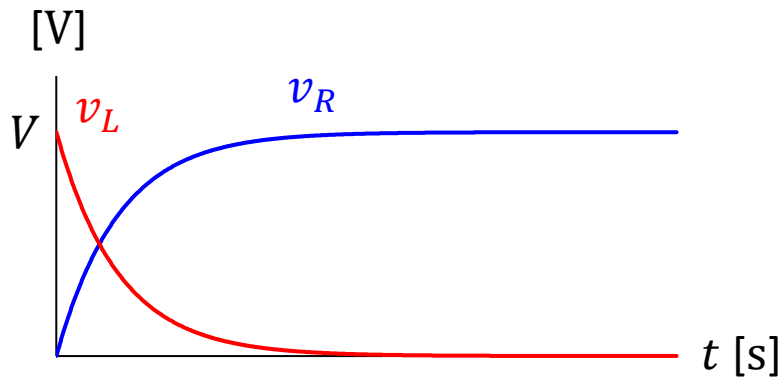(2) Why does  $\frac{dv_R}{dt}$  decrease?

$$\frac{dv_R}{dt} = R \frac{di}{dt} = \frac{R}{L} v_L$$


$v_L$  decreases.  $\Rightarrow \frac{dv_R}{dt}$  decreases.



# Exercise 14.4 (Homework)

Exercise 14.4 (Homework)

# Exercise 14.4.1 (Homework)

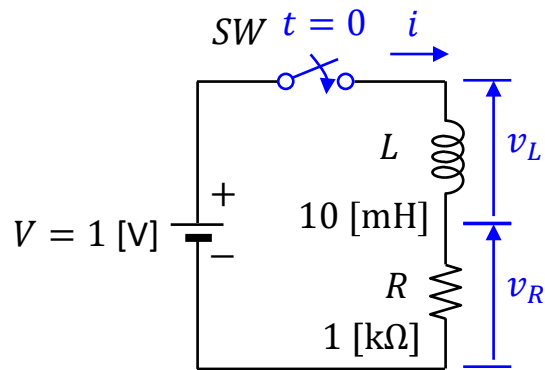

The switch  $SW$  is turned on at  $t = 0$ .

Find  $v_R$ ,  $v_L$  and  $i$  at  $t = \tau$ , where  $\tau$  is the time constant.

# Exercise 14.4.1 (Answer)

Exercise 14.4.1 (Answer)

# Exercise 14.4.1

( $t \geq 0$ )

$$i = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$

$$v_L = V e^{-\frac{R}{L}t}$$


$$v_R = V (1 - e^{-\frac{R}{L}t})$$

$$\text{At } t = \tau = \frac{L}{R} = 10 \text{ } [\mu\text{s}]$$

$$i = \frac{V}{R} (1 - e^{-1}) = \frac{1}{1000} (1 - e^{-1}) \approx 0.63 \text{ [mA]}$$

$$v_L = V e^{-1} = 1 e^{-1} \approx 0.37 \text{ [V]}$$
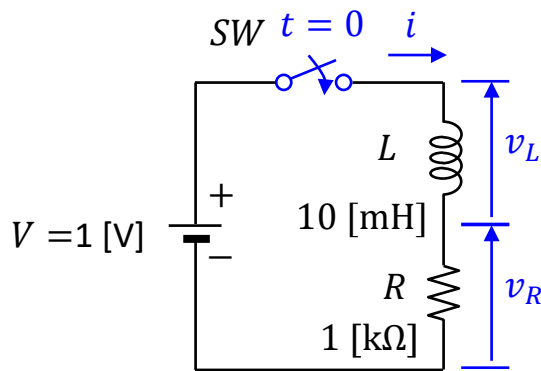
$$v_R = V (1 - e^{-1}) = 1 \times (1 - e^{-1}) \approx 0.63 \text{ [V]}$$




# Exercise 14.6 (Homework)

Exercise 14.6 (Homework)




# Exercise 14.6 (Homework)

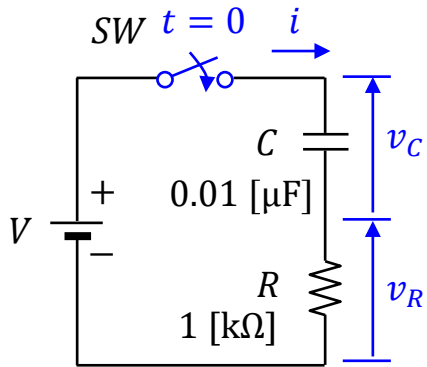

(1) Why are  $v_R = V$  [V] and  $v_C = 0$  [V] at  $t = 0$  ?

(2) What are the values of  $\frac{dq}{dt}$ ,  $\frac{dv_R}{dt}$ , and  $\frac{dv_C}{dt}$  at  $t = 0$  ?

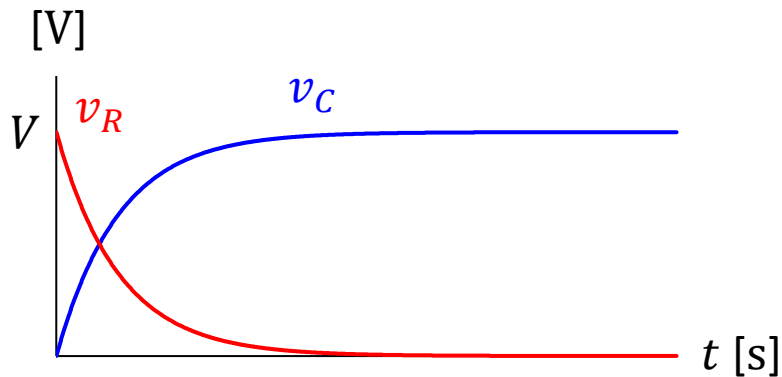
(3) What is time constant of this  $R - C$  circuit ?



# Exercise 14.6 (Answer)

Exercise 14.6 (Answer)

# Exercise 14.6 (Answer)

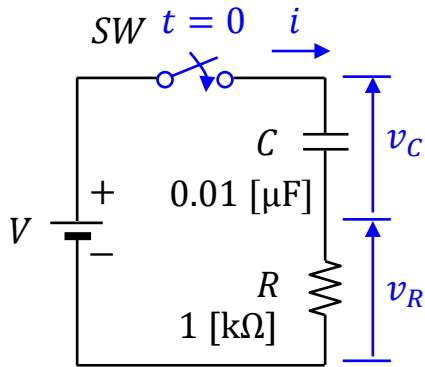


(1) Why are  $v_R = V$  [V] and  $v_C = 0$  [V] at  $t = 0$  ?

$$v_C = \frac{1}{C} \int i dt \Rightarrow i = C \frac{dv_C}{dt}$$

$\Rightarrow v_C$  cannot change instantaneously.


Initial condition:  $q = 0$  at  $t = 0$

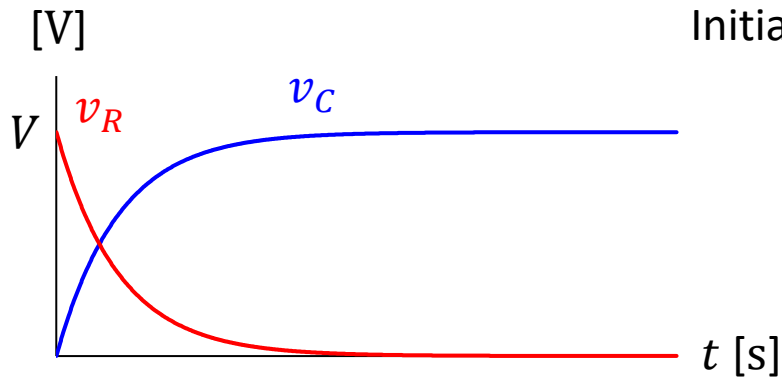

$\Rightarrow v_C = \frac{q}{C} = 0$  at  $t = 0$ .

$\Rightarrow v_R = V$  at  $t = 0$ .

# Exercise 14.6 (Answer)

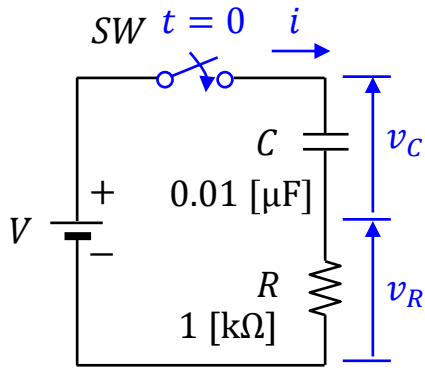

(2) What are  $\frac{dq}{dt}$ ,  $\frac{dv_R}{dt}$ ,  $\frac{dv_C}{dt}$  at  $t = 0$  ?


$$q = CV(1 - e^{-\frac{1}{RC}t})$$

$$\frac{dq}{dt} = \frac{V}{R} e^{-\frac{1}{RC}t}$$


$$i = \frac{dq}{dt}$$

$$\frac{dv_R}{dt} = R \frac{di}{dt} = R \frac{dV}{dt} \frac{1}{R} e^{-\frac{1}{RC}t} = -\frac{V}{RC} e^{-\frac{1}{RC}t}$$
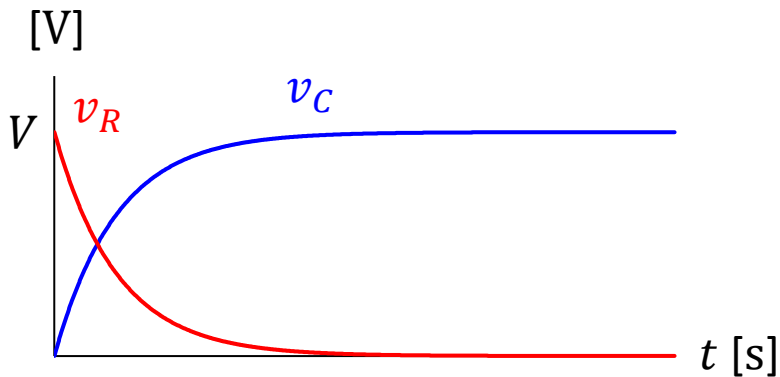
$$\frac{dv_C}{dt} = \frac{1}{C} \frac{dq}{dt} = \frac{V}{RC} e^{-\frac{1}{RC}t}$$



# Exercise 14.6 (Answer)

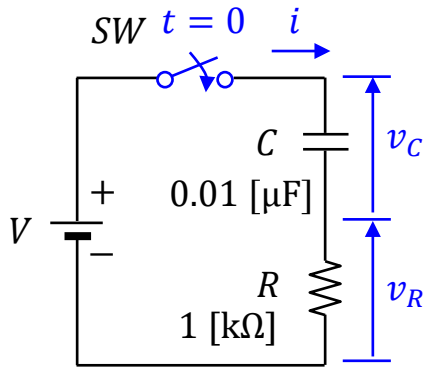


(3) What is time constant of this  $R - C$  circuit ?

$$v_C = V(1 - e^{-\frac{1}{RC}t})$$

The coefficient of  $t$ ,  $1/RC$  determines the rate at which the voltage  $v_C$  approaches to  $V$ .

The reciprocal of this coefficient is defined as the time constant of  $R - C$  circuit.


$$\tau = RC$$

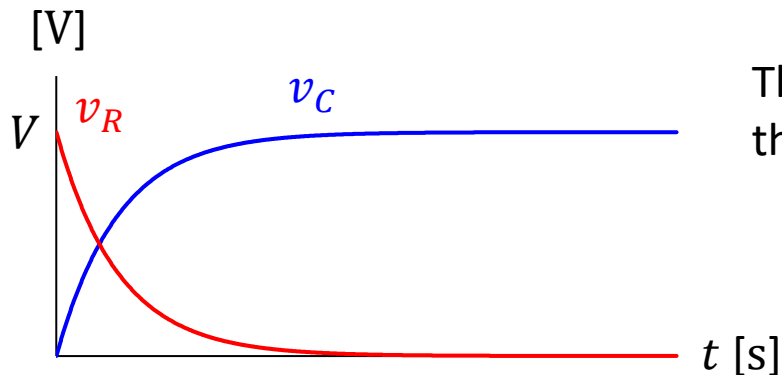

# Exercise 14.7 (Homework)

Exercise 14.7 (Homework)

# Exercise 14.7 (Homework)

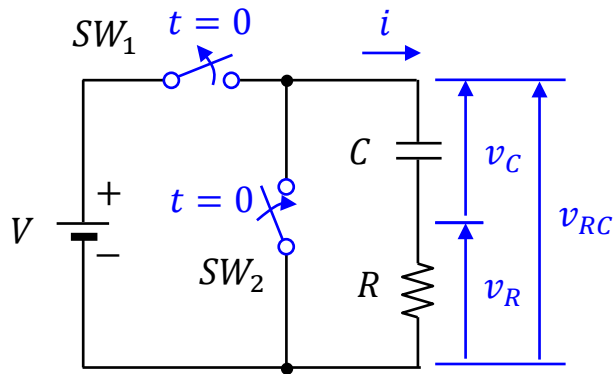

Find  $v_R$  and  $v_C$  for this circuit under the conditions that for  $t \geq 0$ ,  $v_{RC} = 0$ , and at  $t = 0$ ,  $q = CV$ .

# Exercise 14.7 (Answer)

Exercise 14.7 (Answer)



# Exercise 14.7 (Answer)

For  $t \geq 0$ ,  $v = 0$

$$0 = R \frac{dq}{dt} + \frac{q}{C}$$


Assume that  $q = Ae^{-\frac{1}{RC}t} + B$ , where  $A$  and  $B$  are constants.

$$\begin{aligned} 0 &= R \frac{d}{dt} (Ae^{-\frac{1}{RC}t} + B) + \frac{1}{C} (Ae^{-\frac{1}{RC}t} + B) \\ &= \frac{1}{C} B \\ B &= 0 \end{aligned}$$


At  $t = 0$ ,  $q = CV$ : initial condition

$$CV = A$$

$$q = CVe^{-\frac{1}{RC}t}$$

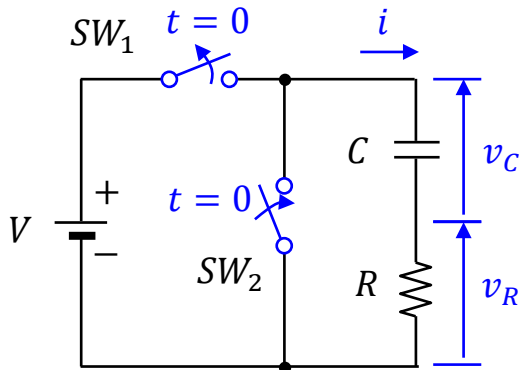


# Exercise 14.7 (Answer)



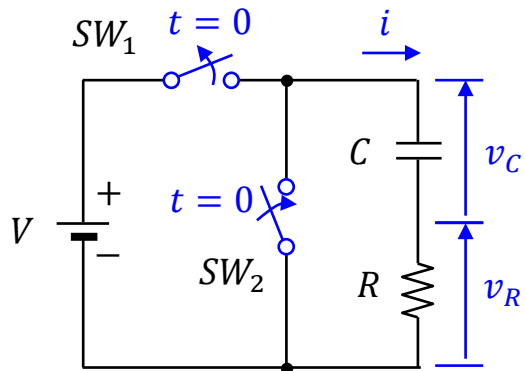


$$\begin{aligned}v_R &= Ri \\&= R \frac{dq}{dt} \\&= R \frac{d}{dt} \left\{ CV e^{-\frac{1}{RC}t} \right\} \\&= -V e^{-\frac{1}{RC}t}\end{aligned}$$
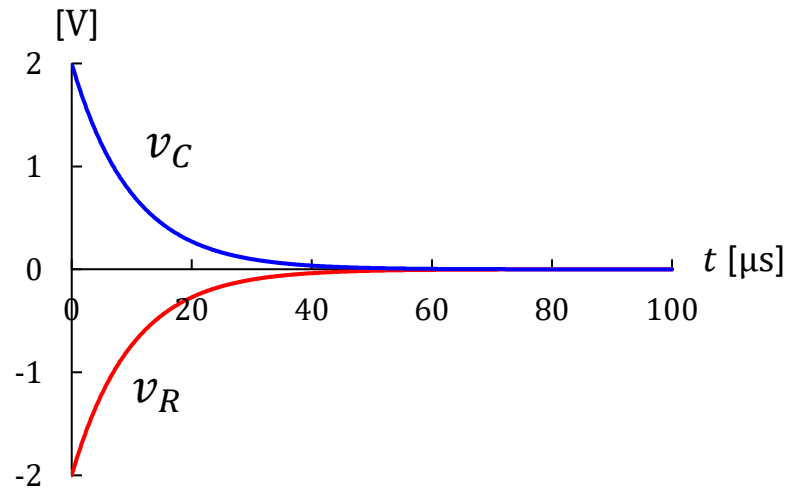
$$\begin{aligned}v_C &= \frac{q}{C} \\&= V e^{-\frac{1}{RC}t}\end{aligned}$$



# For your reference

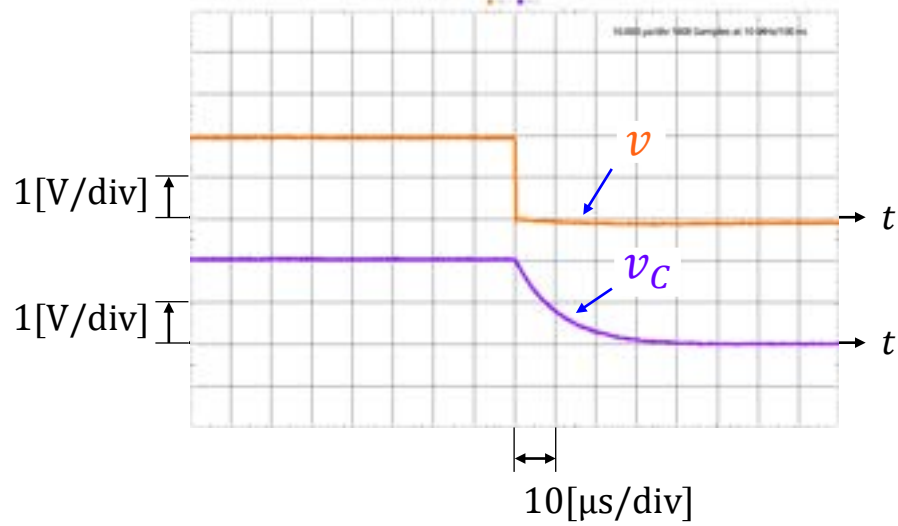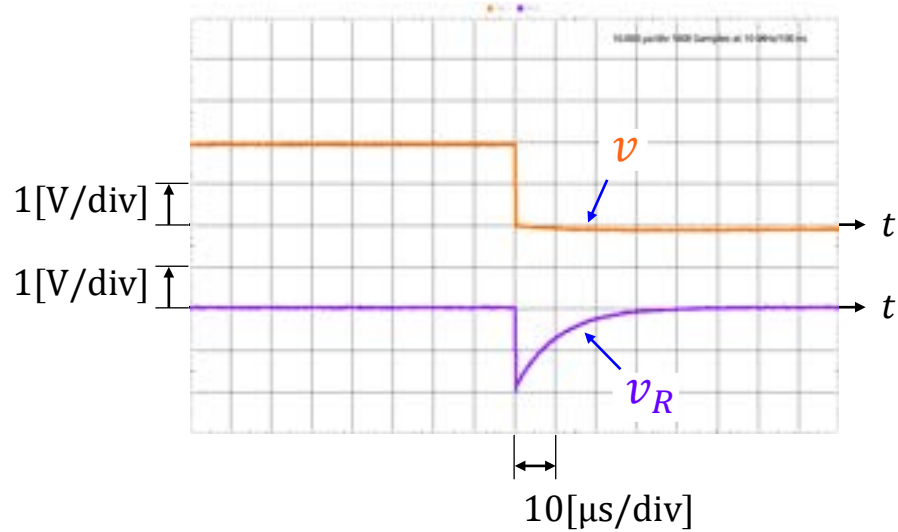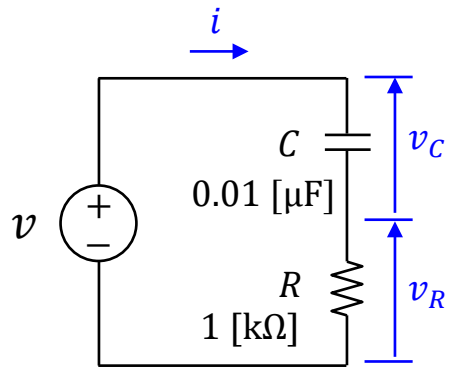


# Exercise 14.8 (Homework)


Exercise 14.8 (Homework)
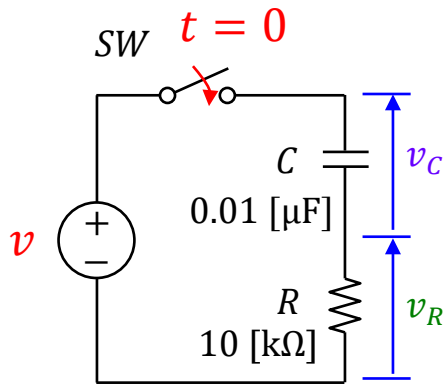
# Exercise 14.8 (Homework)

Find the phase angle  $\theta$  with which no transient response occurs in this circuit.



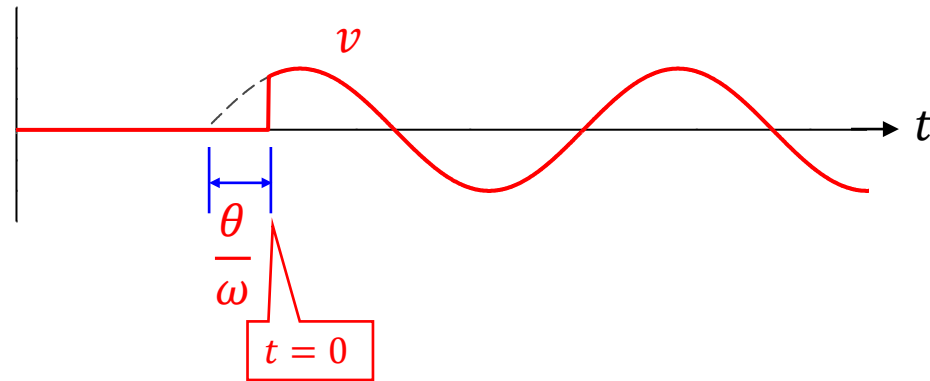
$$v = \begin{cases} 0 & (t < 0) \\ V_m \sin(\omega t + \theta) & (t \geq 0) \end{cases}$$




Initial condition: at  $t = 0, q = 0$ .

# Exercise 14.8 (Homework)

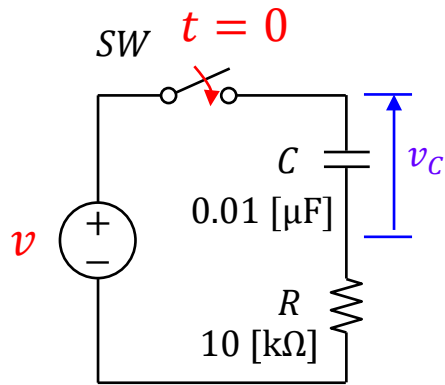

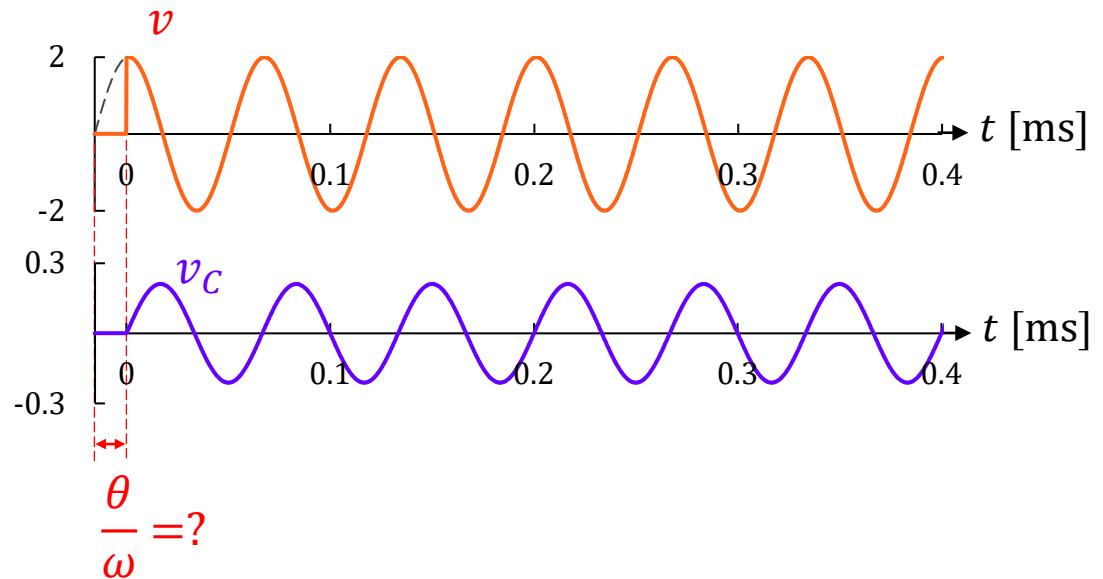
$$V_m = 2 \text{ [V]}$$
$$f = 15 \text{ [kHz]}$$
$$\theta = ? \text{ [rad]}$$




These are calculated waveforms. For  $t \geq 0$ ,  $v_C$  contains only a trigonometric waveform.

# Exercise 14.8 (Homework)

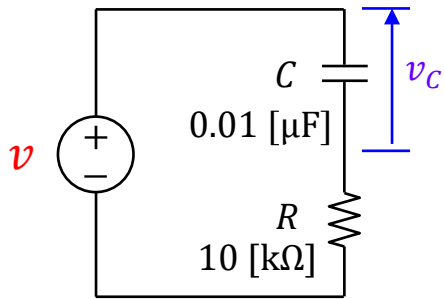
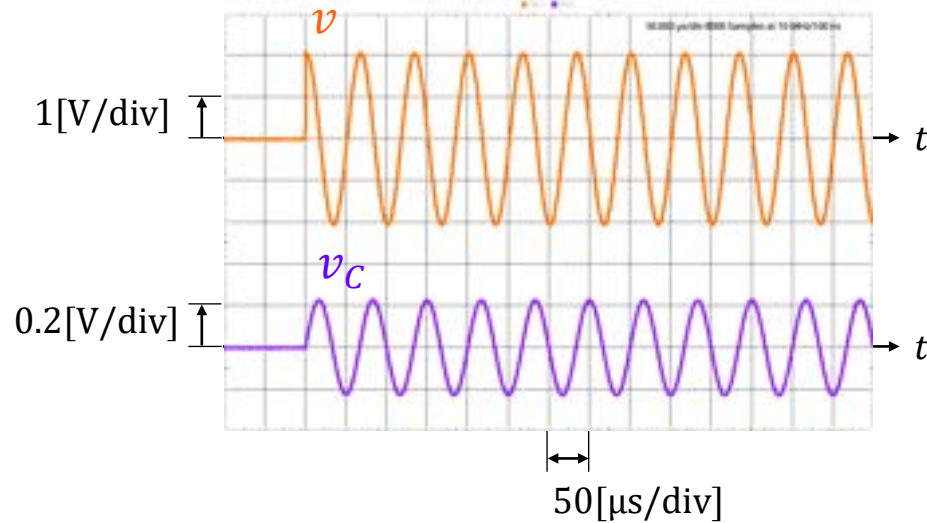
$$V_m = 2 [\text{V}]$$
$$f = 15 [\text{kHz}]$$
$$\theta = ? [\text{rad}]$$




These are experimental waveforms.

# Exercise 14.8 (Answer)

Exercise 14.8 (Answer)



# Exercise 14.8 (Answer)

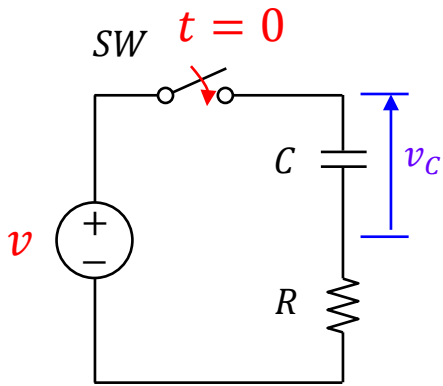

$$\text{If } \theta = \frac{\pi}{2} - \psi$$


$$v_C = \frac{(1/\omega C)V_m}{\sqrt{R^2 + (1/\omega C)^2}} \left\{ \cos(\theta + \psi) e^{-\frac{1}{RC}t} - \cos(\omega t + \theta + \psi) \right\}$$
$$= \frac{(1/\omega C)V_m}{\sqrt{R^2 + (1/\omega C)^2}} \sin \omega t$$

$$\cos(\theta + \psi) = 0$$


$v_C$  has no transient response.

If  $\theta = \frac{\pi}{2} - \psi$ , then the term of transient response is 0. Thus,  $v_C$  has no transient response.

# Exercise 14.8 (Answer)

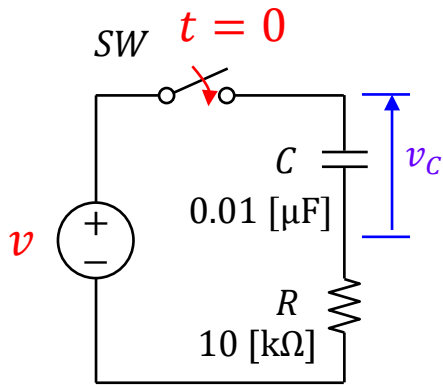

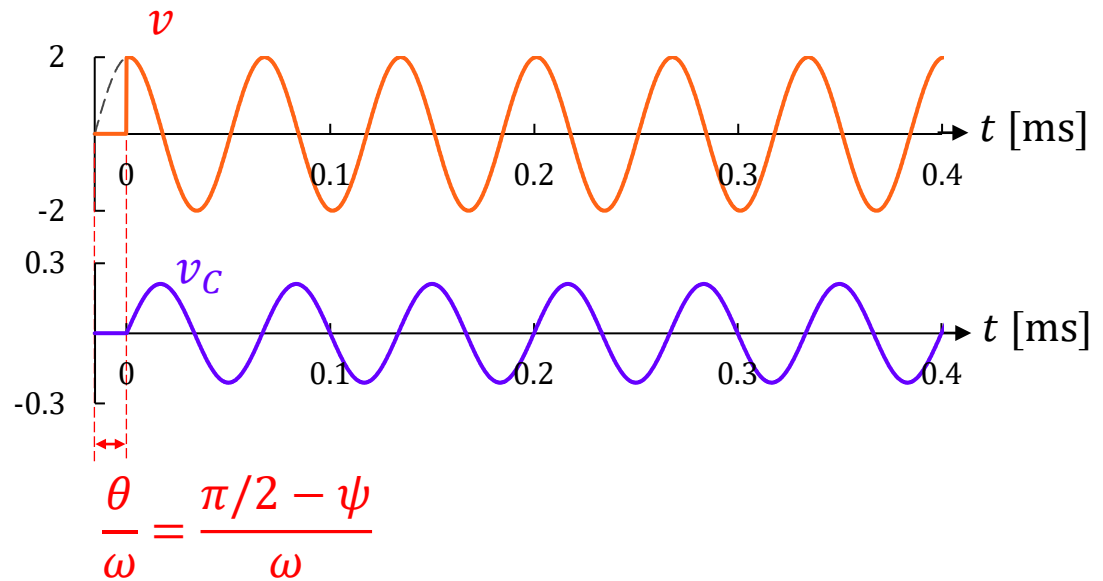
$$V_m = 2 \text{ [V]}$$
$$f = 15 \text{ [kHz]}$$
$$\theta = \frac{\pi}{2} - \psi \text{ [rad]}$$




These are calculated waveform.

# Exercise 14.8 (Answer)

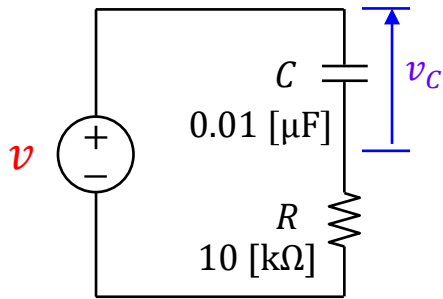
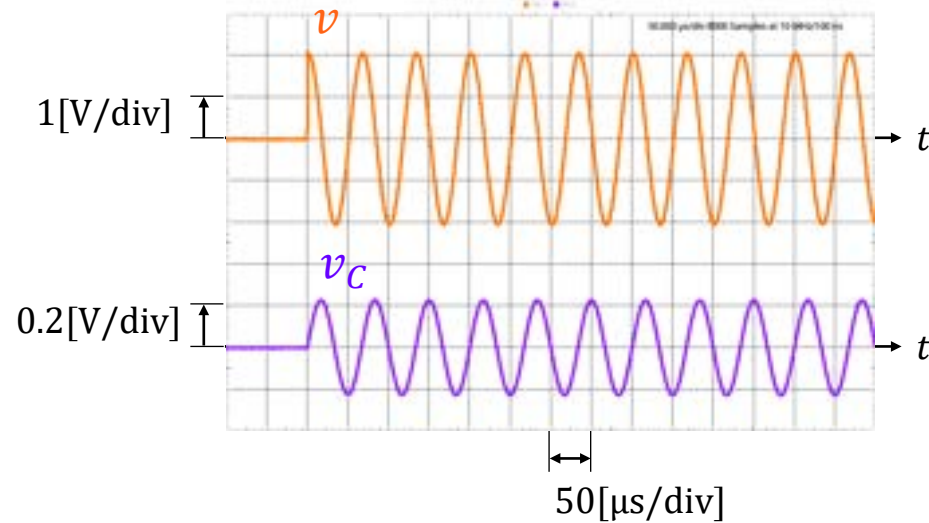
$$V_m = 2 \text{ [V]}$$
$$f = 15 \text{ [kHz]}$$
$$\theta = \frac{\pi}{2} - \psi \text{ [rad]}$$




These are experimental waveforms.

# Exercise 15.4.2 (Homework)

Exercise 15.4.2 (Homework)

# Exercise 15.4.2 (Homework)

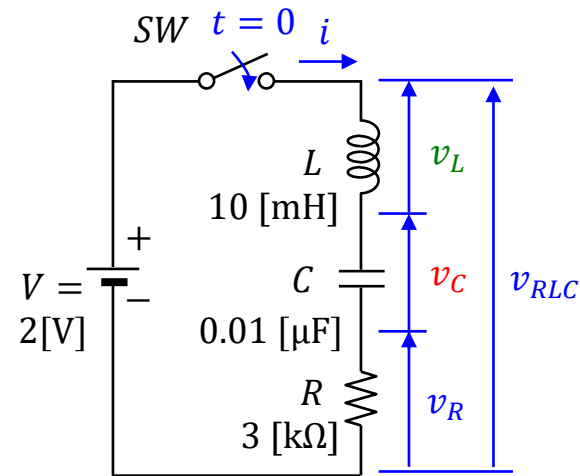

At  $t = 0$ , the switch  $SW$  is turned on.

For  $t \geq 0$ ,  $v_{RLC} = V$


Initial conditions: at  $t = 0$ ,  $i = 0$ ,  $v_C = 1\text{ [V]}$

1. Obtain  $v_R$ ,  $v_L$  and  $v_C$  for  $t \geq 0$ .
2. Draw the waveforms of  $v_R$ ,  $v_L$  and  $v_C$  for  $t \geq 0$ .

# Exercise 15.4.2 (Answers)

Exercise 15.4.2 (Answers)

# Exercise 15.4.2 (Homework)

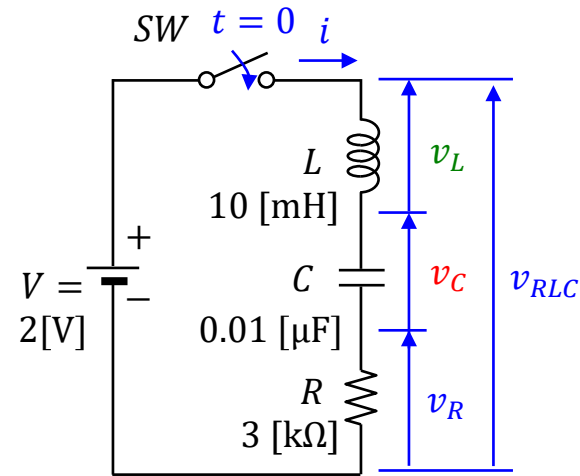

$$\left(\frac{R}{2L}\right)^2 = \left(\frac{3000}{2 \times 0.01}\right)^2 = 2.25 \times 10^{10}$$

$$\frac{1}{LC} = \frac{1}{0.01 \times 0.01 \times 10^{-6}} = 10^{10}$$

$$\left.\vphantom{\begin{matrix} \left(\frac{R}{2L}\right)^2 \\ \frac{1}{LC} \end{matrix}}\right\} \left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$

Assume that

$$q = A_1 e^{p_1 t} + A_2 e^{p_2 t} + B$$

$$\frac{V}{L} = \frac{d^2 q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{q}{LC}$$

$$= A_1 \left( p_1^2 + \frac{R}{L} p_1 + \frac{1}{LC} \right) e^{p_1 t} + A_2 \left( p_2^2 + \frac{R}{L} p_2 + \frac{1}{LC} \right) e^{p_2 t} + \frac{B}{LC}$$


$$= \frac{B}{LC}$$

$$B = CV$$

There is no difference in the process to determine  $B$  as in the previous case for

$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$

# Exercise 15.4.2 (Homework)

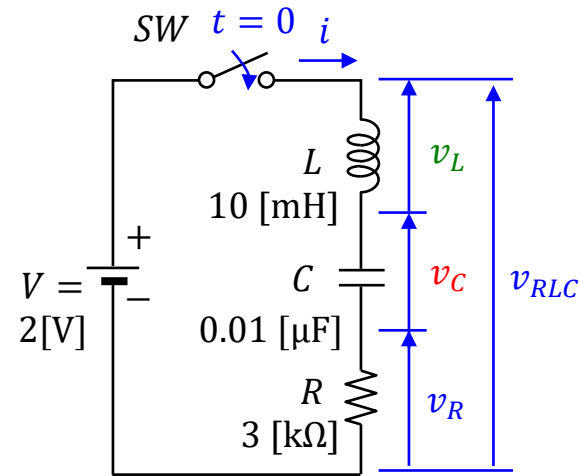

Initial conditions: at  $t = 0, i = 0, q = CV_0$

$$q = A_1 e^{p_1 t} + A_2 e^{p_2 t} + B \Leftrightarrow B = CV$$

$$\frac{dq}{dt} = i = p_1 A_1 e^{p_1 t} + p_2 A_2 e^{p_2 t}$$

$$CV_0 = A_1 + A_2 + CV$$

$$0 = p_1 A_1 + p_2 A_2$$


$$A_1 = \frac{p_2}{p_1 - p_2} C(V - V_0) = \frac{p_2}{2\beta} C(V - V_0)$$

$$A_2 = \frac{-p_1}{p_1 - p_2} C(V - V_0) = \frac{-p_1}{2\beta} C(V - V_0)$$

The difference is only in the initial condition. At  $t = 0, q = CV_0$ .



# Exercise 15.4.2 (Homework)

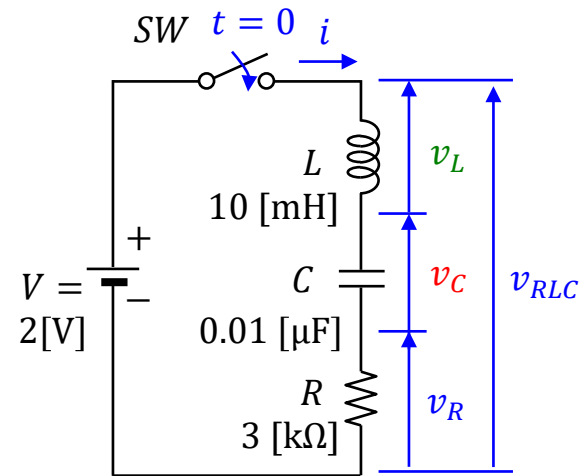

$$q = \frac{C(V - V_0)}{2\beta} (p_2 e^{p_1 t} - p_1 e^{p_2 t}) + CV$$


$$\begin{aligned} i &= \frac{dq}{dt} \\ &= \frac{p_1 p_2}{2\beta} C(V - V_0) (e^{p_1 t} - e^{p_2 t}) \\ &= \frac{(V - V_0)}{2L\beta} (e^{p_1 t} - e^{p_2 t}) \end{aligned}$$

$$v_L = L \frac{di}{dt} = \frac{(V - V_0)}{2\beta} (p_1 e^{p_1 t} - p_2 e^{p_2 t})$$

$$v_C = \frac{q}{C} = \frac{(V - V_0)}{2\beta} (p_2 e^{p_1 t} - p_1 e^{p_2 t}) + V$$

$$v_R = Ri = \frac{\alpha(V - V_0)}{\beta} (e^{p_1 t} - e^{p_2 t})$$

# Exercise 15.4.2 (Homework)

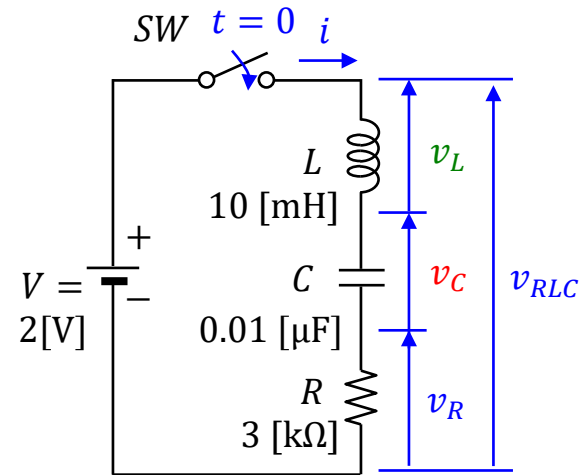

At  $t = 0$ ,

$$v_L = \frac{(V - V_0)}{2\beta} (p_1 - p_2) = \frac{(V - V_0)}{2\beta} 2\beta = V - V_0$$

$$\begin{aligned} v_C &= \frac{q}{C} = \frac{(V - V_0)}{2\beta} (p_2 - p_1) + V = \frac{(V - V_0)}{2\beta} (-2\beta) + V \\ &= V_0 \end{aligned}$$

$$v_R = \frac{\alpha(V - V_0)}{\beta} (e^{p_1 t} - e^{p_2 t}) = \frac{\alpha(V - V_0)}{\beta} (1 - 1) = 0$$

The major differences are the values of  $v_L$  and  $v_C$  at  $t = 0$ .

# Exercise 15.4.2 (Homework)

Initial conditions: at  $t = 0$ ,  $i = 0$ ,  $v_C = 1$  [V]

